


Physics 102 so far

Basic principles of electricity

- Lecture 1 – electric charge
- Lecture 2 – Coulomb's law
- Lecture 3 – the electric field
- Lecture 4 – electric potential energy and work
- Lecture 5 – electric potential

Applications of electricity – circuits

- Lecture 6 – capacitance & resistance
- Lecture 7 – simple circuits
- Lecture 8 – Kirchhoff's rules
- Lecture 9 – RC circuits

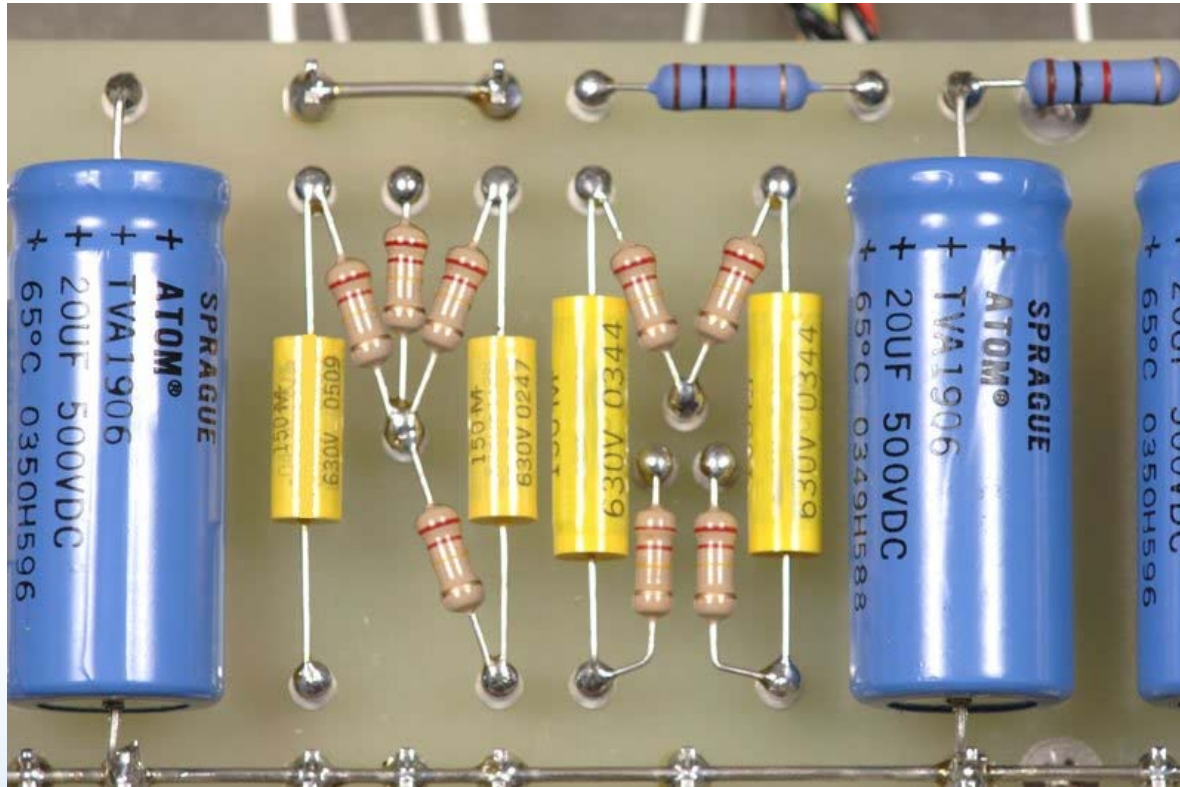


Phys 102 – Lecture 6

Circuit elements: resistors, capacitors, and batteries


Today we will learn about...

Circuit elements that:

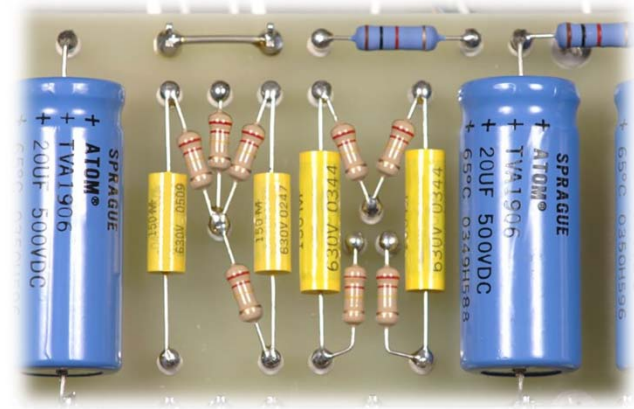
- 1) Serve as conduits for charge – wires
- 2) Pump charges around – batteries
- 3) Regulate flow of charge – resistors
- 4) Store and release charge – capacitors



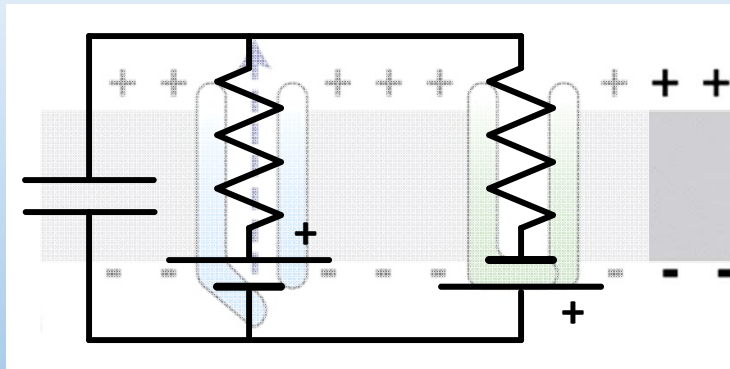These elements are idealizations of components in electronic circuits & in nature



Ex: neurons, circulatory system

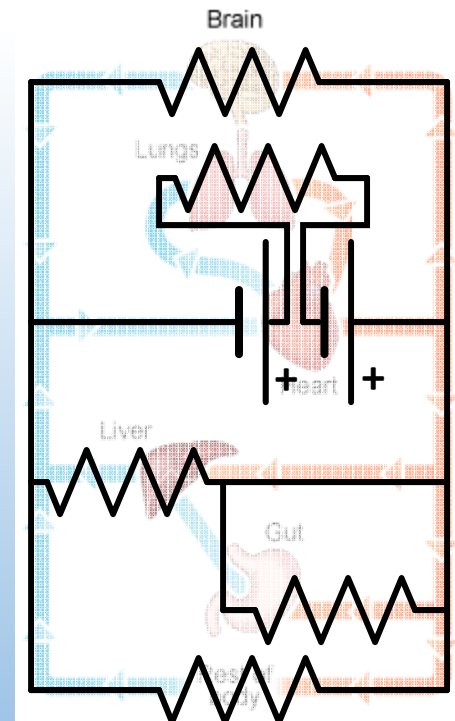

Electric current


Current – measure of flow of charge (+ charge, by convention)

Counts total charge ΔQ passing through area in a time interval Δt

$$I \equiv \frac{\Delta Q}{\Delta t}$$

Unit: A (“Amp” or “Ampere”)

1A = 1C/s

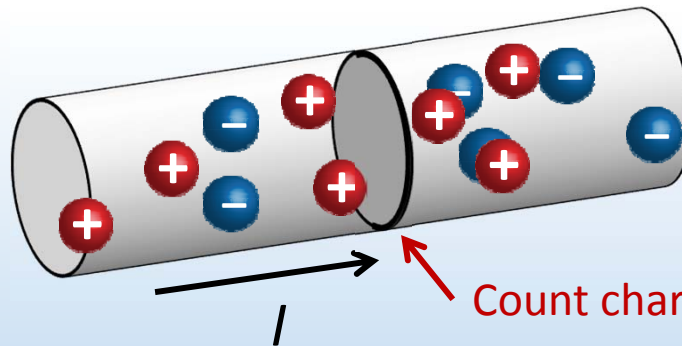


In electronic circuits, electrons ($-e$) carry current, flow opposite to current

In liquid or gas, both cations and anions can carry current



ACT: Two light bulbs

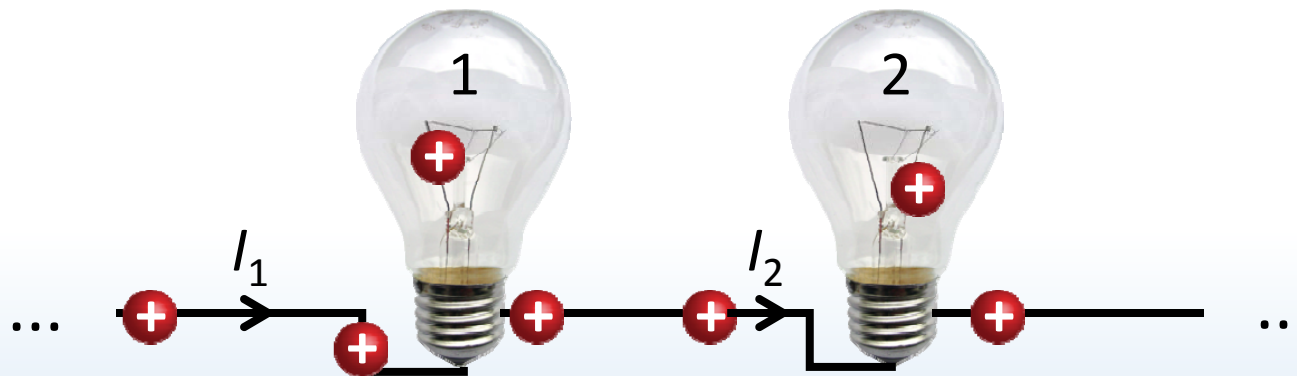Two light bulbs 1 and 2 are connected end-to-end by conducting wire. If a current I_1 flows through bulb 1, what is the current I_2 in bulb 2?



A. $I_2 < I_1$

B. $I_2 = I_1$

C. $I_2 > I_1$

Charges are conserved! Current does NOT get “used up” by light bulb


Same current entering bulb 1, leaving bulb 1, entering bulb 2, leaving bulb 2 ...

Batteries & electromotive force

Battery – maintains a constant electric potential difference (“Electromotive force” – emf ϵ)



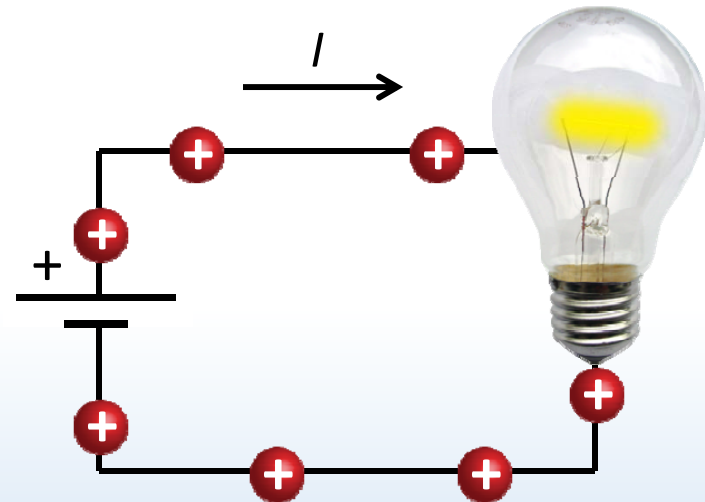Electric potential is 9 V higher at + end relative to – end. Potential difference across a circuit element is its “voltage”



Electric potential difference drives current around circuit


Battery does NOT determine how much current flows

Battery does NOT generate new charges, it “pushes” charges, like a pump



ACT: Two batteries

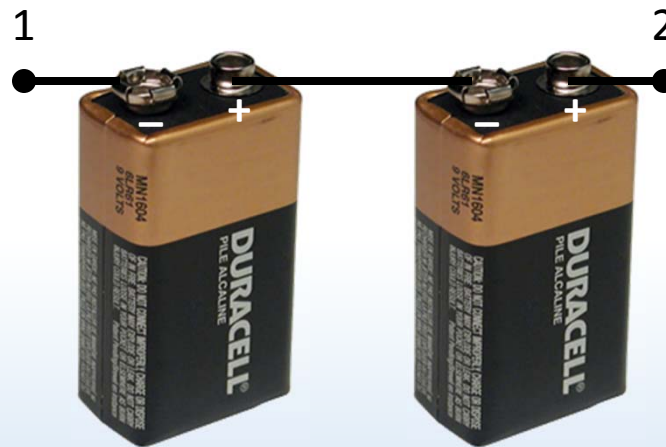Two 9 V batteries are connected end-to-end by conducting wire. What is the electric potential at point 2 relative to point 1?



A. +18 V

B. +9 V


C. -18 V

D. -9 V

Battery 1 increases electric potential by 9 V
Battery 2 increases electric potential by another 9 V

Resistance and Ohm's law

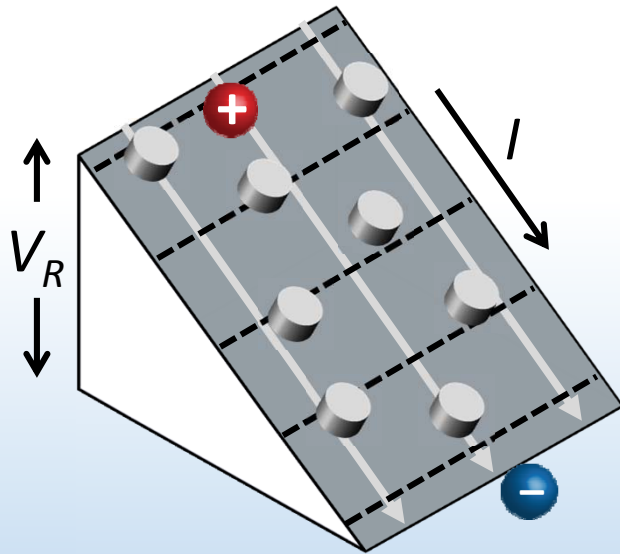Moving charges collide with each other, ions, defects inside material
Flow rate depends on electric potential difference



$$I \propto V_R \quad \leftarrow \text{Double potential difference, double current}$$

DEMO

Resistance – proportionality constant between current and voltage

Ohm's law: $R \equiv \frac{V_R}{I}$ Units: Ω ("Ohms")

Potential difference causes current to flow ("downhill", by convention)
Resistance regulates the amount of flow

Physical resistance

Resistor – circuit element designed to have resistance



Resistance depends on material parameters and geometry

Resistivity – density of scatterers

$$R = \rho \frac{L}{A}$$

Length – the longer the resistor, the more scattering

Cross sectional area – the wider the resistor, the more charges flow

DEMO

| Material | ρ ($\Omega \cdot \text{m}$) |
|------------|------------------------------------|
| Copper | 1.7×10^{-8} |
| Iron | 9.7×10^{-8} |
| Sea water | 0.22 |
| Muscle | 13 |
| Fat | 25 |
| Pure water | 2.4×10^5 |

Basis for measuring body fat percentage






ACT: CheckPoint 1.1

Which of the following three copper resistors has the *lowest* resistance?

A.


10%

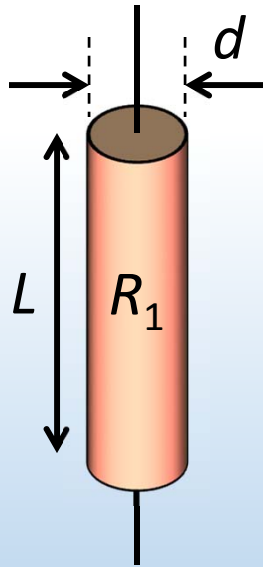

$$R_1 = \rho \frac{L}{A}$$

B.


62%

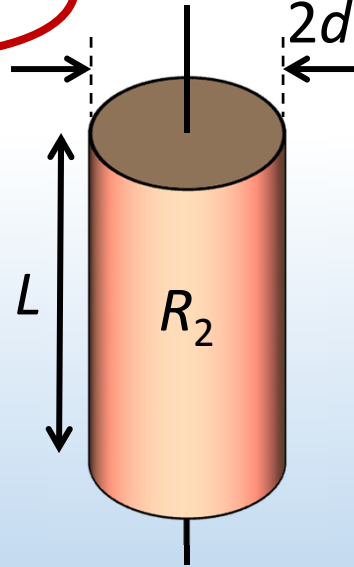

$$R_2 = \rho \frac{L}{4A}$$

C.

28%

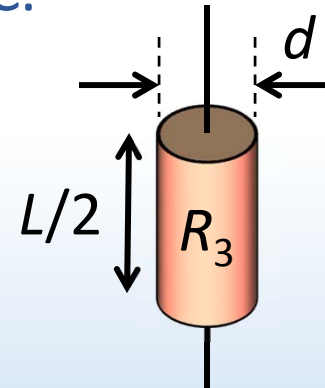

$$R_3 = \rho \frac{L}{2A}$$

Power generated and dissipated

Battery does work pumping charges through circuit

Ex: a 9 V battery does 9 J of work per 1 C of charge pumped

Where does the energy come from? Chemical energy in battery

Power – rate of energy conversion

$$P_{batt} = \frac{\Delta U}{\Delta t} = \frac{\Delta Q}{\Delta t} \varepsilon = I \varepsilon$$

Units: W (“Watts”)
1 W = 1 J/s = 1 V A


Resistor dissipates electric potential energy

Charges lose electric potential energy in collisions inside resistor

$$P_{diss} = IV_R = I^2 R = \frac{V_R^2}{R}$$

Where does the energy go? Heat and/or light

Calculation: light bulb filament

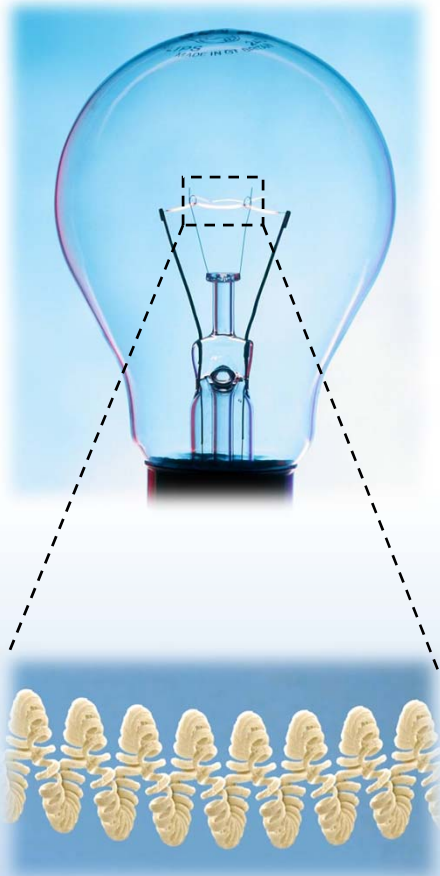

An incandescent light bulb is essentially a resistor that dissipates energy as heat and light. A typical light bulb dissipates 60 W with 120 V from an outlet.

The resistive element is a thin (40- μm diameter) *filament* of tungsten. How long must the filament be?

Approach: find resistance of filament, relate it to length

$$P = IV = I^2 R = \frac{V^2}{R} \quad R = \rho \frac{L}{A}$$


$$L = \frac{AR}{\rho} = \frac{AV^2}{\rho P} = \frac{\pi(20 \times 10^{-6} \text{ m})^2 (120 \text{ V})^2}{(5 \times 10^{-7} \Omega \cdot \text{m})(60 \text{ W})} = 0.6 \text{ m}$$

Resistivity of tungsten (at temp. of filament): $5.0 \times 10^{-7} \Omega \cdot \text{m}$

About 2 ft !

Capacitance

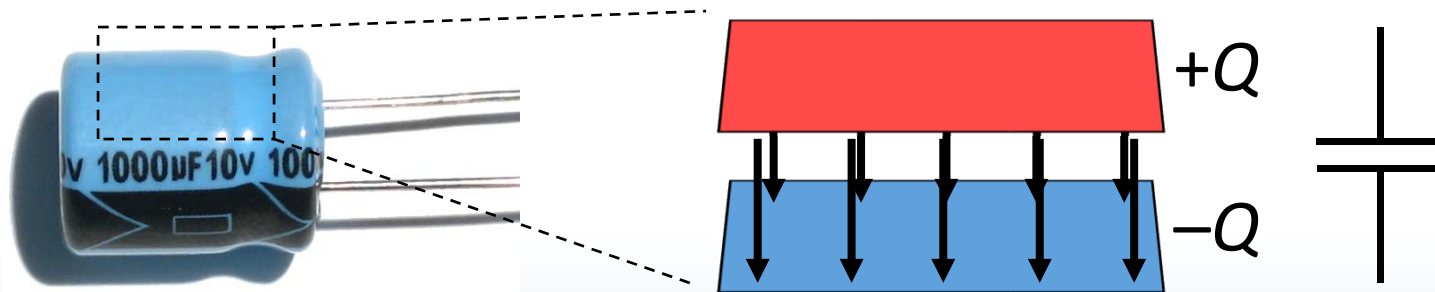Capacitor – circuit element that stores separated charge
Consists of two conductors separated by a small gap



Capacitance – measures the ability to store charge Q given a voltage V_C applied between the conductors

$$C \equiv \frac{Q}{V_C}$$


Units: F ("Farad")
 $1 \text{ F} = 1 \text{ C/V}$

Parallel plate capacitor

Capacitor made up of two large conducting plates of area A separated by a small gap d

Electric field is uniform between plates (Recall Lect. 3)

$$E \propto \frac{Q}{\epsilon_0 A}$$

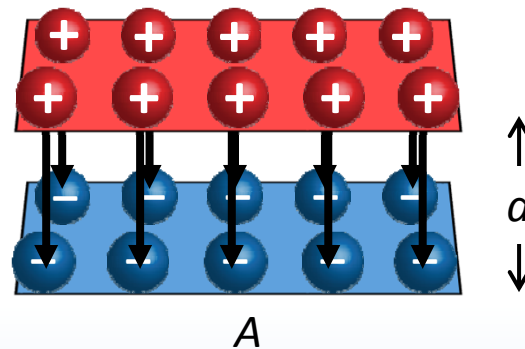

Field strength \propto density of field lines \propto density of charges

Work to move $+q$ charge from $+$ to $-$ plate (Recall Lect. 4)

$$W_E = +qEd = -(U_- - U_+) \quad V_+ - V_- = \frac{U_+ - U_-}{q} = +Ed = V_C$$



Capacitor voltage

For a parallel plate capacitor: $C = \frac{\epsilon_0 A}{d}$

Capacitance depends on geometry

Capacitor energy

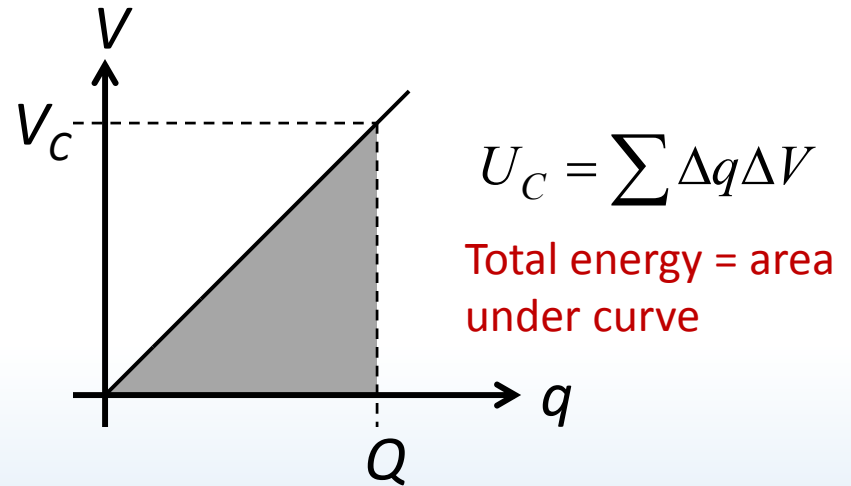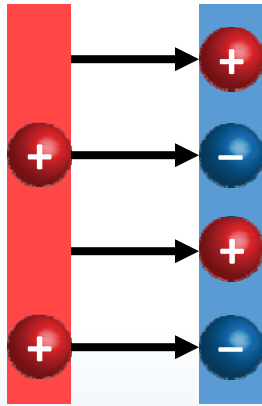Separated charges have potential energy (Recall Lect. 4)



Imagine transferring + charge from one plate to the other
Each time add Δq , electric field and voltage increase by ΔE and ΔV

$$U_C = \frac{1}{2} Q V_C = \frac{1}{2} C V_C^2 = \frac{1}{2} \frac{Q^2}{C}$$

Important factor of $\frac{1}{2}$! Don't confuse this equation with $U = qV$ for individual charge q

Why separate charge?


A way to store *and* release energy



Camera flash



Defibrillator

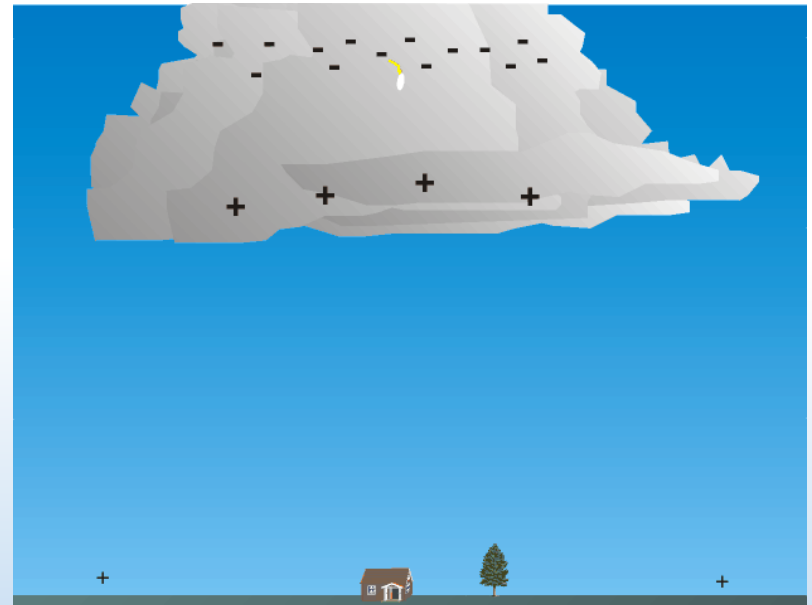

Lightning strike



ACT: Parallel plates

A parallel plate capacitor carries a charge Q . The plates are then pulled a small distance further apart.



What happens to the charge Q on each plate?

A. Q increases


B. Q stays constant

C. Q decreases

Charge is conserved! There are no wires for charges to flow through, so they stay on the capacitor plates

Checkpoint 2

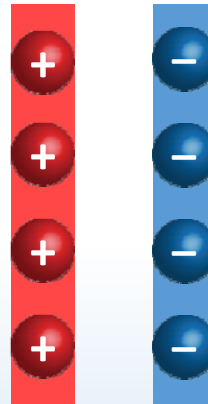A parallel plate capacitor carries a charge Q . The plates are then pulled a small distance further apart.



DEMO

The capacitance increases $C = \epsilon_0 A / d$

True **False**

The electric field increases $E = Q / \epsilon_0 A$

True **False**

The voltage between the plates increases $V_C = Ed$

True False

The energy stored increases $U_C = \frac{1}{2} C V_C^2$

True False

Dielectrics


Imagine placing insulating material (dielectric) between plates

External field polarizes dielectric
Excess $+q$ and $-q$ charges build up on opposite planes

Parallel planes of $+q$ and $-q$
create own E field, cancel out
part of external E field

$$\vec{E}_{diel} = \frac{\vec{E}_{ext}}{\kappa}$$

Dielectric constant $\kappa > 1$

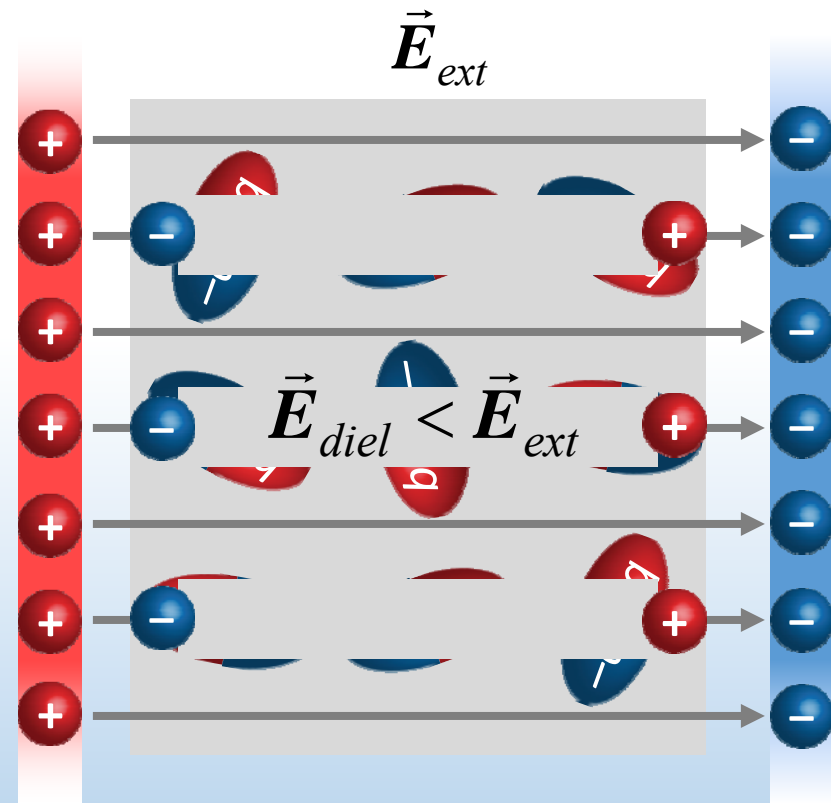

(Recall Lect. 3 – conductors)

Dielectric constant κ

Dielectric constant κ measures how much a material is polarized by electric field

Since $\vec{E} = \vec{E}_0 / \kappa$, need less E (or V) to store same Q , so $C = Q/V$ increases:

Capacitance with
dielectric


Dielectric constant

$$C = \kappa C_0$$

Capacitance without
dielectric

| Material | $\kappa (> 1)$ |
|---------------|----------------|
| Vacuum | 1 (exactly) |
| Air | 1.00054 |
| Rubber | 3-4 |
| Glass | 5 |
| Cell membrane | 7-9 |
| Pure water | 80 |

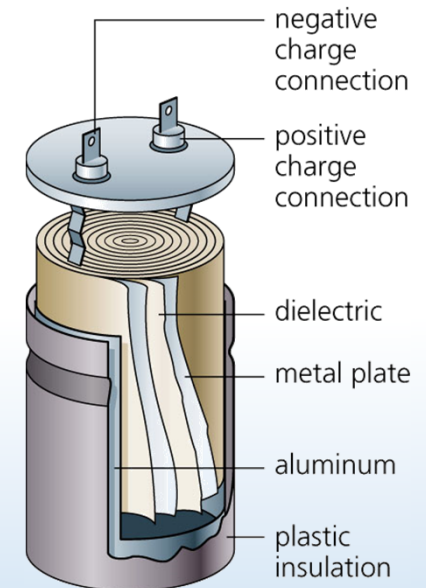
Capacitance depends on material parameters
(dielectric) and geometry



Calculation: capacitance of a cell

Channels in a cell's membrane create a charge imbalance (recall Lect. 5), with + charge outside, – inside. The separated charge gives the cell *capacitance*, with the membrane acting as a dielectric ($\kappa = 7$).

Based on EXAM 1, FA09

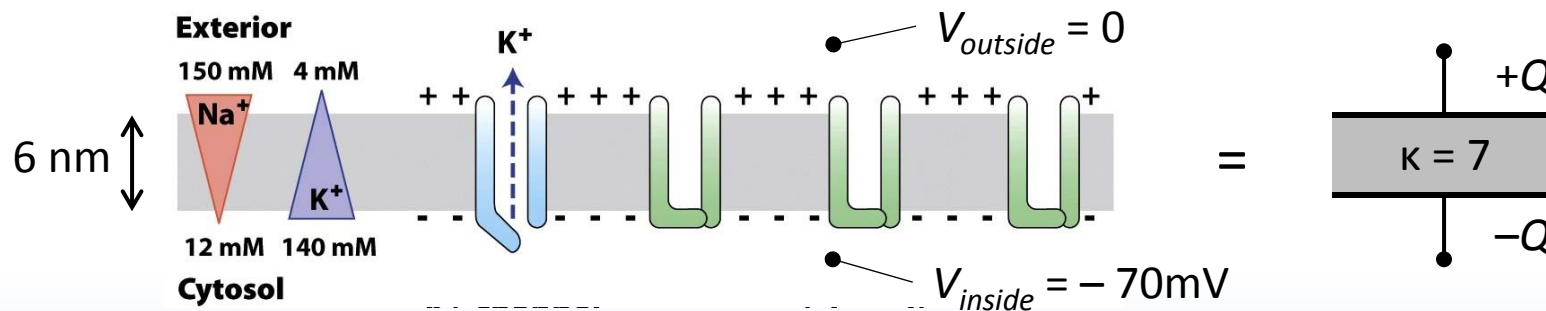

What is the capacitance of a $1\text{-}\mu\text{m}^2$ flat patch of cell?

$$C = \kappa \epsilon_0 \frac{A}{d} = 7(8.85 \times 10^{-12}) \frac{(10^{-6} \text{ m})^2}{6 \times 10^{-9} \text{ m}} = 0.01 \text{ pF}$$

At rest, a cell has a -70 mV voltage across it. How much charge is necessary to generate this voltage?


$$Q = CV = (10^{-14} \text{ F})(0.07 \text{ V}) = 0.7 \text{ fC} \quad N = \frac{Q}{e} = \frac{7 \times 10^{-16} \text{ C}}{1.6 \times 10^{-19} \text{ C}} \approx 4,500$$

Not very much! <1 excess ion per $10 \times 10 \text{ nm}^2$



ACT: Capacitor dielectric

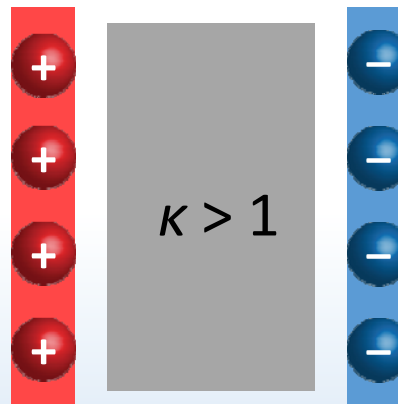A parallel plate capacitor carries a charge Q . A dielectric with $\kappa > 1$ is inserted between the plates.



DEMO

What happens to energy U_C stored in the capacitor?

A. U_C increases

B. U_C stays constant

C. U_C decreases

Approach: what stays constant, what changes?

Q stays constant, C increases

$$U_C = \frac{1}{2} QV = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C}$$

Summary of today's lecture

- Batteries generate emf ϵ , pump charges
- Resistors *dissipate* energy as power: $P = IV$
Resistance: how difficult it is for charges to get through: $R = \rho L/A$
Voltage determines *current*: $V = IR$
Ideal wires have $R = 0$, $V = 0$
- Capacitors *store* energy as separated charge: $U = \frac{1}{2}QV$
Capacitance: ability to store separated charge: $C = \kappa\epsilon_0 A/d$
Voltage determines *charge*: $V = Q/C$
- Don't mix capacitor and resistor equations!