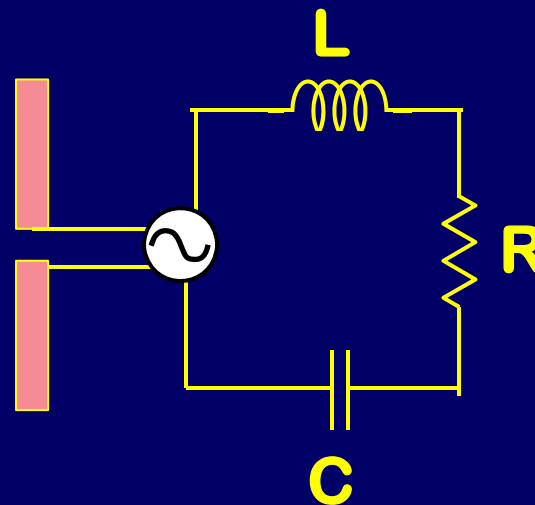


Physics 102: Lecture 13

RLC circuits & Resonance



Review: AC Circuit

- $I = I_{\max} \sin(2\pi ft) = I_L = I_R = I_C$

- $V_R = I_{\max} R \sin(2\pi ft)$

V_R in phase with I

- $V_C = I_{\max} X_C \sin(2\pi ft - \pi/2)$



V_C lags I "ICE"

$$V_{C,\max} = I_{\max} X_C \quad X_C = 1/\omega C$$

- $V_L = I_{\max} X_L \sin(2\pi ft + \pi/2)$

V_L leads I "ELI"
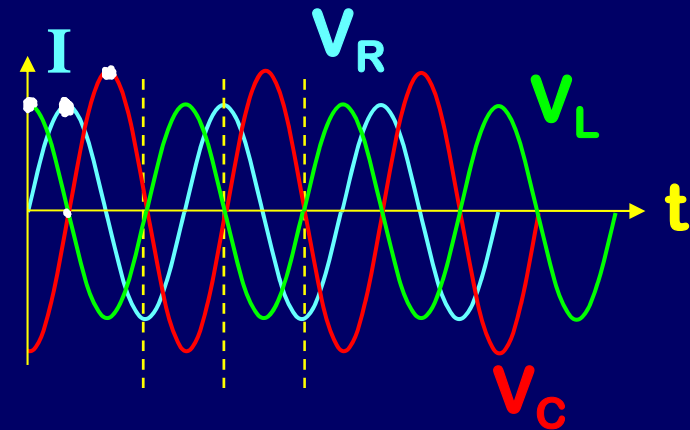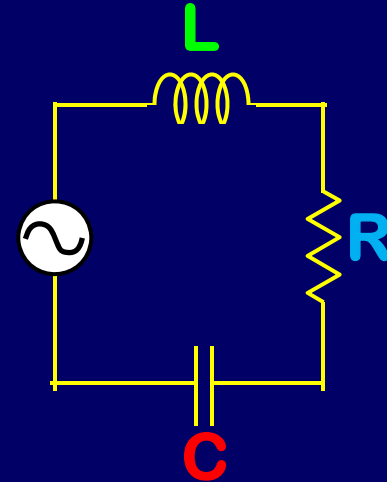
$$V_{L,\max} = I_{\max} X_L \quad X_L = \omega L$$




Goal:

write down equations for all of the voltages



$$V_R = I_{\max} R \sin(2\pi ft)$$



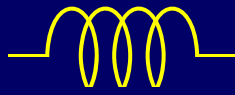
$$V_L = I_{\max} X_L \sin(2\pi ft + \pi/2)$$


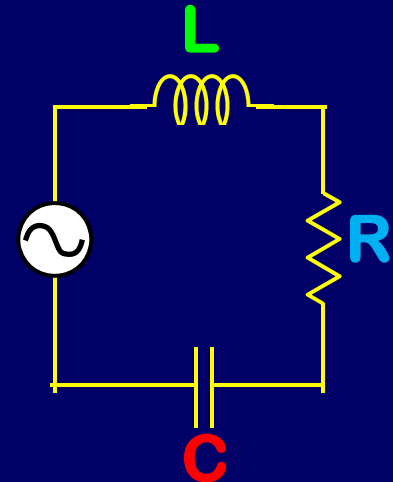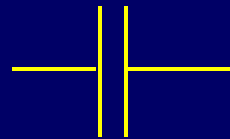
$$V_C = I_{\max} X_C \sin(2\pi ft - \pi/2)$$



The only element left: generator!

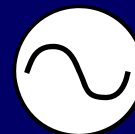


$$V_{gen} = V_{gen,max} \sin(2\pi ft + \underline{\phi})$$

ϕ : “phase angle”

Like a shift in time!

$\phi < 0$: shift forward lag (ex: C)

$\phi > 0$: shift backward lead (ex: L)

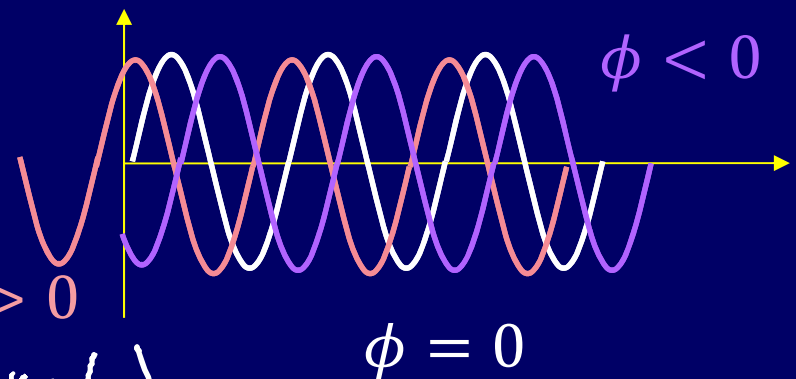

Kirchhoff: generator voltage

- Instantaneous voltage across generator (V_{gen}) must equal sum of voltage across all of the elements at all times:

$$V_{\text{gen}}(t) = V_R(t) + V_C(t) + V_L(t)$$



~~$$V_{\text{gen,max}} = V_{L,\text{max}} + V_{R,\text{max}} + V_{C,\text{max}}$$~~

What is $V_{\text{gen,max}}$?

Define impedance Z : $V_{\text{gen,max}} \equiv I_{\text{max}} Z$

Like: $V=IR$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

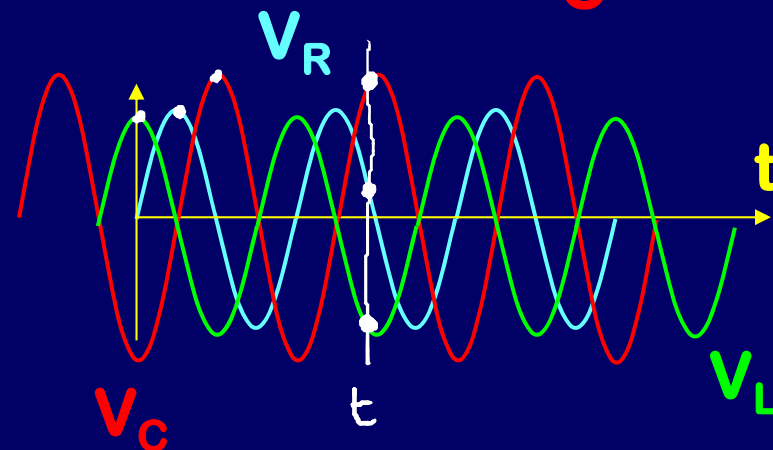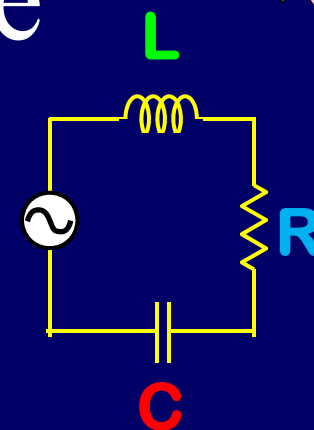


One last ingredient: is the generator voltage leading or lagging the current?

$$I = I_{max} \sin(2\pi ft)$$

$$V_{gen} = I_{max} Z \sin(2\pi ft + \phi)$$

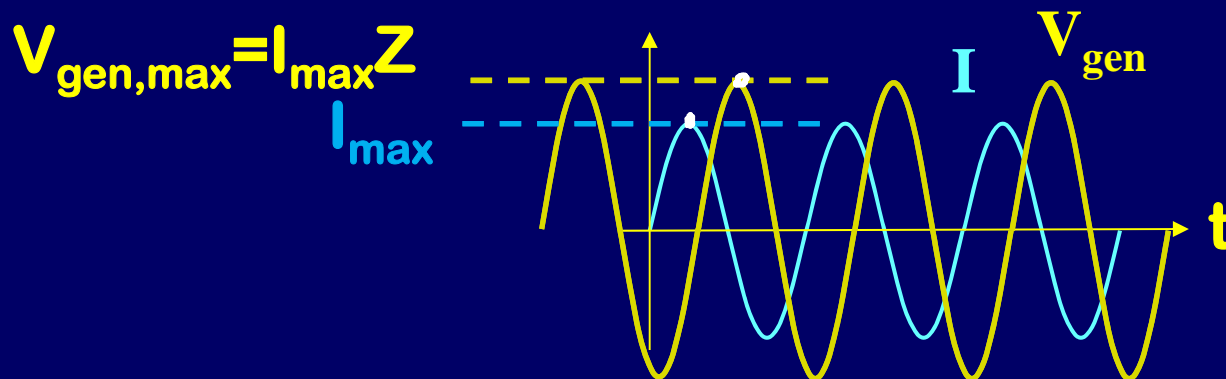Phase angle: $\tan(\phi) = \frac{(X_L - X_C)}{R}$



This example:
 $\phi < 0$, **voltage**
is lagging

Example



Problem Time!

An AC circuit with $R = 2 \Omega$, $C = 15 \text{ mF}$, and $L = 30 \text{ mH}$ is driven by a generator with voltage $V(t) = 2.5 \sin(8\pi t)$ Volts. Calculate the maximum current in the circuit, and the phase angle.

$$I_{\max} = V_{\text{gen,max}} / Z$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$


$$Z = \sqrt{2^2 + \left(8\pi \times .030 - \frac{1}{8\pi \times .015}\right)^2} = 2.76 \Omega$$

$$I_{\max} = 2.5 / 2.76 = 0.91 \text{ Amps}$$

$$\tan(\phi) = \frac{X_L - X_C}{R} = \frac{(8\pi \times .030 - \frac{1}{8\pi \times .015})}{2} \Rightarrow \phi = -43.5^\circ$$

$$X_L = 2\pi f L$$

$$X_C = \frac{1}{2\pi f C}$$

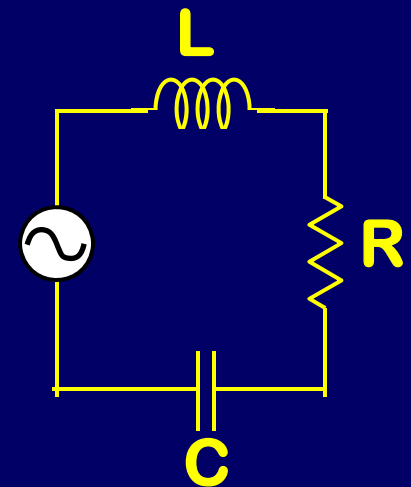

Power in RLC circuits

- The voltage generator supplies power.
 - Only resistor dissipates power.
 - Capacitor and Inductor store and release energy.
- $P(t) = I(t)V_R(t)$ oscillates so sometimes power loss is large, sometimes small.
- Average power dissipated by resistor:

$$\overline{P} = \frac{1}{2} I_{\max} V_{R,\max} = I_{\text{rms}} V_{R,\text{rms}}$$

$$= \frac{1}{2} I_{\max} V_{\text{gen},\max} \cos(\phi)$$

$$= I_{\text{rms}} V_{\text{gen},\text{rms}} \cos(\phi)$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

If there is only a resistor, $\phi = 0$




ACT: Power dissipation

Which one of these circuits dissipates the most average power?



$$V_{\text{gen,max}} = 10 \text{ V}$$

$$V_{\text{gen,max}} = 100 \text{ V}$$

$$\varepsilon = 1 \text{ V}$$

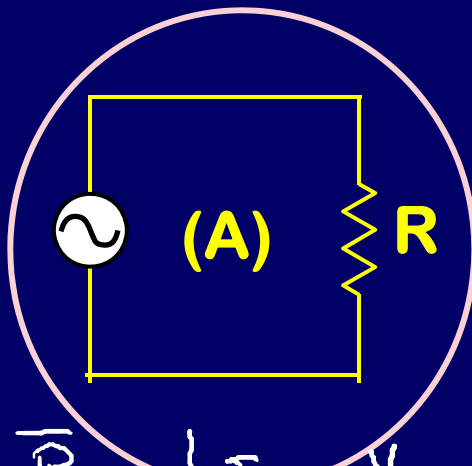

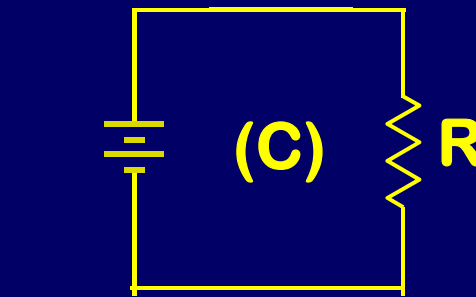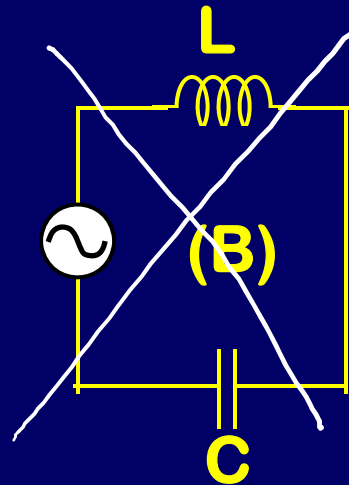
$$\begin{aligned} \text{A) } \overline{P} &= \frac{1}{2} I_{\text{max}} V_{A,\text{max}} \\ &= \frac{1}{2} I_{\text{max}} V_{\text{gen,max}} \\ &= \frac{1}{2} \frac{V_{\text{gen,max}}^2}{R} = \frac{50}{R} \end{aligned}$$



$$\begin{aligned} \text{C) } P &= I \varepsilon \\ &= \frac{\varepsilon^2}{R} \\ &= \frac{1}{R} \end{aligned}$$

Kirchhoff: generator voltage

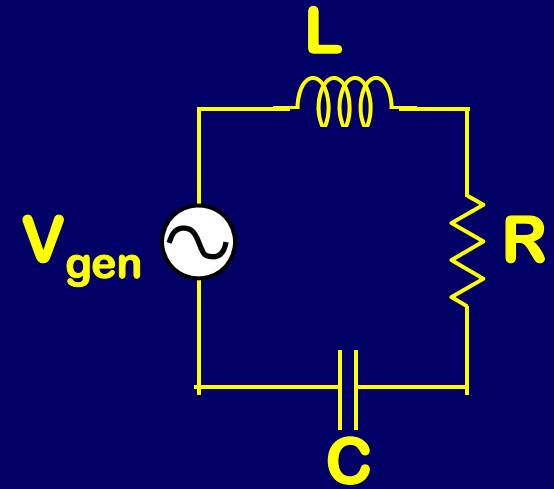


Write down Kirchhoff's Loop Equation:

$$V_{\text{gen}}(t) = \cancel{V_L(t)} + V_R(t) + \cancel{V_C(t)} \text{ at every instant of time}$$


If the frequency is just right...

$$V_{\text{gen}}(t) = V_R(t)$$

Resonance!

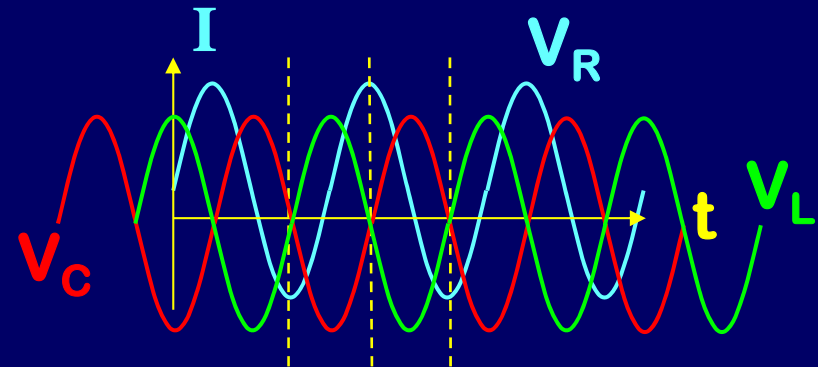


Examples of mechanical resonance

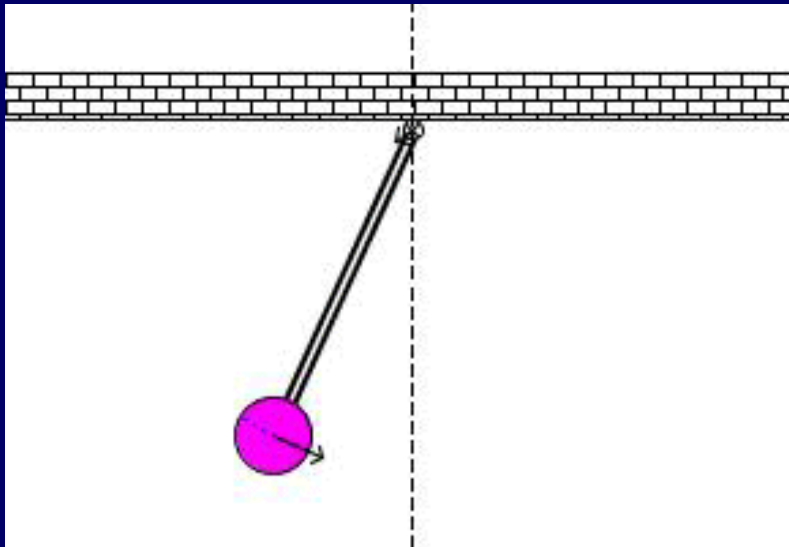

Pendulum:

$$\omega_0 = \sqrt{g/l}$$

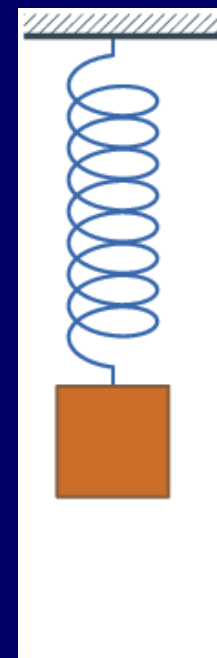


Mass on a spring:

$$\omega_0 = \sqrt{k/m}$$

Common features:

- **Energy converts between two forms (kinetic & potential)**
- **Weak input at ω_0 leads to a big response!**

Resonance!

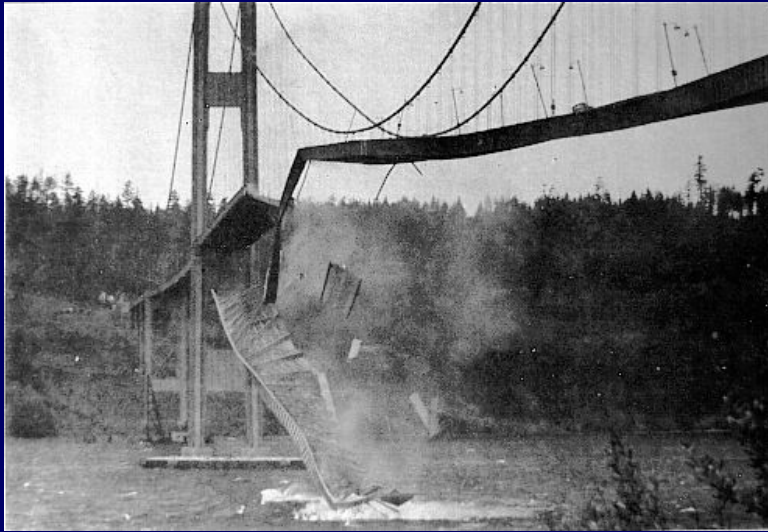


Tacoma Narrows Bridge




Millennium Bridge

Electric energy

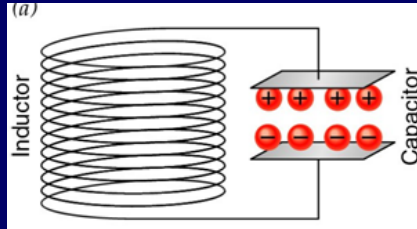


$$V_C = V_{C, \max}$$

$$V_L = -V_{L, \max}$$

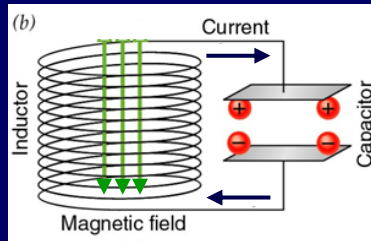


$$V_C = 0$$


$$V_L = 0$$

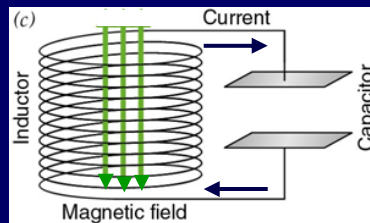

Magnetic energy


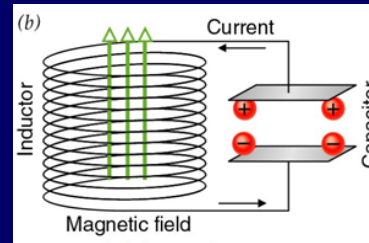


Magnetic energy

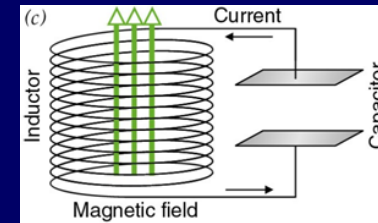

$$V_C = 0$$

$$V_L = 0$$

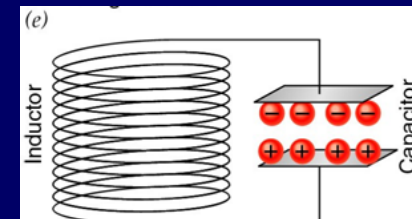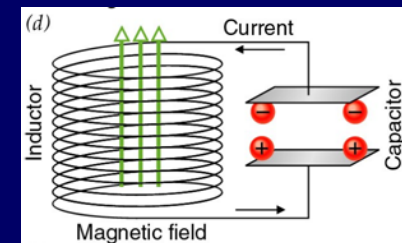

Electric energy


$$V_C = -V_{C, \max}$$

$$V_L = V_{L, \max}$$

RLC circuit:
Electrical
resonance

$$f_0$$

Resonance

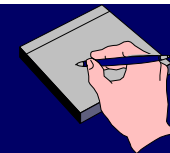

R is independent of f

X_L increases with f


$$X_L = 2\pi fL$$

X_C decreases with f

$$X_C = 1/(2\pi fC)$$

Z: X_L and X_C subtract

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

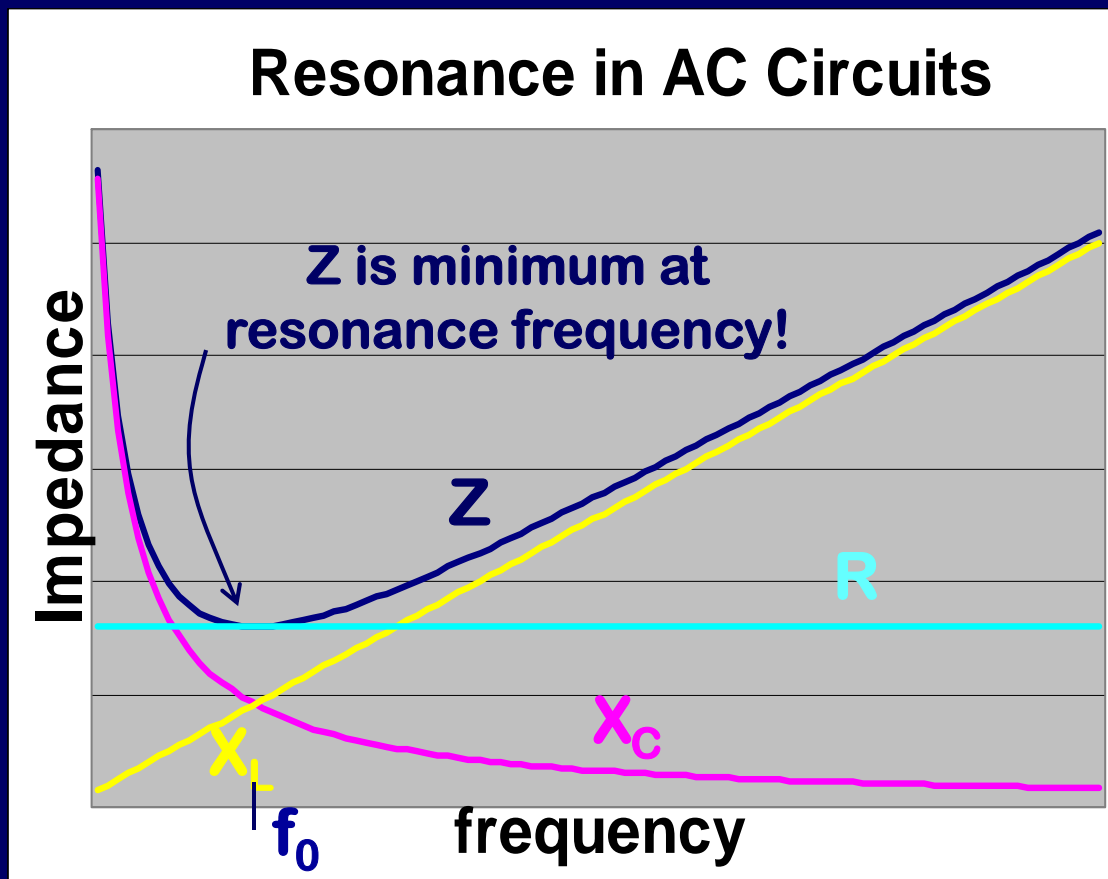


Resonance: $X_L = X_C$

$$V_{L, \max} = V_{C, \max}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$2\pi f_0 L = \frac{1}{2\pi f_0 C}$$
$$\tan \phi = \frac{X_L - X_C}{R} = 0$$

Resonance

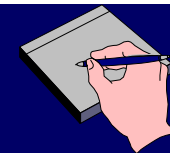

R is independent of f

X_L increases with f

$$X_L = 2\pi fL$$


X_C decreases with f

$$X_C = 1/(2\pi fC)$$

Z: X_L and X_C subtract

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$


Resonance: $X_L = X_C$

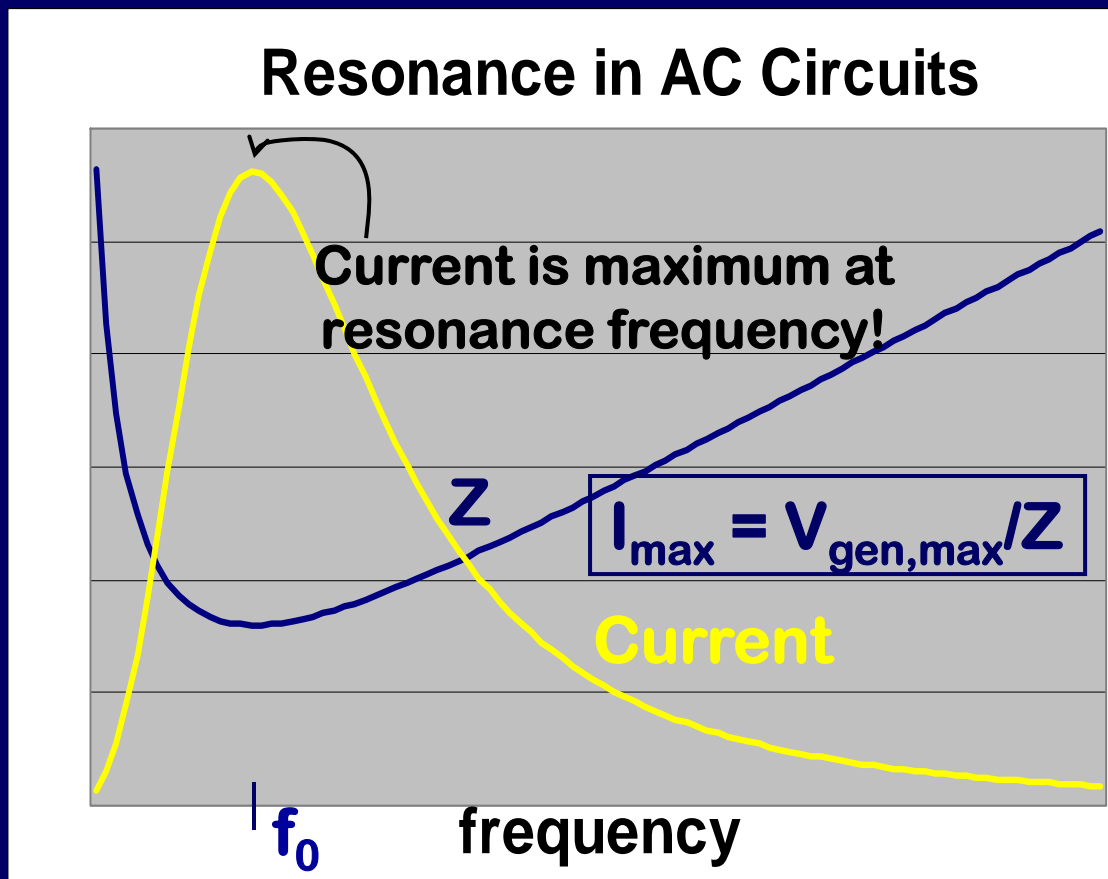

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

CheckPoint 14.1

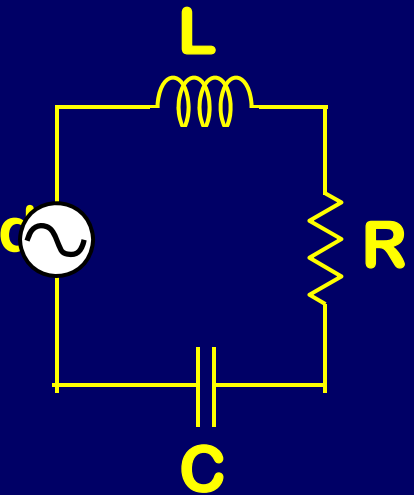As the frequency of the circuit is either raised above or lowered below the resonant frequency, the impedance of the circuit:




48% Always increases

27% Only increases for lowering the frequency




25% Only increases for raising the frequency

Z is minimum at f_0 !

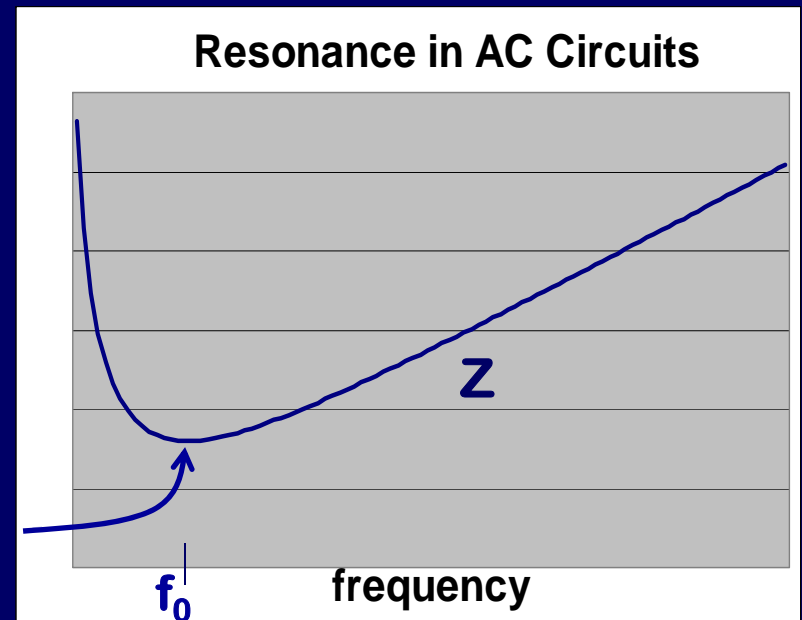

Any other frequency will have higher Z !

What is it good for?

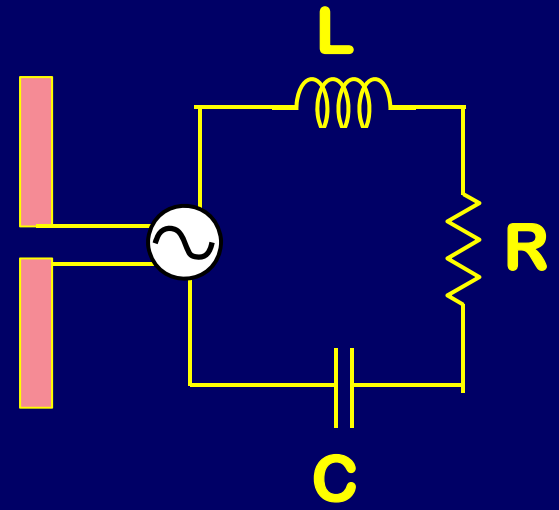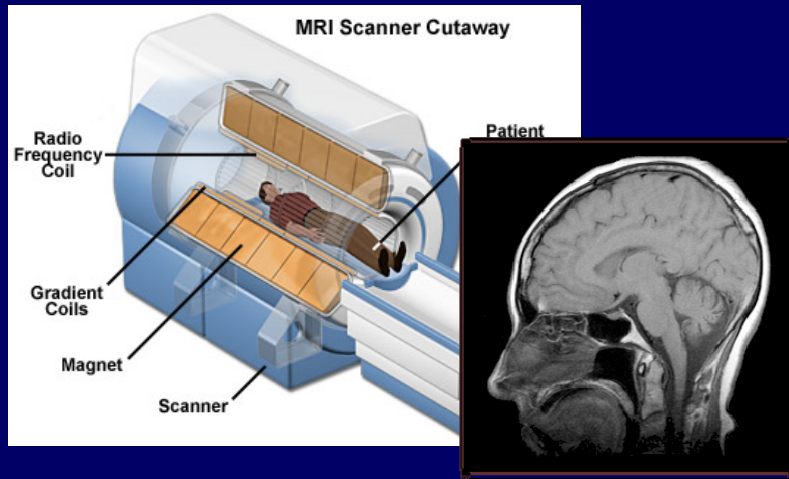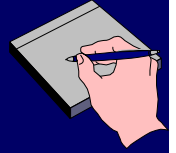

- Current through circuit depends on frequency (maximum at resonance frequency f_0)
 - Radio receiver
 - NMR/MRI
 - Picks out radio station freq f_0
 - Picks out signal from protons at f_0

Magnetic Resonance Imaging

Nobel Prize Medicine, 2003



Lauterbur, UIUC




Mansfield




Faraday's Law + RLC circuit!

Example

Resonance in Radios

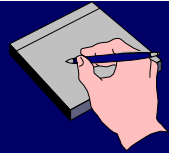

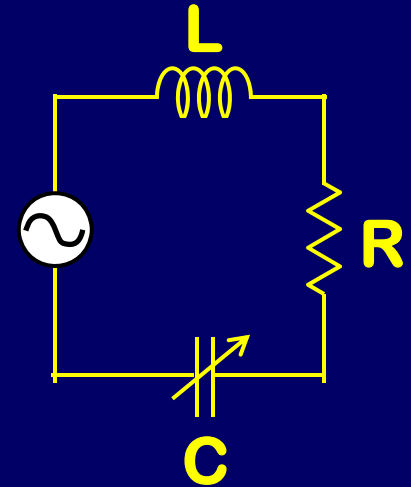An AC circuit with $R = 2 \, \Omega$, $L = 0.30 \, \mu\text{H}$ and variable capacitance is connected to an antenna to receive radio signals at the resonance frequency. If you want to listen to music broadcasted at 96.1 MHz, what value of C should be used?



$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$C = \frac{1}{(2\pi f_0)^2 L} = \frac{1}{(2\pi \times 96.1 \times 10^6)^2 \times 0.30 \times 10^{-6}} = 9.1 \times 10^{-12} \, \text{F}$$



ACT: Radios



Your radio is tuned to FM 96.1 MHz and want to change it to FM 105.9 MHz, which of the following will work.

1. Increase Capacitance
2. Decrease Capacitance
3. Neither, you need to change R

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Higher frequency needs smaller capacitor so it can develop voltage quicker.

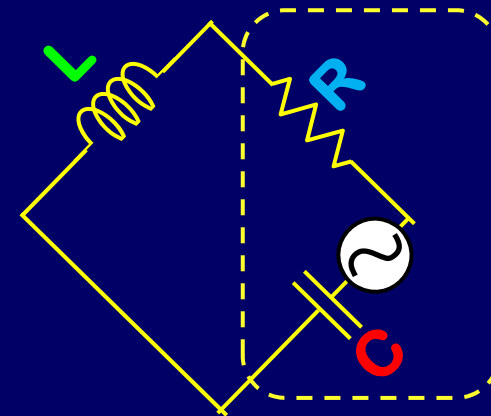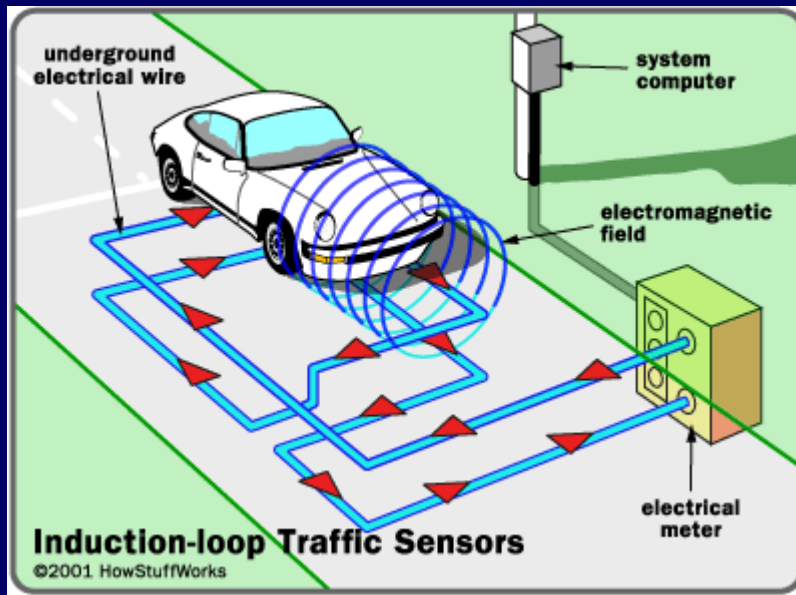Another use for RLC circuits: traffic sensors



AC Summary

Resistors: $V_{R,\max} = I_{\max} R$

In phase with I

Capacitors: $V_{C,\max} = I_{\max} X_C$ $X_C = 1/(2\pi f C)$

Lags I

Inductors: $V_{L,\max} = I_{\max} X_L$ $X_L = 2\pi f L$

Leads I

Generator: $V_{\text{gen},\max} = I_{\max} Z$ $Z = \sqrt{R^2 + (X_L - X_C)^2}$

Can lead or lag I $\tan(\phi) = (X_L - X_C)/R$

Power is only dissipated in resistor:

$$\bar{P} = \frac{1}{2} I_{\max} V_{\text{gen},\max} \cos(\phi)$$