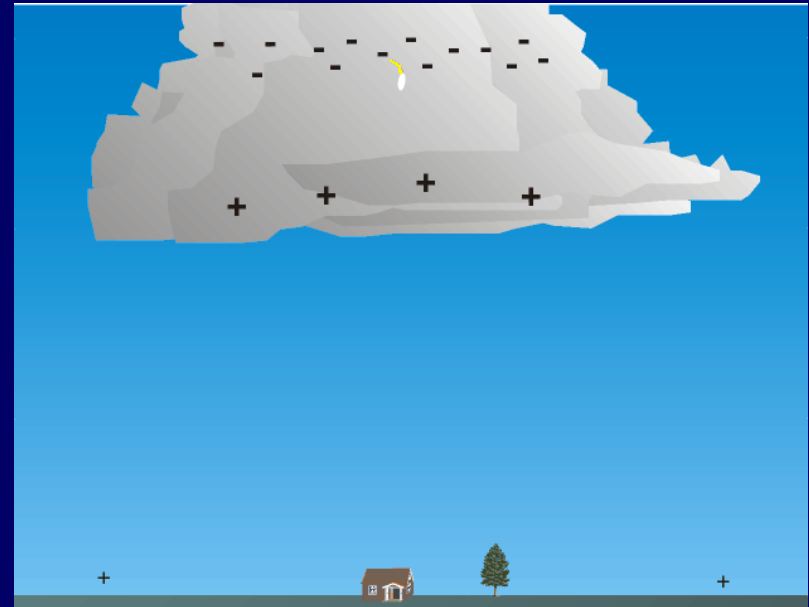


Physics 102: Lecture 04

Capacitors (& batteries)





Physics 102 so far

Basic principles of electricity

- Lecture 1 – electric charge & electric force
- Lecture 2 – electric field
- Lecture 3 – electric potential energy and electric potential

Applications of electricity – circuits

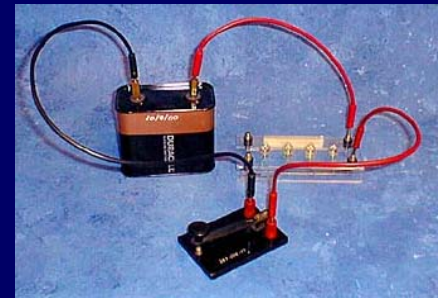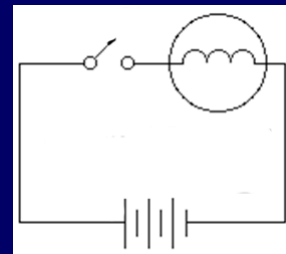- Lecture 4 – capacitance
- Lecture 5 – resistance
- Lecture 6 – Kirchhoff's rules
- Lecture 7 – RC circuits
- Lecture 12 & 13 – AC circuits



Recall from last lecture.....
Electric Fields, Electric Potential

Comparison:

Electric *Potential Energy* vs. Electric *Potential*



ΔV_{AB} : the difference in electric potential between points B and A

ΔU_{AB} : the change in electric potential energy of a charge q when moved from A to B


$$\Delta U_{AB} = q \Delta V_{AB}$$

Electric Potential: Summary

- E field lines point from **higher** to **lower** potential
- For positive charges, going from **higher** to **lower** potential is “downhill”

Positive charges tend to go “downhill”, from + to –

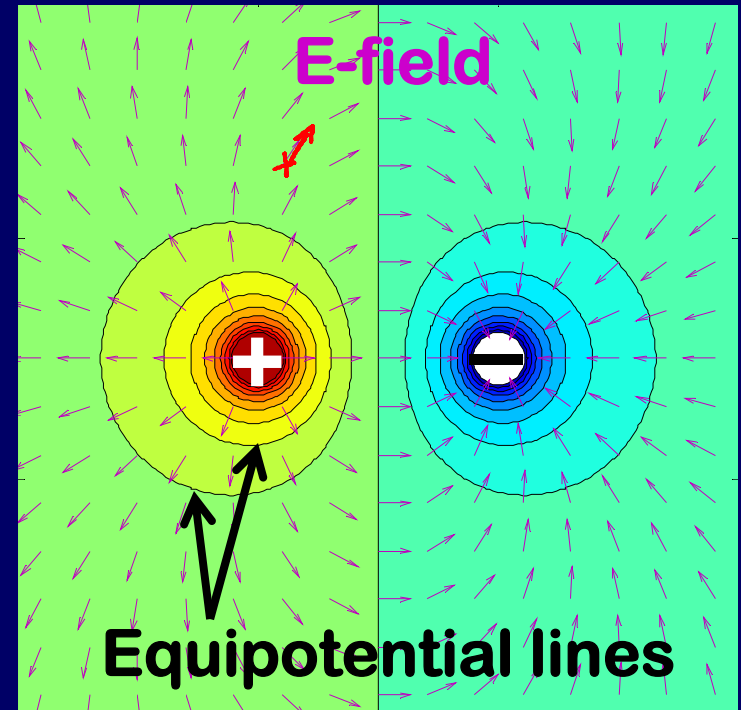Negative charges go in the opposite direction, from – to +



$$\Delta U_{AB} = q \Delta V_{AB}$$

Uniform Electric Field: Important Special Case

Two large parallel conducting plates of area A


+ Q on one plate

− Q on other plate


Then E is

- **uniform** between the two plates:
 $E = 4\pi kQ/A$
- **zero** everywhere else
- This result is **independent of plate separation**

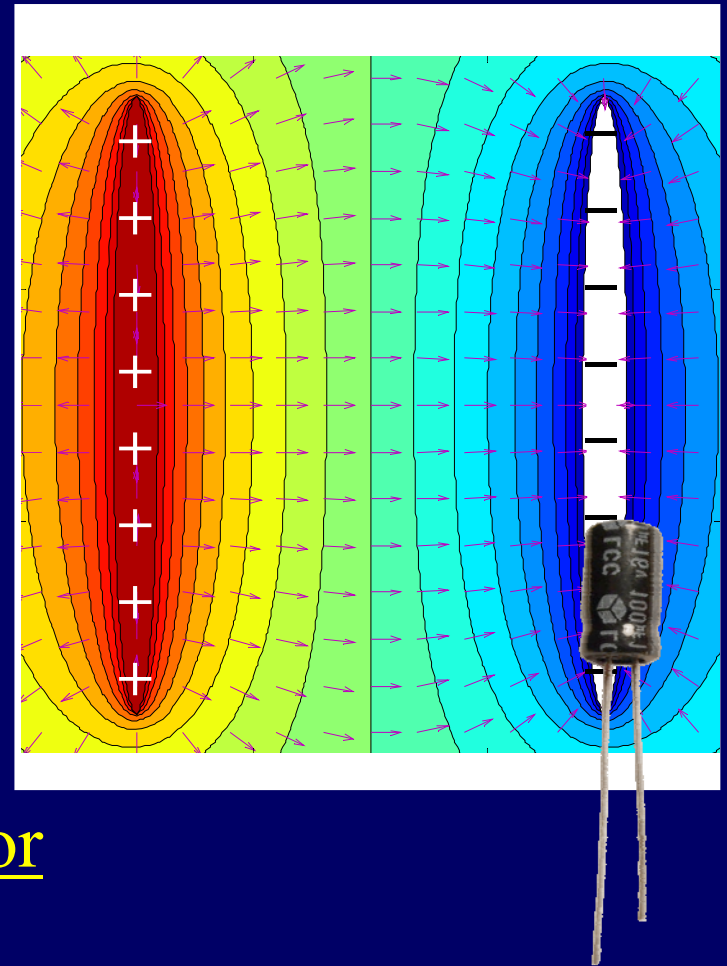This is called a parallel plate capacitor



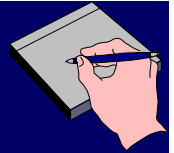Parallel Plate Capacitor: Potential Difference




Charge Q on plates


Leet. 3

$$V = V_A - V_B = +E d \quad (\text{like } W_{\text{ext}} = qEd = \Delta U; \Delta V = \Delta U/q)$$
$$= 4 \pi k Q d / A$$

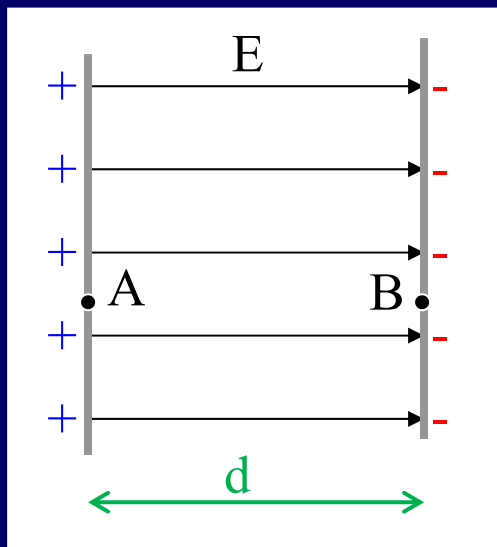Voltage is proportional
to the charge! $V \propto Q$



PhET Simulation

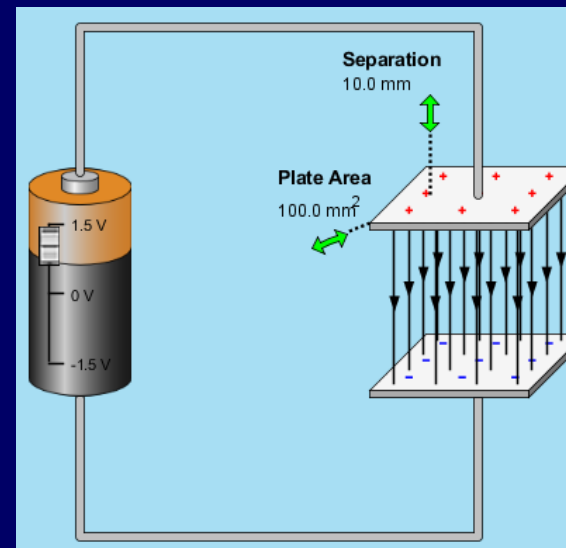

Capacitance: The ability to store separated charge $C \equiv Q/V$



- Any pair conductors separated by a small distance. (e.g. two metal plates)
- Capacitor stores separated charge $Q = CV$
 - Positive Q on one conductor, negative Q on other
 - Net charge is zero

- Stores Energy $U_c = \left(\frac{1}{2}\right) Q V$

$$U_c = \frac{1}{2} C V^2 = \frac{1}{2} Q^2 / C$$

Units:


1 Coulomb/Volt
= 1 Farad (F)

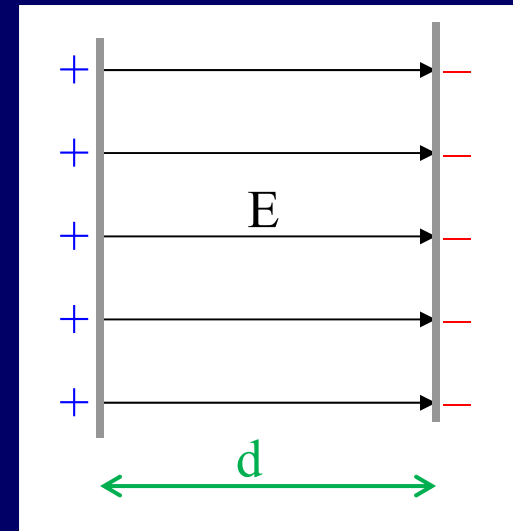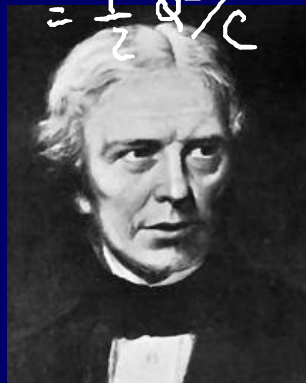


Why Separate Charge?

A way to store and release energy!

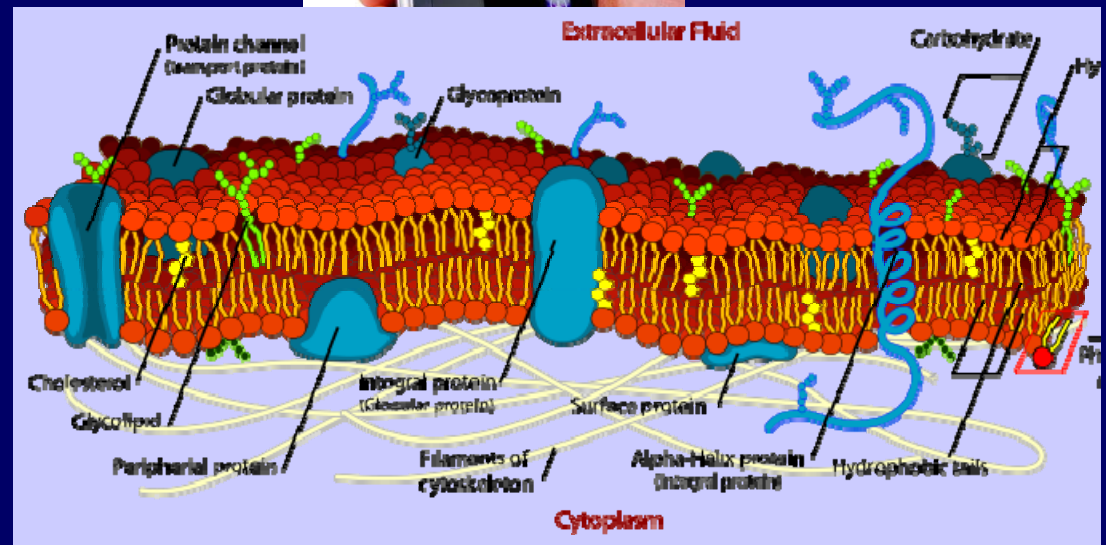- Camera Flash
- Defibrillator
- AC \rightarrow DC
- Tuners / resonant circuits
 - Radio
 - Cell phones
- Electronics
 - Touch screen
- Cell membranes



Capacitance of Parallel Plate Capacitor

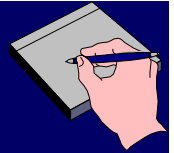

$$V = Ed \quad E = 4\pi kQ/A$$

(Between two large plates)

$$\text{So: } V = 4\pi kQd/A$$

$$\text{Recall: } C \equiv Q/V$$



$$\text{So: } C = A/(4\pi kd)$$

Recall:

$$\epsilon_0 = 1/(4\pi k) = 8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2$$

$$C = \epsilon_0 A/d$$

Parallel plate capacitor

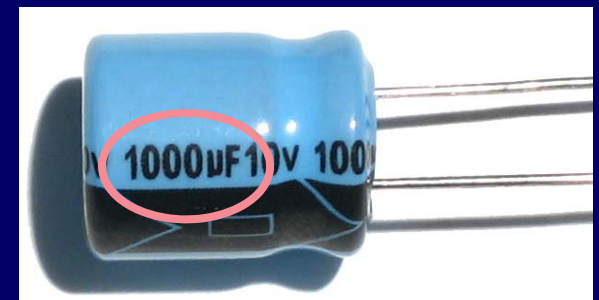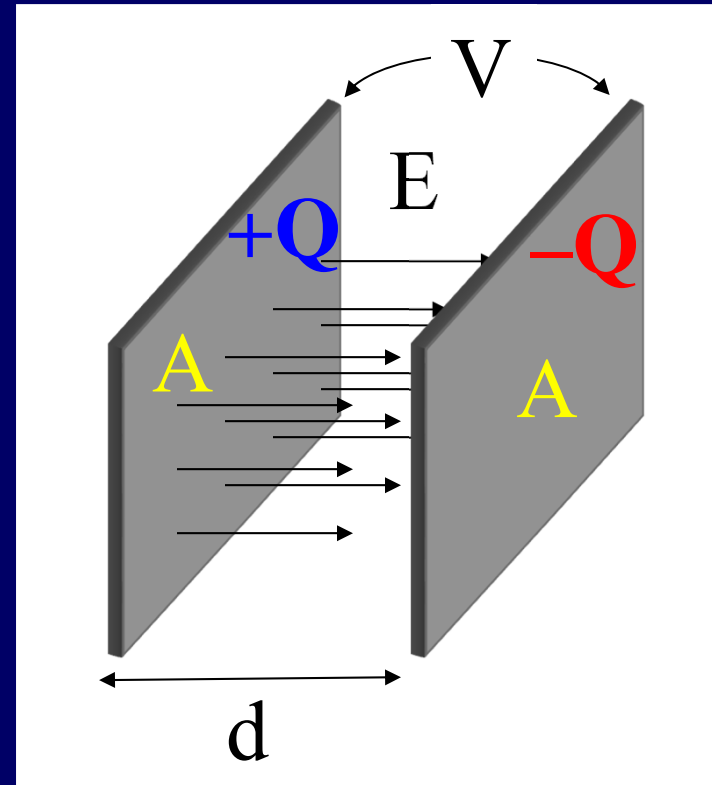

Dielectric

- Placing a dielectric (insulator) between the plates **increases the capacitance**.



Dielectric
constant ($\kappa > 1$)

$$C = \kappa C_0$$

Capacitance
without dielectric


Capacitance **with**
dielectric

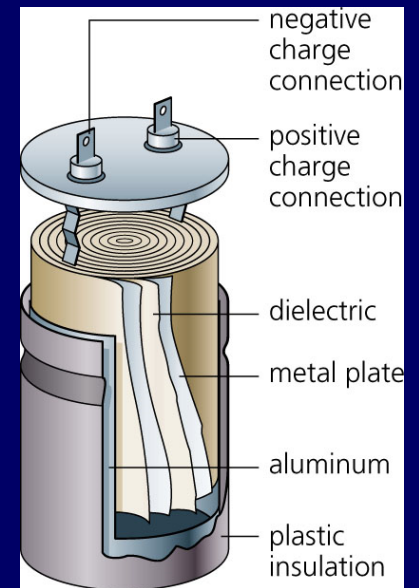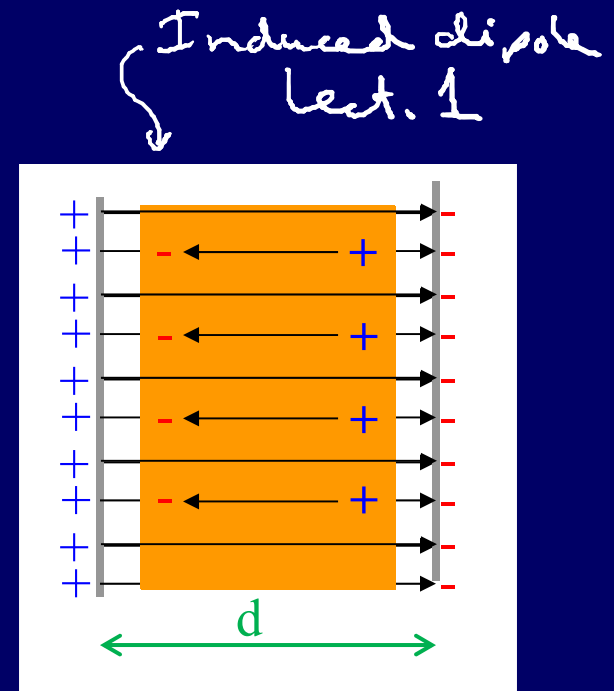For same charge Q , E (and V)
is reduced so $C = Q/V$ increases





ACT: Parallel Plates

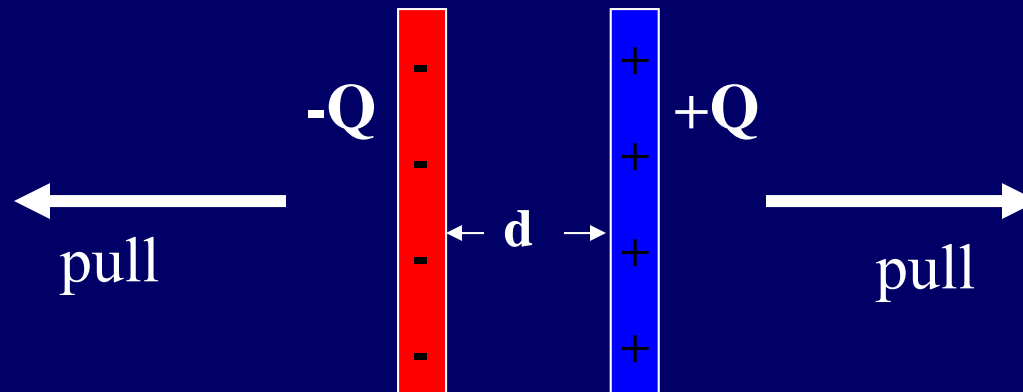

A parallel plate capacitor given a charge Q . The plates are then pulled a **small** distance further apart. What happens to the charge Q on each plate of the capacitor?


A) Increases

B) Constant

C) Decreases

Remember charge is real/physical. There is no place for the charges to go.

CheckPoint 4.1

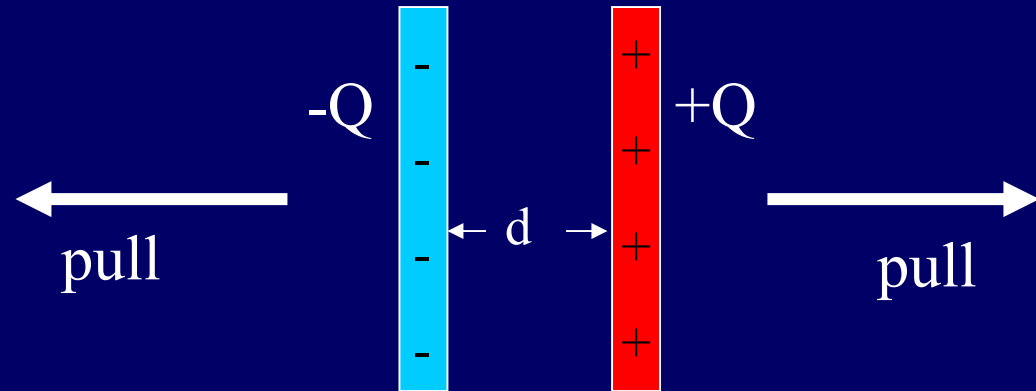

A parallel plate capacitor given a charge Q . The plates are then pulled a **small** distance further apart. Which of the following apply to the situation after the plates have been moved?

1) The capacitance increases

87%

True

False

$$C = \epsilon_0 A / d \quad C \text{ decreases!}$$

2) The electric field increases

92%

True

False

$$E = Q / (\epsilon_0 A) \quad \text{Constant}$$

3) The voltage between the plates increases

19%


True

False

$$V = Ed$$



ACT/CheckPoint 4.1

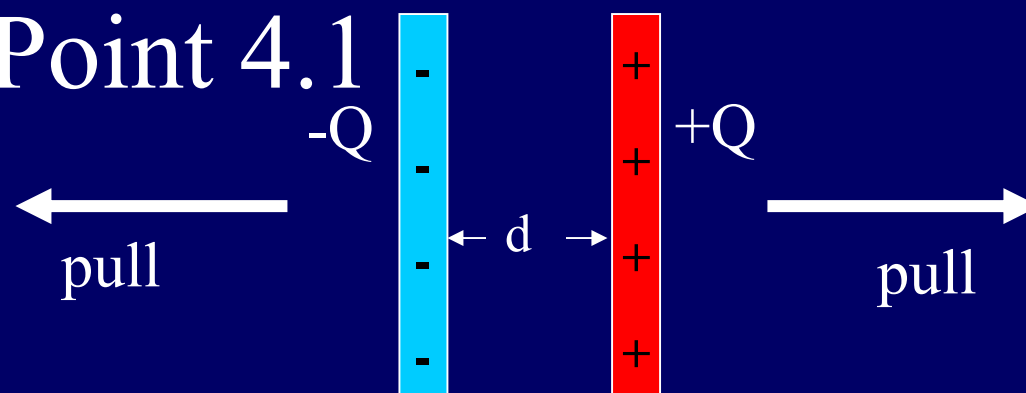

A parallel plate capacitor given a charge Q . The plates are then pulled a **small** distance further apart. Which of the following apply to the situation after the plates have been moved?

The energy stored in the capacitor

A) increases

B) constant

C) decreases

$$U = \frac{1}{2} QV \quad Q \text{ constant, } V \text{ increased}$$



Plates are attracted to each other, you must pull them apart, so the potential energy of the plates increases.

$$W_{\text{you}} = \Delta U$$


Capacitors are used in circuits!



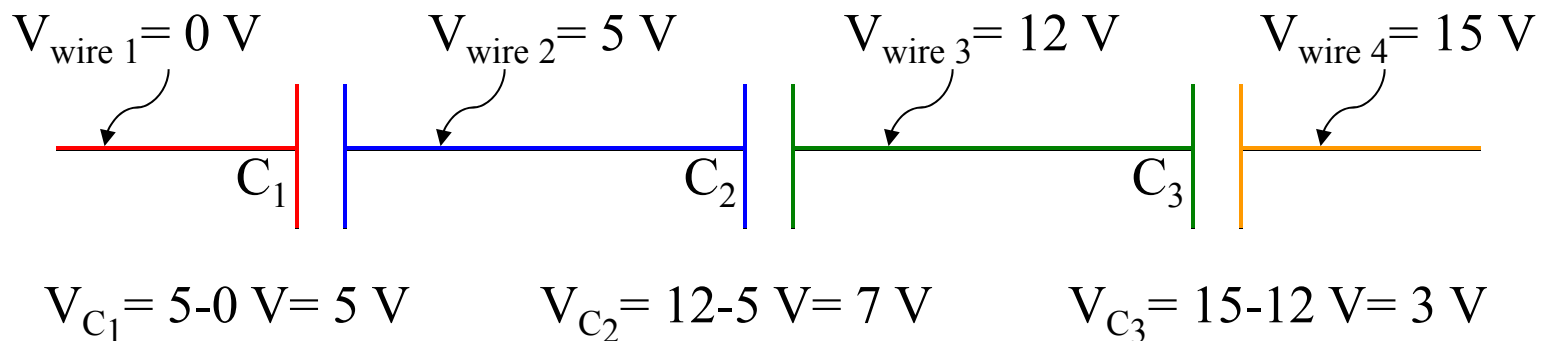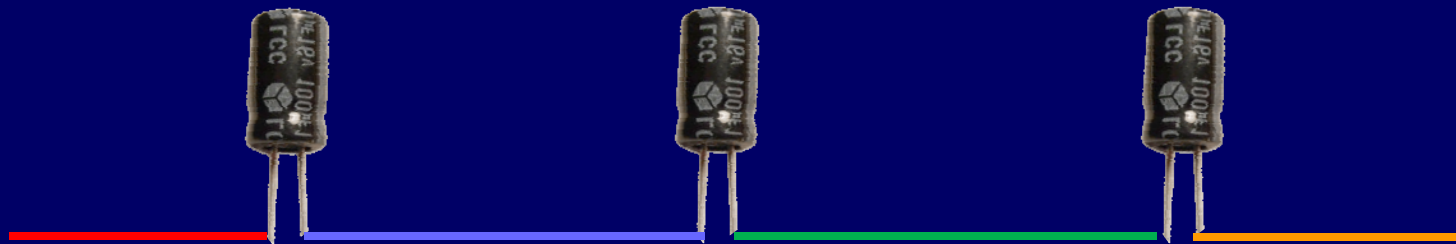
- In circuits, elements are connected by wires.
- Any connected region of wire has the same potential. $E=0$, $V = \text{const.}$
- The potential difference across an element is the *element's* “voltage.”



To understand complex circuits...

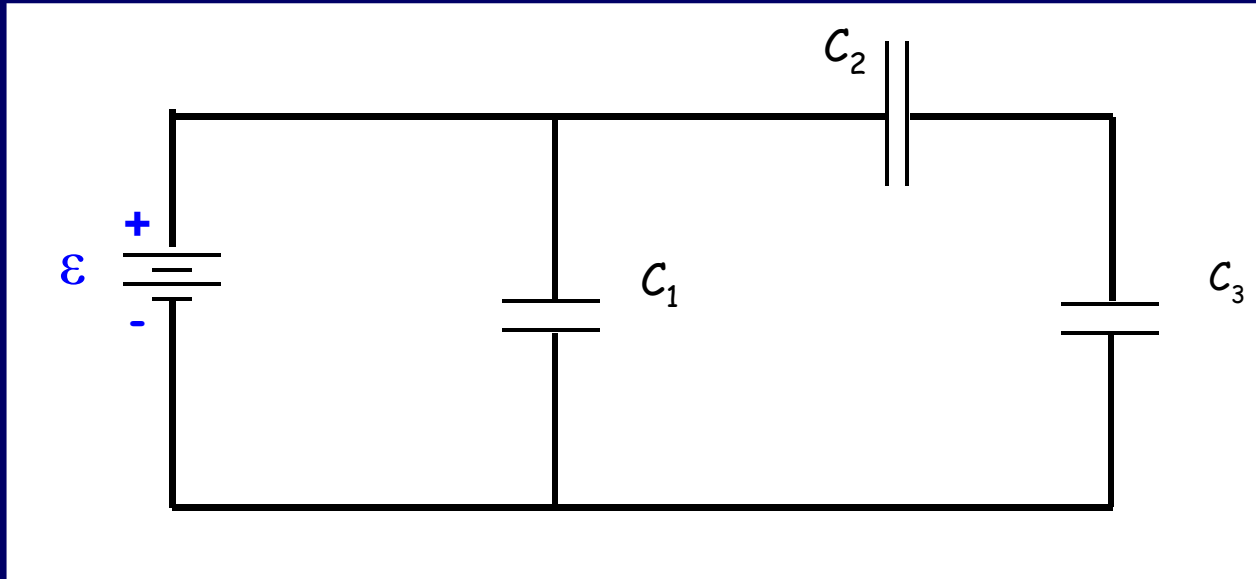


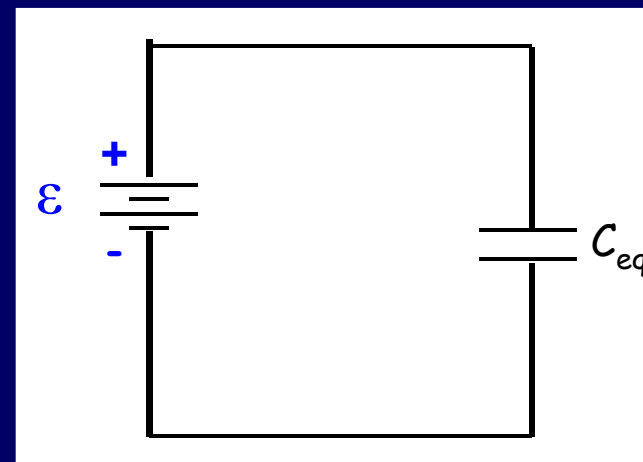...treat capacitors in series and parallel as a fictitious equivalent capacitor!




Capacitors in Parallel

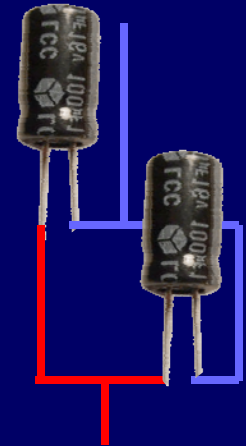
- Both ends connected together by wire
- Same voltage: $V_1 = V_2 = V_{eq}$
- Share Charge: $Q_{eq} = Q_1 + Q_2$
- Equivalent C: $C_{eq} = C_1 + C_2$



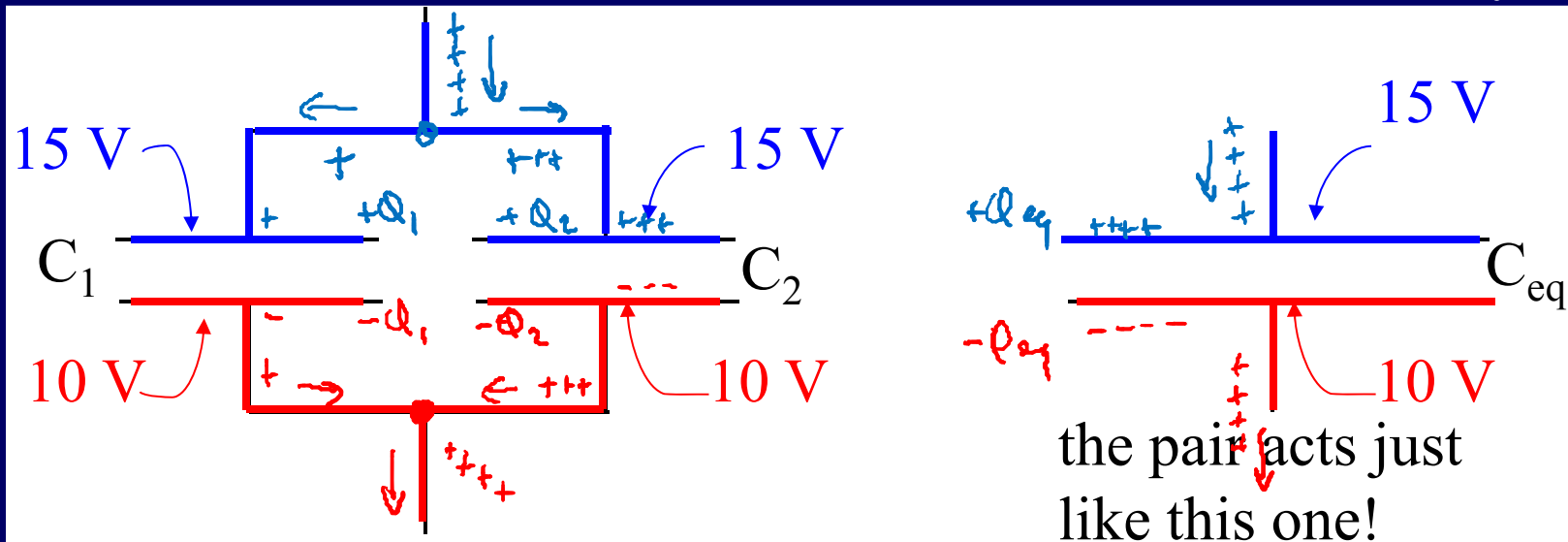Add areas – remember $C = \epsilon_0 A/d$



Example

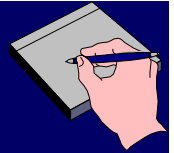

Parallel Practice


A $4\ \mu\text{F}$ capacitor and $6\ \mu\text{F}$ capacitor are connected in parallel and charged to 5 volts. Calculate C_{eq} , and the charge on each capacitor.

$$C_{\text{eq}} = C_4 + C_6 = 4\ \mu\text{F} + 6\ \mu\text{F} = 10\ \mu\text{F}$$

$$Q_4 = C_4 V_4 = (4\ \mu\text{F})(5\ \text{V}) = 20\ \mu\text{C}$$

$$Q_6 = C_6 V_6 = (6\ \mu\text{F})(5\ \text{V}) = 30\ \mu\text{C}$$
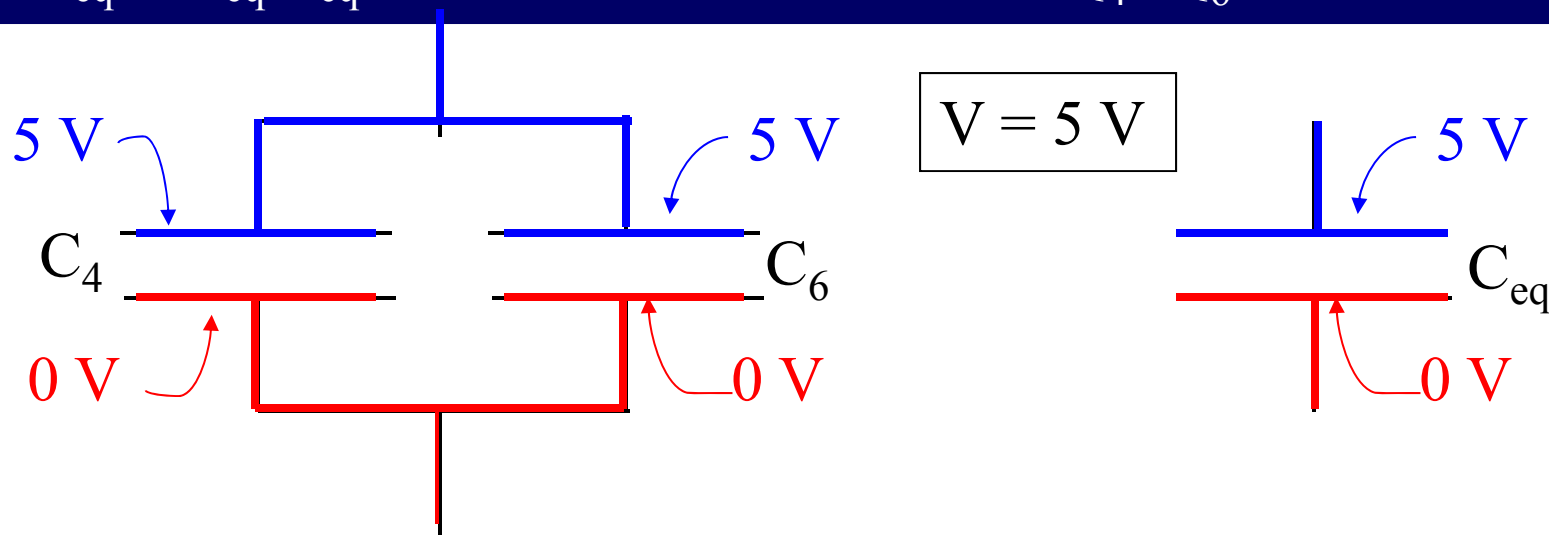
$$Q_{\text{eq}} = C_{\text{eq}} V_{\text{eq}} = (10\ \mu\text{F})(5\ \text{V}) = 50\ \mu\text{C} = Q_4 + Q_6$$






Capacitors in Series

- Connected end-to-end with NO other exits

- Same Charge: $Q_1 = Q_2 = Q_{eq}$


- Share Voltage: $V_1 + V_2 = V_{eq}$

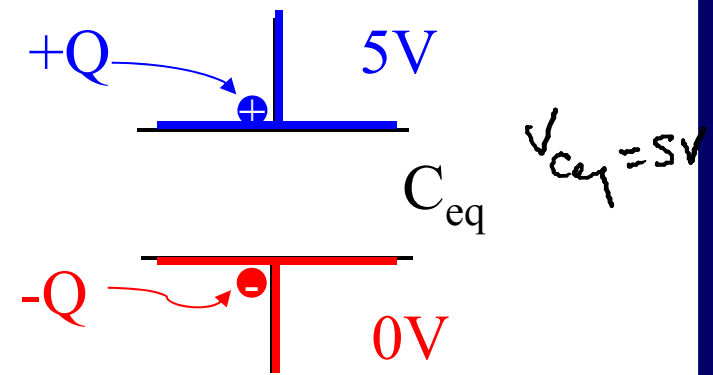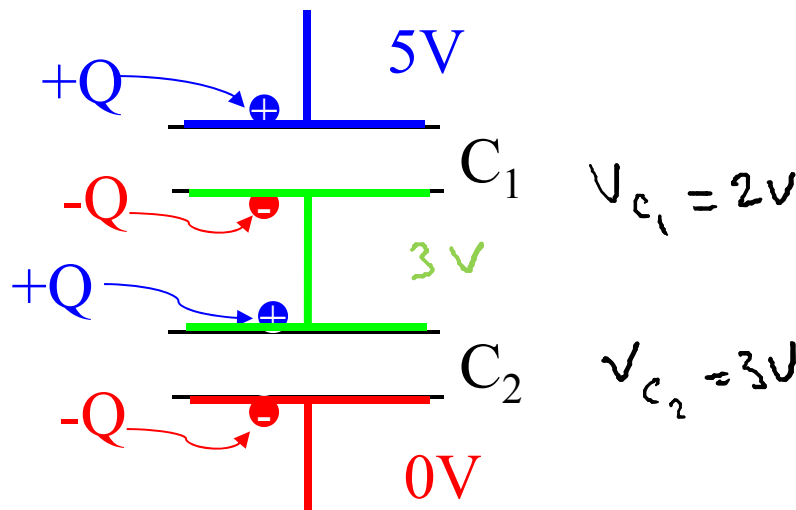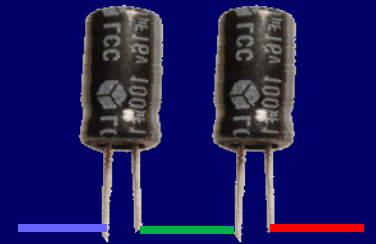- Equivalent C: $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$ Add d – remember $C = \epsilon_0 A/d$



Example

Series Practice

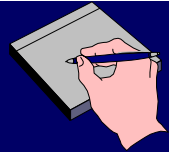


A $4\ \mu\text{F}$ capacitor and $6\ \mu\text{F}$ capacitor are connected in series and charged to 5 volts. Calculate C_{eq} , and the charge on the $4\ \mu\text{F}$ capacitor.

$$C_{eq} = \left(\frac{1}{C_4} + \frac{1}{C_6} \right)^{-1} = \left(\frac{1}{4\ \mu\text{F}} + \frac{1}{6\ \mu\text{F}} \right)^{-1} = 2.4\ \mu\text{F}$$

$$Q = CV$$
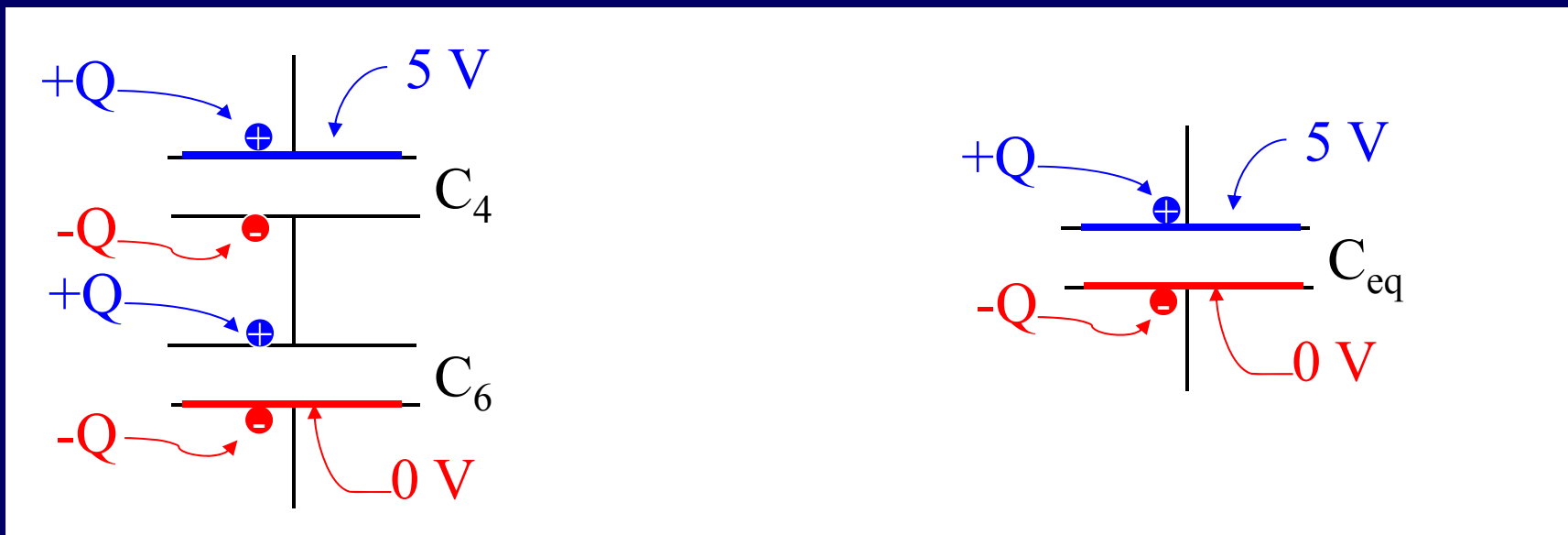
$$Q_4 = Q_6 = Q_{eq} = C_{eq}V = (2.4\ \mu\text{F})(5\text{V}) = 12\ \mu\text{C}$$




Comparison:

Series vs. Parallel


Series

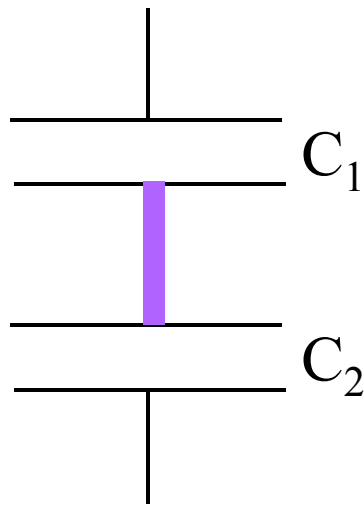- Can follow a wire from one element to the other with no branches in between.



Parallel

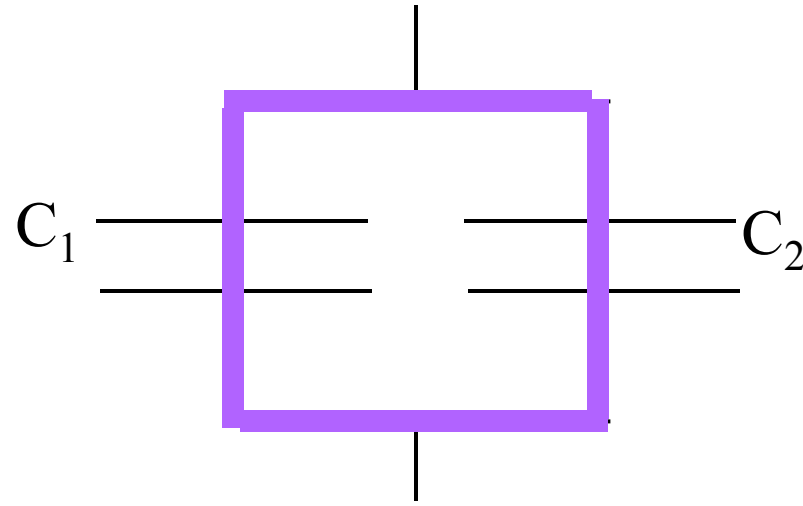- Can find a loop of wire containing both elements but no others (may have branches).




Electromotive Force

- **Battery**

- Maintains constant potential **difference** V (electromotive force – emf ε)
- Does NOT produce or supply charges, just “pushes” them.

Like a pump for charge!

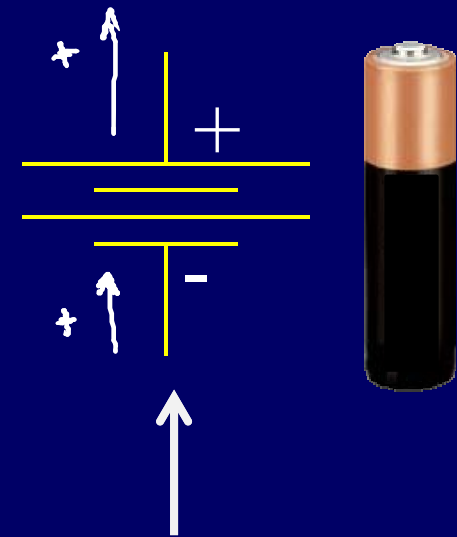


Usually “0V”
by convention

CheckPoint 4.4

A circuit consists of three initially uncharged capacitors C_1 , C_2 , and C_3 , which are then connected to a battery of emf ε . The capacitors obtain charges q_1 , q_2 , q_3 , and have voltages across their plates V_1 , V_2 , and V_3 . C_{eq} is the equivalent capacitance of the circuit. Which of these are true?

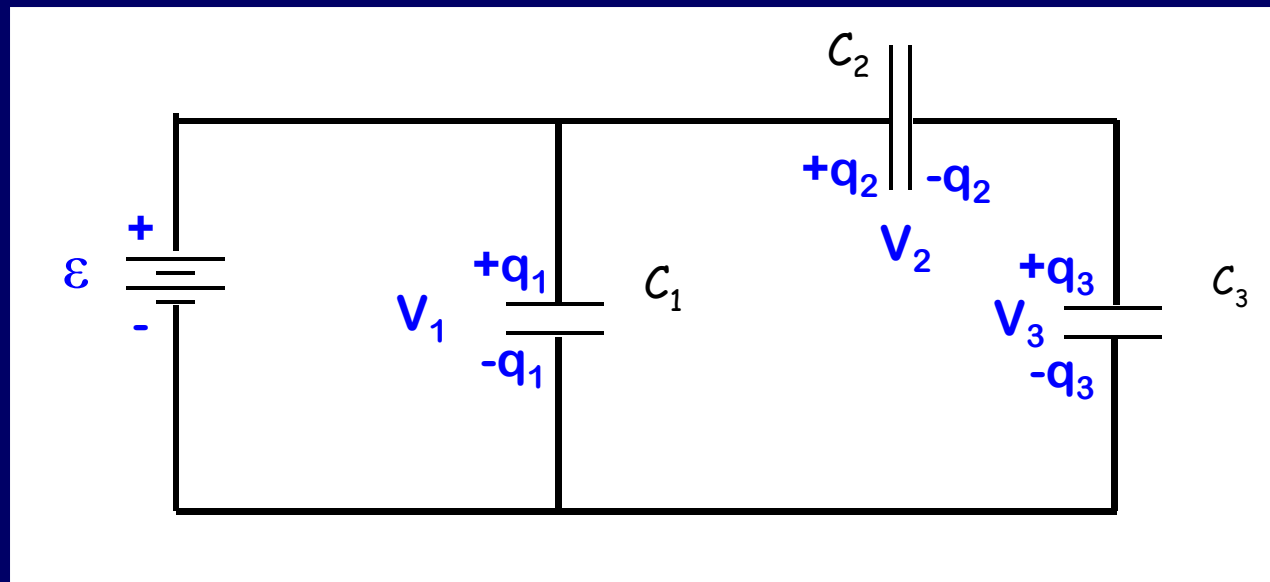
- 1) $q_1 = q_2$
- 2) $q_2 = q_3$
- 3) $V_2 = V_3$
- 4) $\varepsilon = V_1$
- 5) $V_1 < V_2$





ACT/CheckPoint 4.4: Which is true?

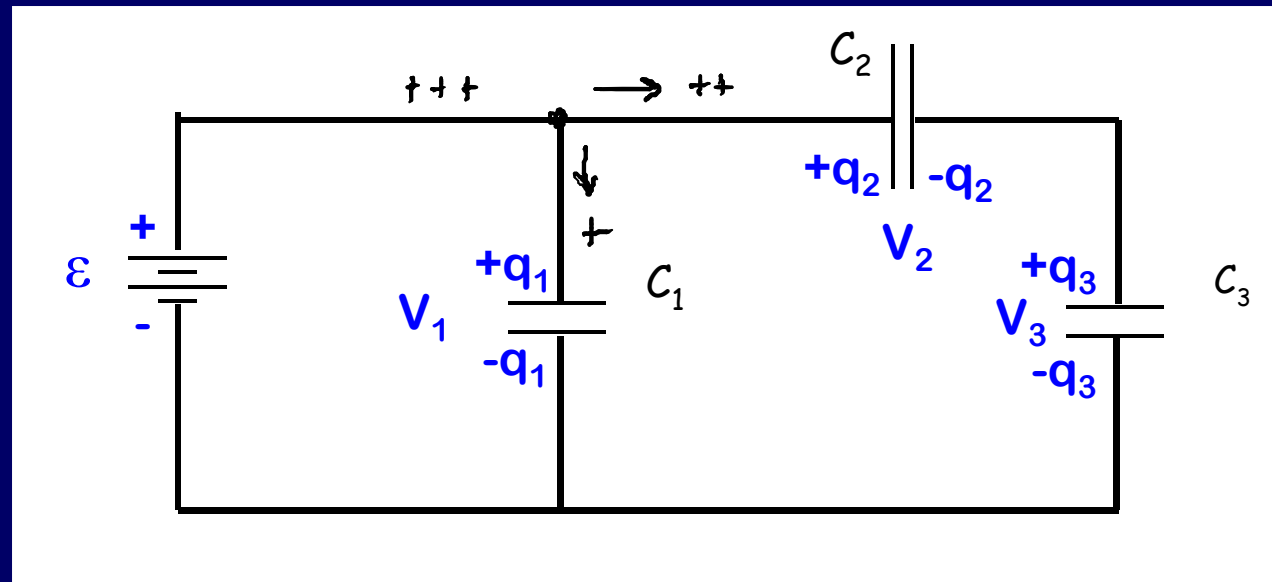A circuit consists of three initially uncharged capacitors C_1 , C_2 , and C_3 , which are then connected to a battery of emf ε . The capacitors obtain charges q_1 , q_2 , q_3 , and have voltages across their plates V_1 , V_2 , and V_3 . C_{eq} is the equivalent capacitance of the circuit.




1) $q_1 = q_2$ Not necessarily. C_1 and C_2 are NOT in series.

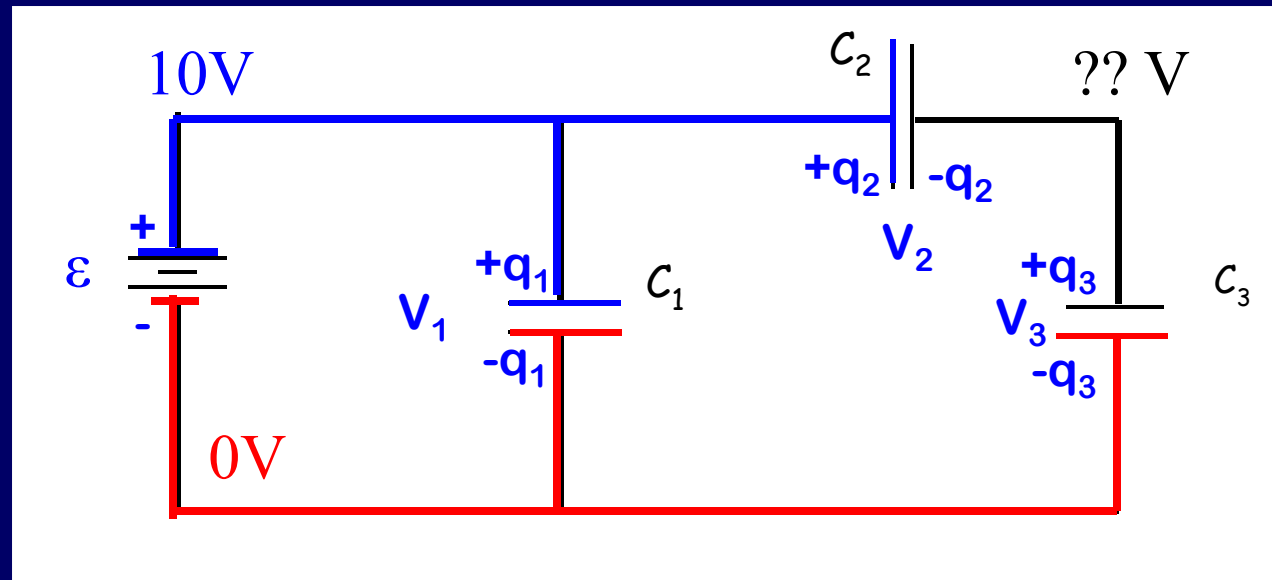2) $q_2 = q_3$ Yes! C_2 and C_3 are in series.



ACT/CheckPoint 4.4: Which is true?

A circuit consists of three initially uncharged capacitors C_1 , C_2 , and C_3 , which are then connected to a battery of emf ε . The capacitors obtain charges q_1 , q_2 , q_3 , and have voltages across their plates V_1 , V_2 , and V_3 . C_{eq} is the equivalent capacitance of the circuit.



1) $V_2 = V_3$ Not necessarily, only if $C_2 = C_3$

2) $\varepsilon = V_1$ Yes! Both ends are connected by wires

Recap of Today's Lecture

- Capacitance $C = Q/V$
- Parallel Plate: $C = \epsilon_0 A/d$
- Capacitors in parallel: $C_{eq} = C_1 + C_2$
- Capacitors in series: $1/C_{eq} = 1/C_1 + 1/C_2$
- Batteries provide fixed potential difference