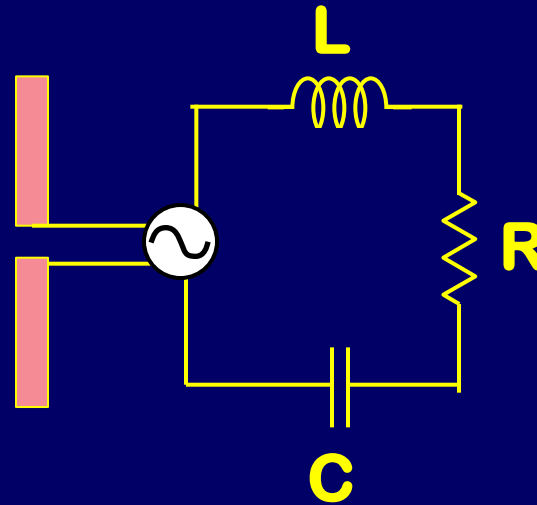


Physics 102: Lecture 13


RLC circuits & Resonance



Ch 21 Prob. 41, 43, 49, 53, 55, 59

Review: AC Circuit

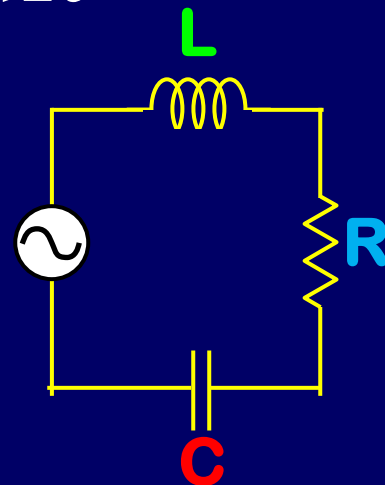- $I = I_{\max} \sin(2\pi ft)$
- $V_R = I_{\max} R \sin(2\pi ft)$
 V_R in phase with I
- $V_C = I_{\max} X_C \sin(2\pi ft - \pi/2)$




V_C lags I “ICE”

$$V_{C,\max} = I_{\max} X_C \quad X_C = 1/\omega C$$

- $V_L = I_{\max} X_L \sin(2\pi ft + \pi/2)$

V_L leads I “ELI”
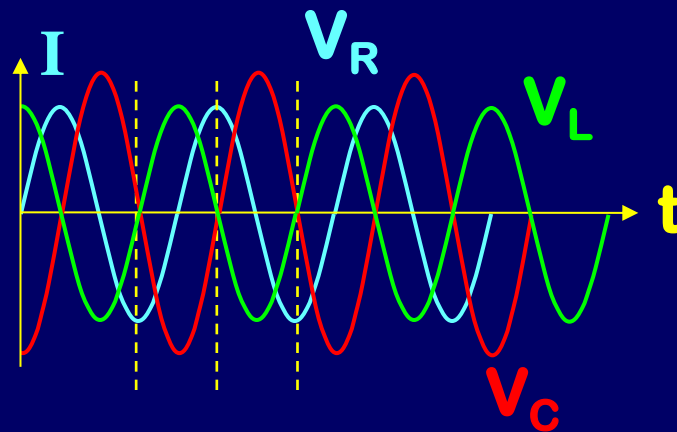
$$V_{L,\max} = I_{\max} X_L \quad X_L = \omega L$$



Goal:

write down equations for all of the voltages



$$V_R = I_{\max} R \sin(2\pi ft)$$



$$V_L = I_{\max} X_L \sin(2\pi ft + \pi/2)$$


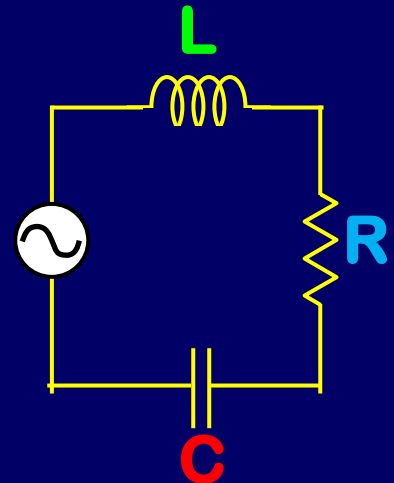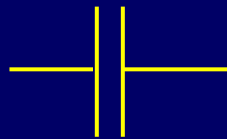
$$V_C = I_{\max} X_C \sin(2\pi ft - \pi/2)$$



The only element left: generator!




$$V_{gen} = V_{gen,max} \sin(2\pi ft + \phi)$$

ϕ : “phase angle”

Like a shift in time!

$\phi < 0$: shift forward


$\phi > 0$: shift backward

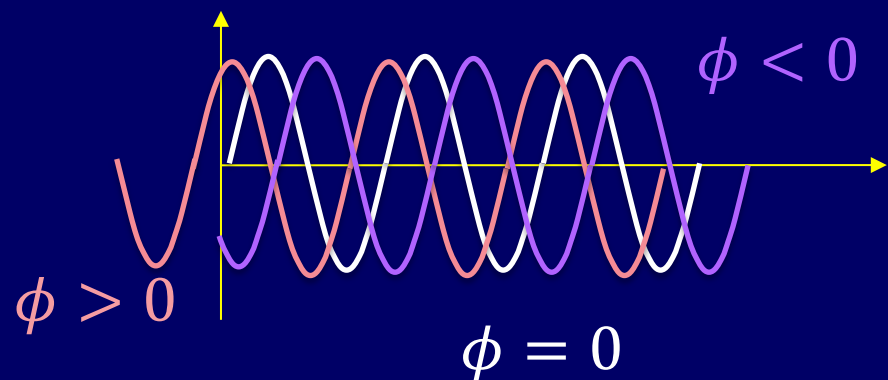

Kirchhoff: generator voltage




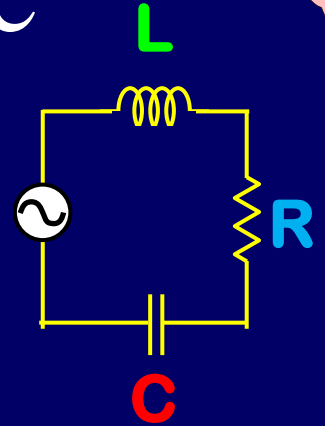- Instantaneous voltage across generator (V_{gen}) must equal sum of voltage across all of the elements at all times:



$$V_{\text{gen}}(t) = V_R(t) + V_C(t) + V_L(t)$$
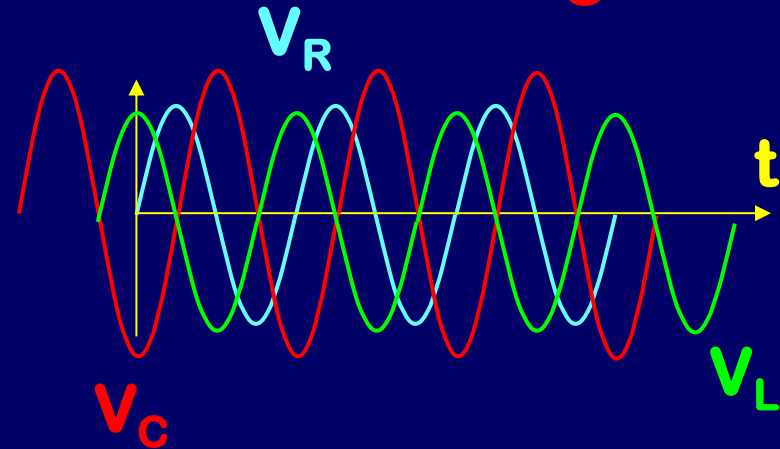
$$V_{\text{gen,max}} \neq V_{L,\text{max}} + V_{R,\text{max}} + V_{C,\text{max}}$$



What is $V_{\text{gen,max}}$?

Define impedance Z : $V_{\text{gen,max}} \equiv I_{\text{max}} Z$

Like: $V=IR$


$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

One last ingredient: is the generator voltage leading or lagging the current?

$$I = I_{max} \sin(2\pi ft)$$


$$V_{gen} = I_{max} Z \sin(2\pi ft + \phi)$$

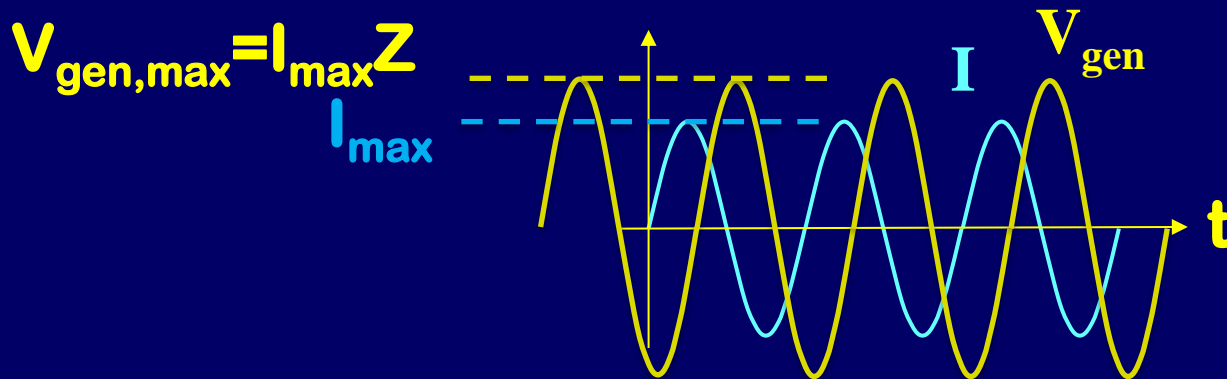Phase angle: $\tan(\phi) = \frac{(X_L - X_C)}{R}$



This example:
 $\phi < 0$, **voltage**
is lagging

Example

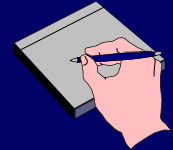

Problem Time!

An AC circuit with $R = 2 \Omega$, $C = 15 \text{ mF}$, and $L = 30 \text{ mH}$ is driven by a generator with voltage $V(t) = 2.5 \sin(8\pi t)$ Volts. Calculate the maximum current in the circuit, and the phase angle.


$$I_{\max} = V_{\text{gen,max}} / Z$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{2^2 + \left(8\pi \times .030 - \frac{1}{8\pi \times .015}\right)^2} = 2.76 \Omega$$

$$I_{\max} = 2.5 / 2.76 = 0.91 \text{ Amps}$$
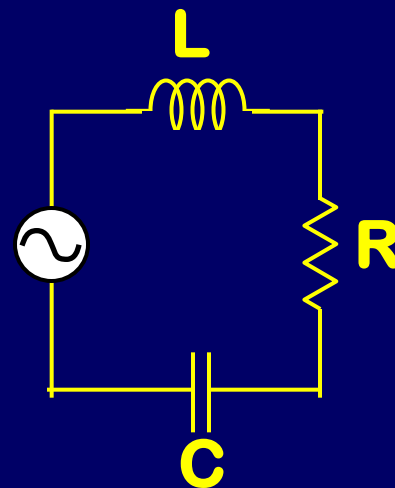
$$\tan(\phi) = \frac{X_L - X_C}{R} = \frac{(8\pi \times .030 - \frac{1}{8\pi \times .015})}{2} \Rightarrow \phi = -43.5^\circ$$



Power in RLC circuits

- The voltage generator supplies power.
 - Only resistor dissipates power.
 - Capacitor and Inductor store and release energy.
- $P(t) = I(t)V_R(t)$ oscillates so sometimes power loss is large, sometimes small.
- Average power dissipated by resistor:

$$\begin{aligned}\overline{P} &= \frac{1}{2} I_{\max} V_{R,\max} \\ &= \frac{1}{2} I_{\max} V_{\text{gen},\max} \cos(\phi) \\ &= I_{\text{rms}} V_{\text{gen},\text{rms}} \cos(\phi)\end{aligned}$$

If there is only a resistor, $\phi = 0$



ACT: Power dissipation




Which one of these circuits dissipates the most average power?

The resistance $R=2\Omega$ for circuits A and C, $R=0$ for B

$$V_{\text{gen,max}} = 10 \text{ V}$$

$$V_{\text{gen,max}} = 100 \text{ V}$$

$$\varepsilon = 1 \text{ V}$$

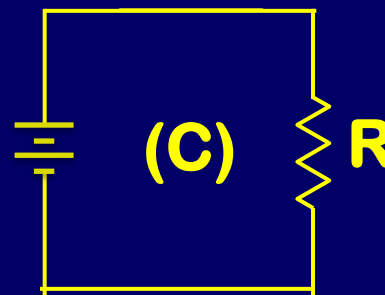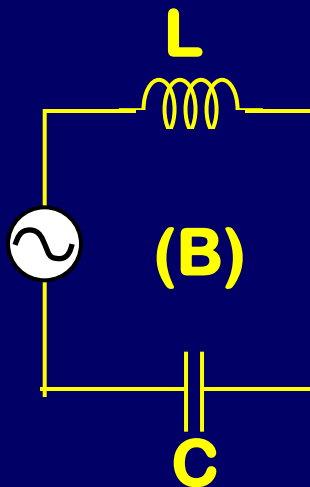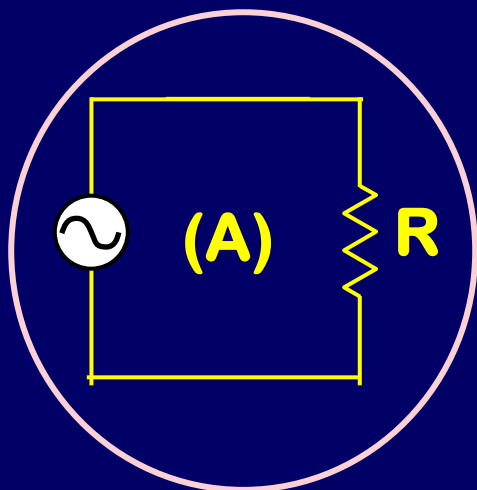

$$P_{\text{avg}} = \frac{1}{2} I_{\text{max}} V_{\text{gen,max}}$$

$$= \frac{1}{2} V_{\text{gen,max}}^2 / R$$

$$= 25 \text{ W}$$


$$P_{\text{avg}} = 0$$

$$\text{Resistor} = 0$$

$$P = \varepsilon^2 / R$$

$$= 0.5 \text{ W}$$

Kirchhoff: generator voltage

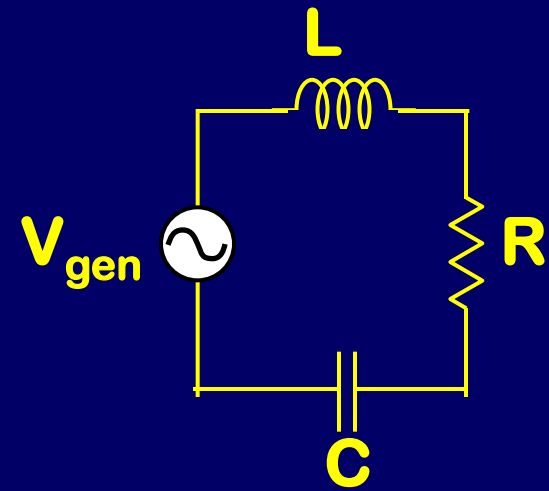


Write down Kirchhoff's Loop Equation:

$$V_{\text{gen}}(t) = V_L(t) + V_R(t) + V_C(t) \text{ at every instant of time}$$


If the frequency is just right...

$$V_{\text{gen}}(t) = V_R(t)$$

Resonance!

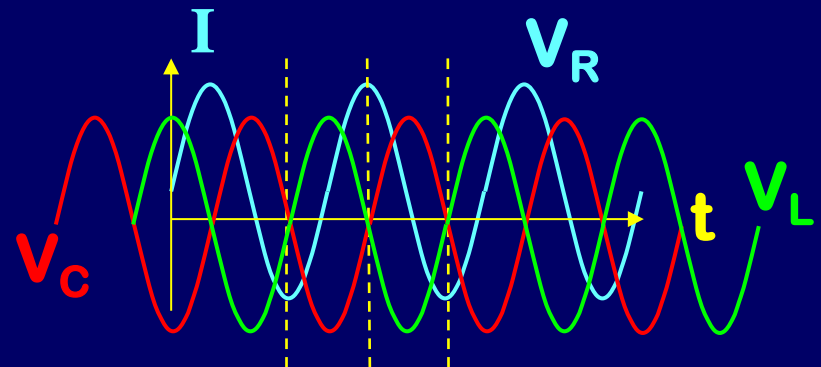


Examples of mechanical resonance

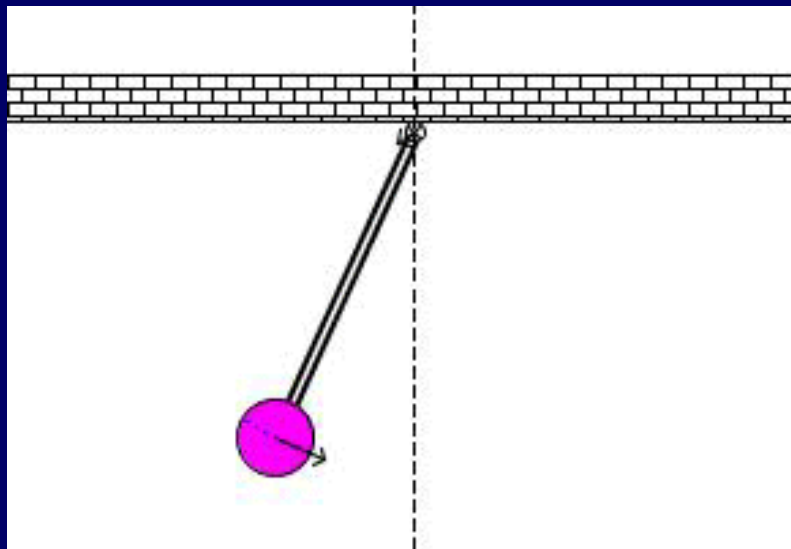

Pendulum:

$$\omega_0 = \sqrt{g/l}$$

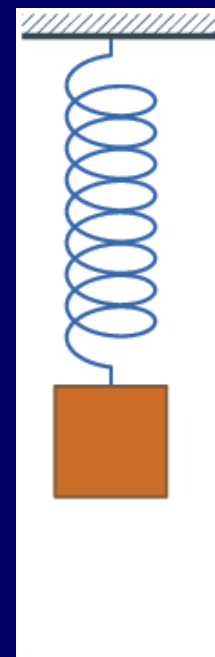

Mass on a spring:

$$\omega_0 = \sqrt{k/m}$$

Common features:

- **Energy converts between two forms (kinetic & potential)**
- **Weak input at ω_0 leads to a big response!**

Resonance!





Tacoma Narrows Bridge





Millennium Bridge




Electric energy

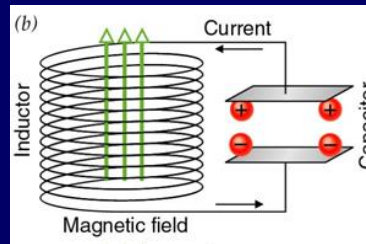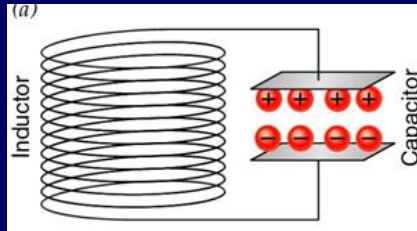


Magnetic energy

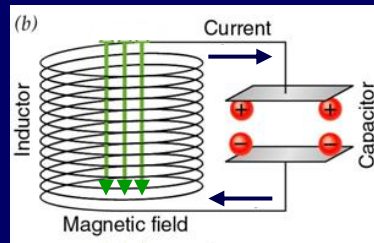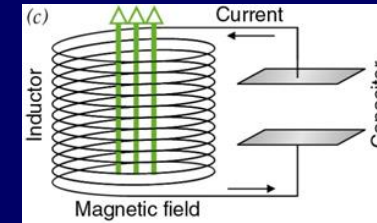


**RLC circuit:
Electrical
resonance**

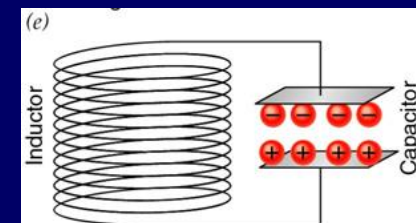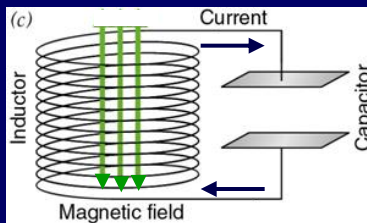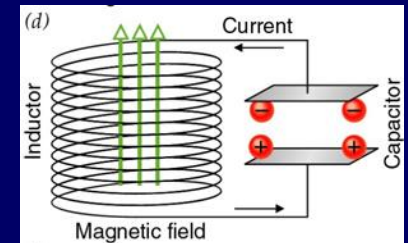

Magnetic energy

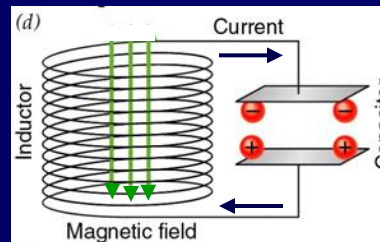

Electric energy

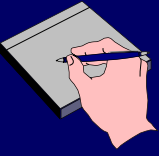

Resonance

R is independent of **f**

X_L increases with **f**

$$X_L = 2\pi fL$$

X_C decreases with **f**


$$X_C = 1/(2\pi fC)$$


Z: **X_L** and **X_C** subtract

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Resonance: **$X_L = X_C$**

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

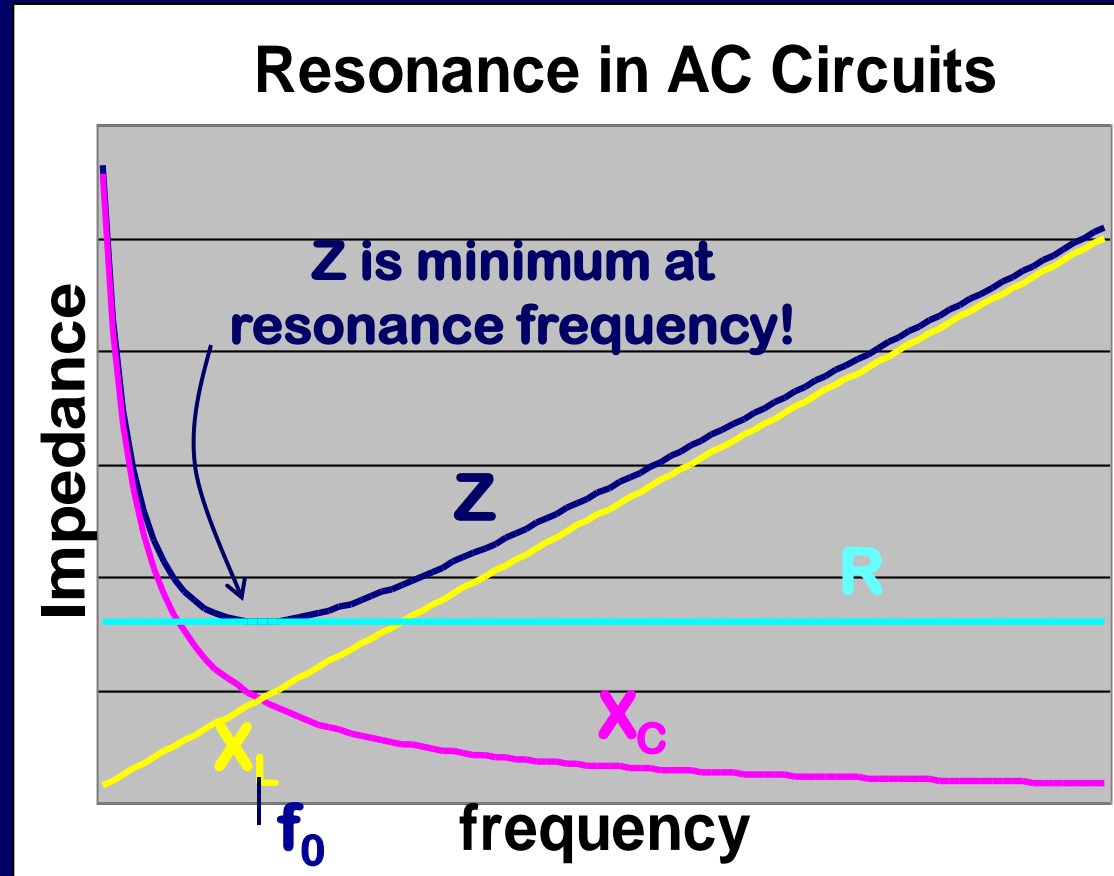

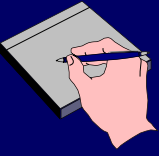

Resonance

R is independent of **f**

X_L increases with **f**

$$X_L = 2\pi fL$$


X_C decreases with **f**

$$X_C = 1/(2\pi fC)$$

Z: **X_L** and **X_C** subtract

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$


Resonance: X_L = X_C

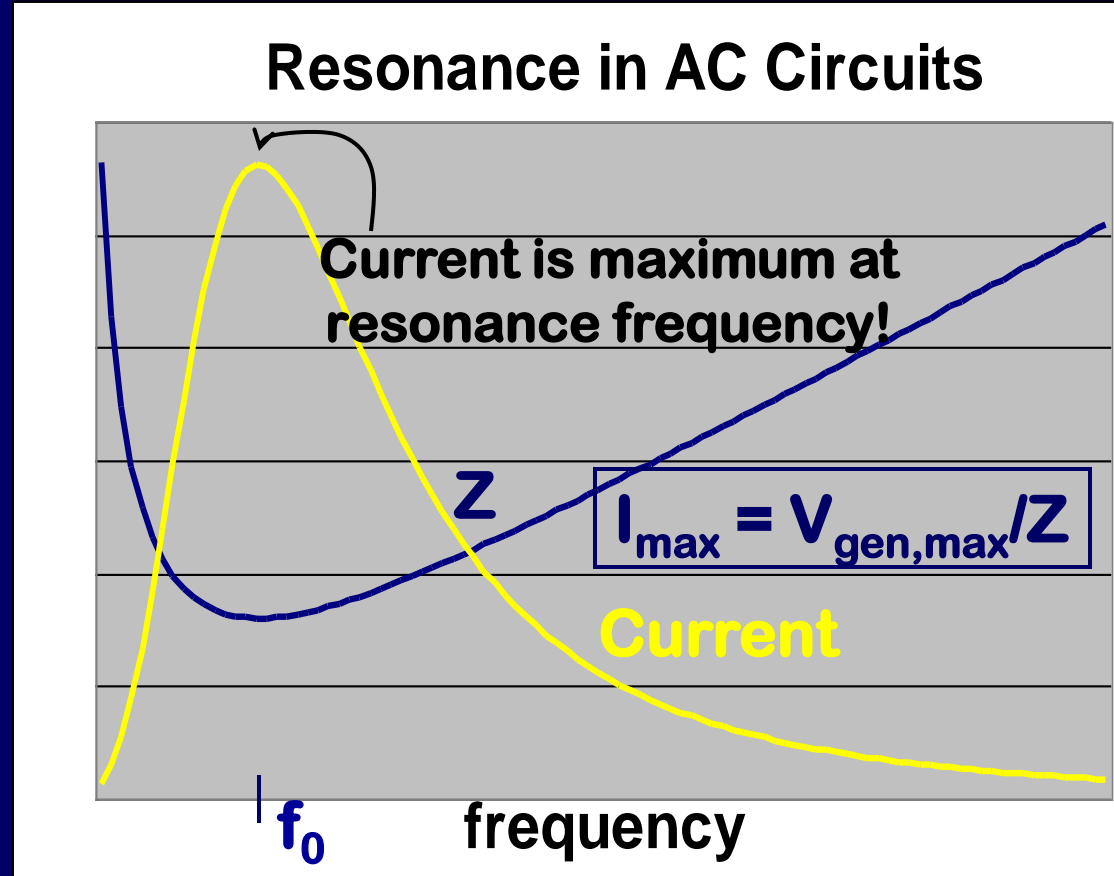

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

CheckPoint 14.1

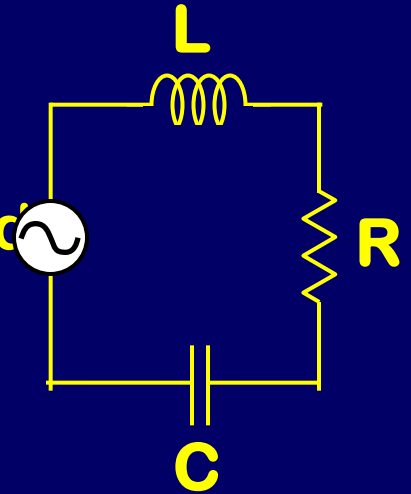As the frequency of the circuit is either raised above or lowered below the resonant frequency, the impedance of the circuit:




48% Always increases

30% Only increases for lowering the frequency



22% Only increases for raising the frequency

Z is minimum at f_0 !

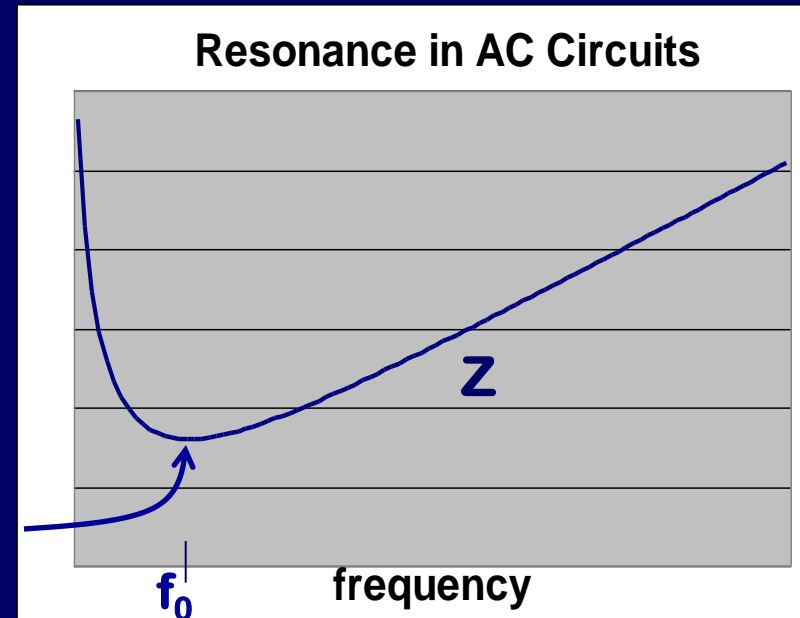

Any other frequency will have higher Z !

What is it good for?

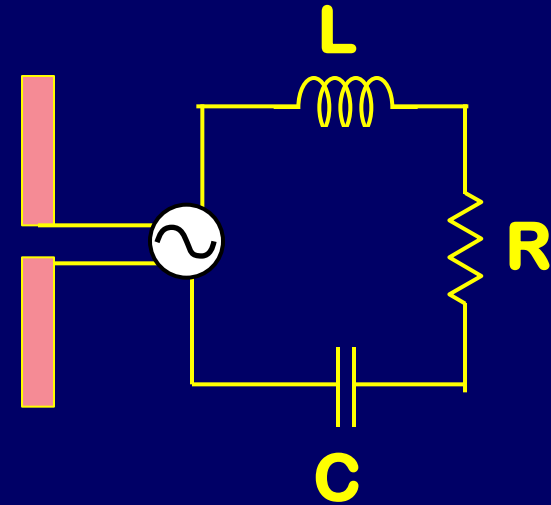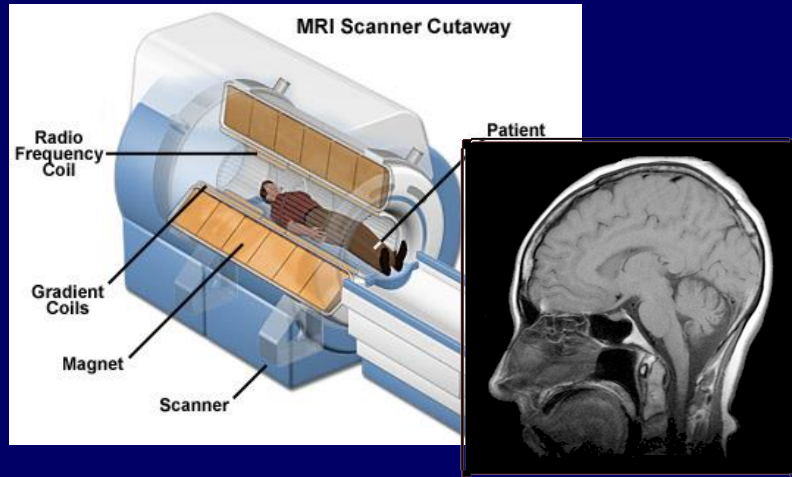

- Current through circuit depends on frequency (maximum at resonance frequency f_0)
 - Radio receiver
 - NMR/MRI
 - Picks out radio station freq f_0
 - Picks out signal from protons at f_0

Magnetic Resonance Imaging


Nobel Prize Medicine, 2003



Lauterbur, UIUC




Mansfield

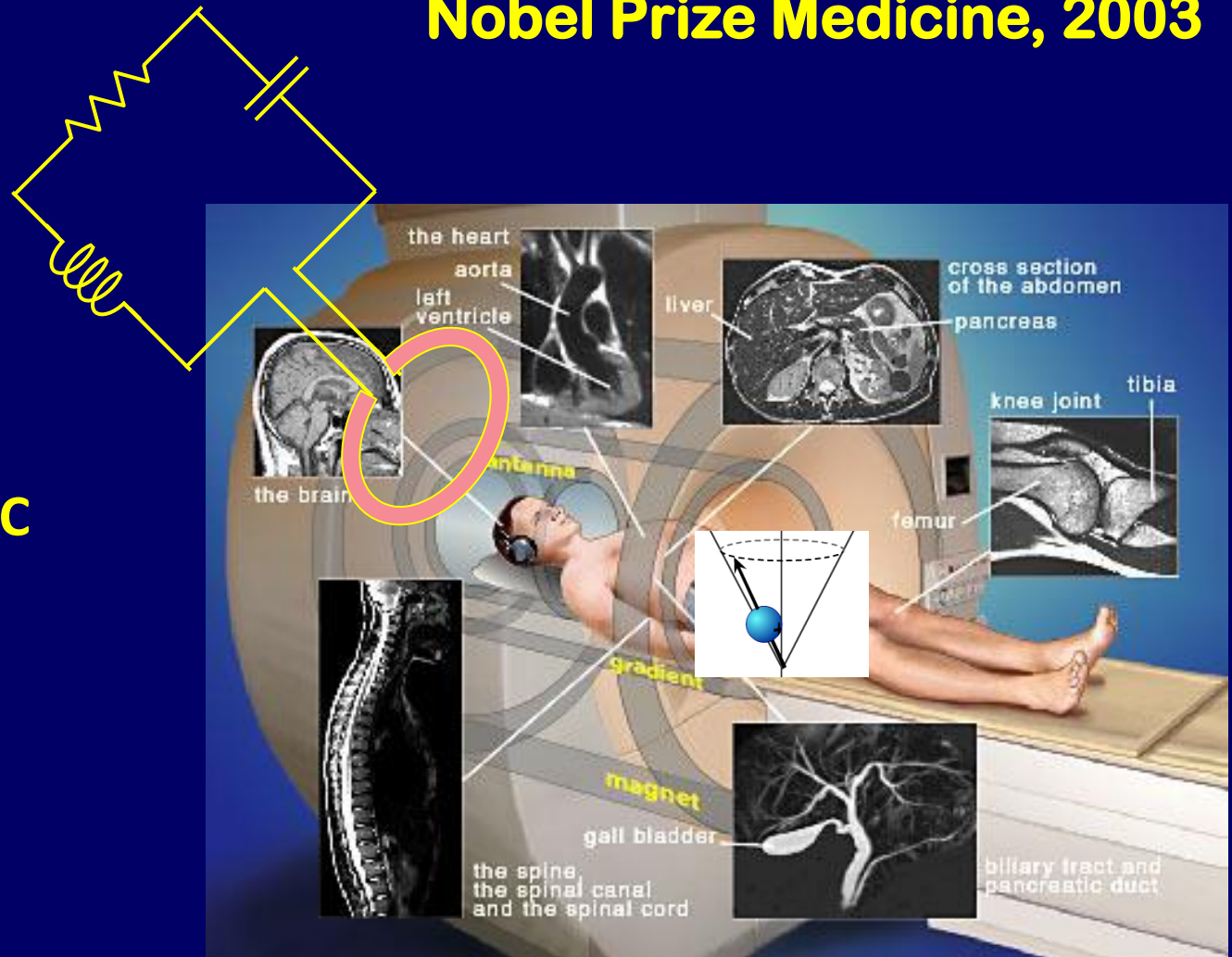


Faraday's Law + RLC circuit!

Example

Resonance in Radios

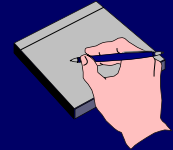

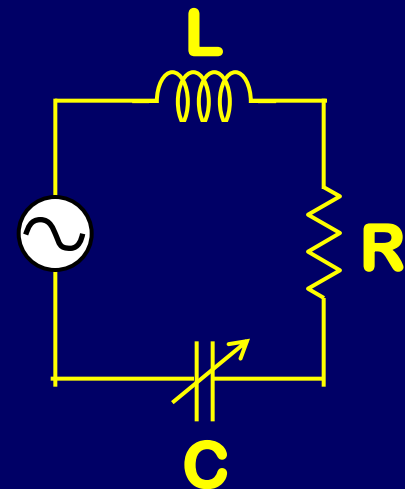An AC circuit with $R = 2 \, \Omega$, $L = 0.30 \, \mu\text{H}$ and variable capacitance is connected to an antenna to receive radio signals at the resonance frequency. If you want to listen to music broadcasted at $96.1 \, \text{MHz}$, what value of C should be used?



$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$C = \frac{1}{(2\pi f_0)^2 L} = \frac{1}{(2\pi \times 96.1 \times 10^6)^2 \times 0.30 \times 10^{-6}} = 9.1 \times 10^{-12} \, \text{F}$$



ACT: Radios



Your radio is tuned to FM 96.1 MHz and want to change it to FM 105.9 MHz, which of the following will work.

1. Increase Capacitance
2. Decrease Capacitance
3. Neither, you need to change R

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Higher frequency needs smaller capacitor so it can develop voltage quicker.

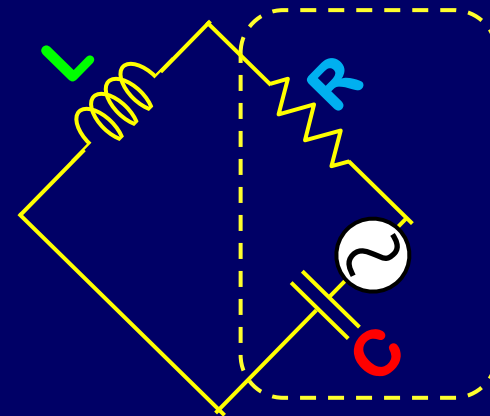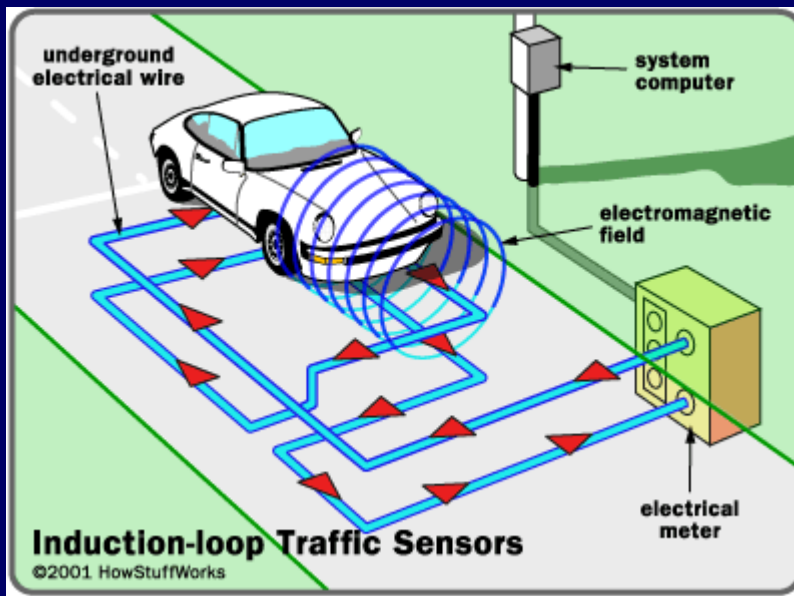Another use for RLC circuits: traffic sensors



AC Summary

Resistors: $V_{R,\max} = I_{\max} R$

In phase with I

Capacitors: $V_{C,\max} = I_{\max} X_C$ $X_C = 1/(2\pi f C)$

Lags I

Inductors: $V_{L,\max} = I_{\max} X_L$ $X_L = 2\pi f L$

Leads I

Generator: $V_{\text{gen},\max} = I_{\max} Z$ $Z = \sqrt{R^2 + (X_L - X_C)^2}$

Can lead or lag I $\tan(\phi) = (X_L - X_C)/R$

Power is only dissipated in resistor:

$$\bar{P} = \frac{1}{2} I_{\max} V_{\text{gen},\max} \cos(\phi)$$