






Phys 102 – Lecture 8


Circuit analysis and Kirchhoff's rules

Recall from last time...

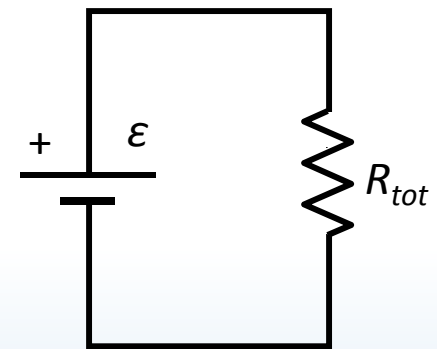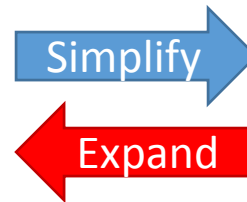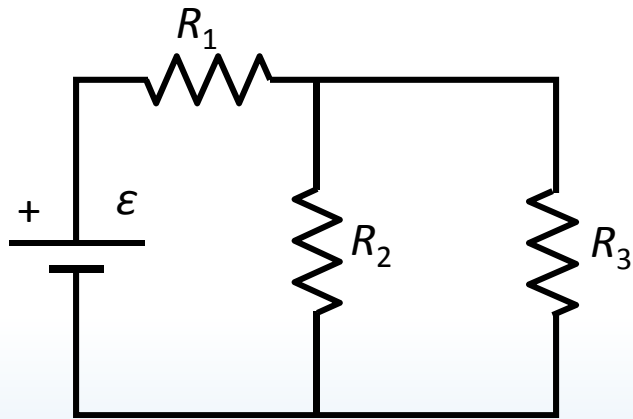We solved circuits like... by combining series & parallel components



What about a circuit like...

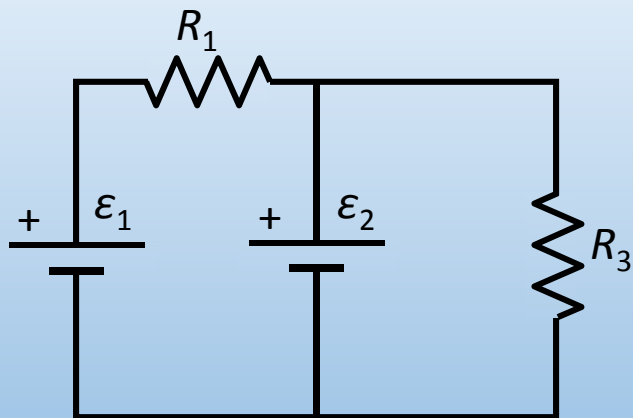


Kirchhoff's loop rule

Voltages around a loop sum to zero

$$\sum \Delta V = 0$$


Is voltage positive or negative?

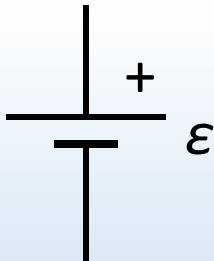

Batteries: + end is always at higher potential



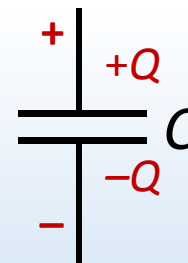
Resistors: higher/lower potential depends on current direction




Capacitors: higher/lower potential depends on which plate has +Q/-Q

Label +/- for higher/lower electric potential

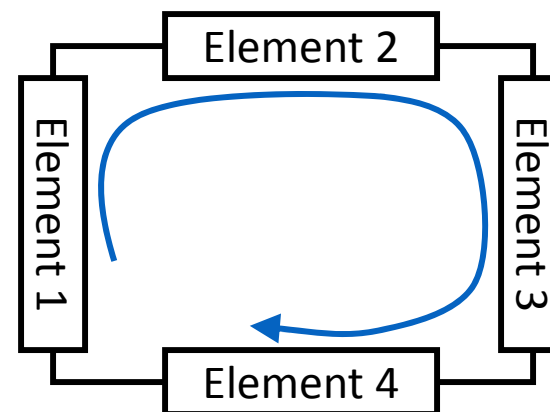Go around loop and write $+V_{\text{element}}$ if electric potential increases $-V_{\text{element}}$ if it decreases



Calculation: single loop practice

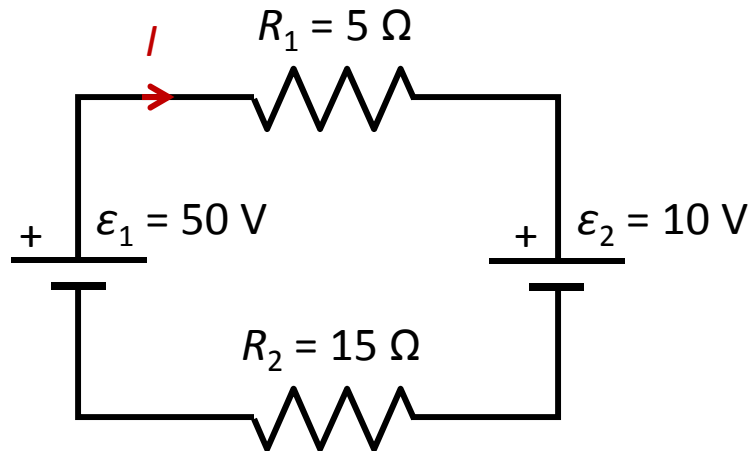

Calculate the current I in the circuit



What if we go around the loop the “wrong” way?

What if we’re not given the current direction?

What if we pick the “wrong” direction?

Calculation: single loop practice

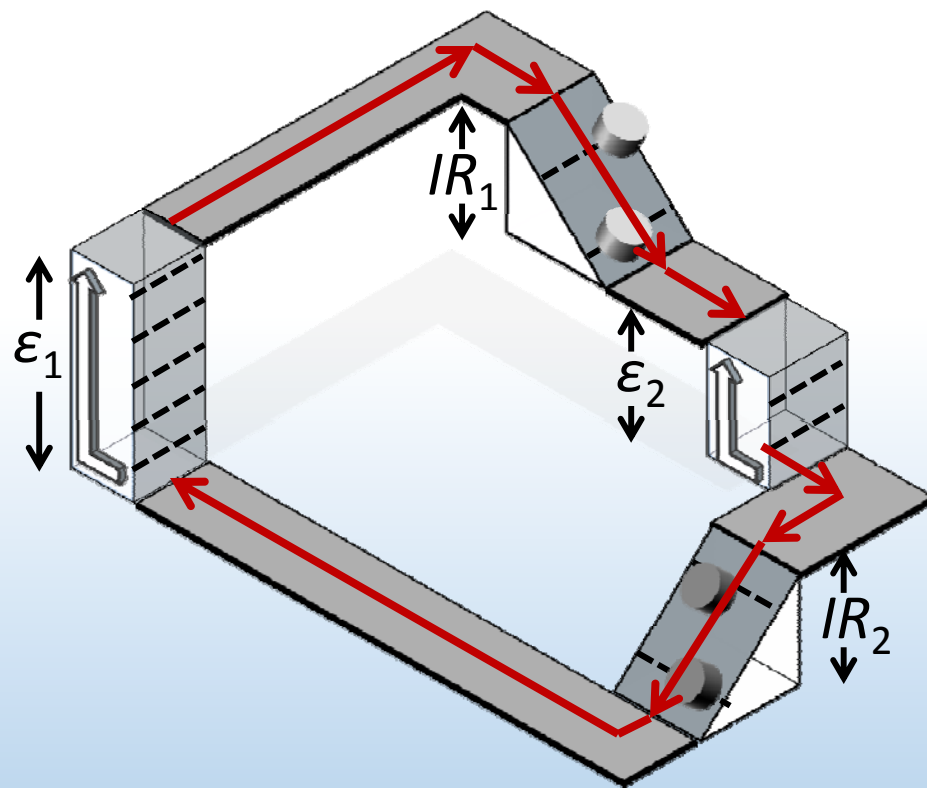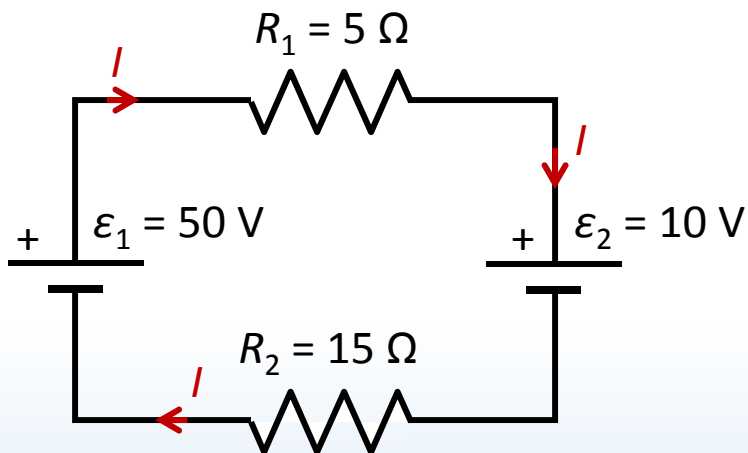How can the current be driven opposite battery 2?






ACT: Checkpoint 1.1

Calculate the current through R_1 .

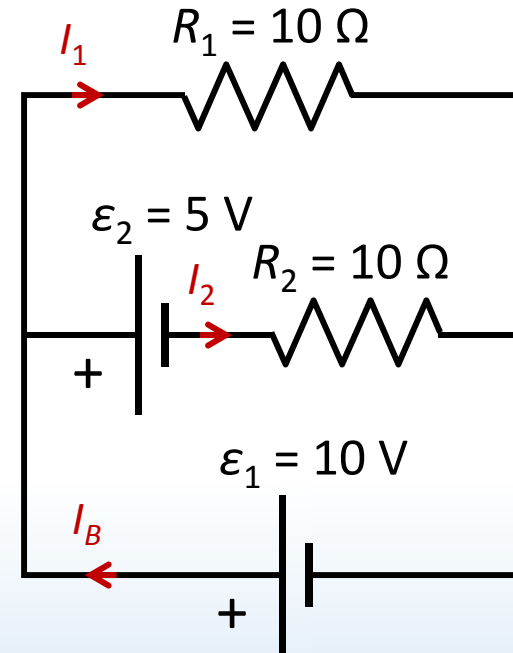- A. $I_1 = 0.5 \text{ A}$
- B. $I_1 = 1.0 \text{ A}$
- C. $I_1 = 1.5 \text{ A}$






ACT: Checkpoint 1.2



Calculate the current through R_2 .

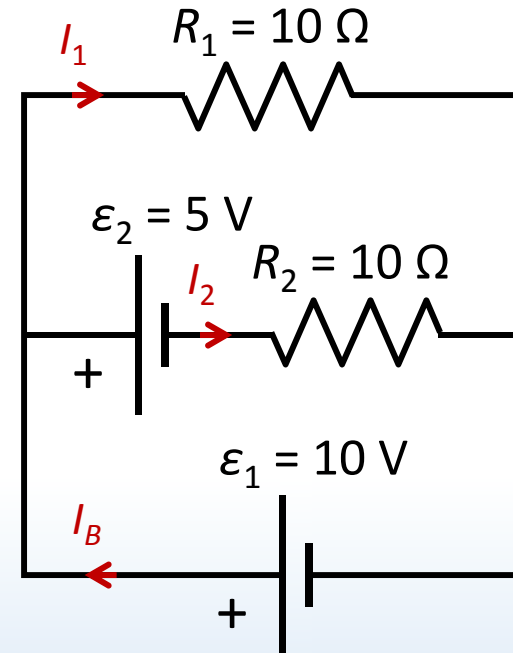- A. $I_1 = 0.5 \text{ A}$
- B. $I_1 = 1.0 \text{ A}$
- C. $I_1 = 1.5 \text{ A}$



Nerve cell equivalent circuit

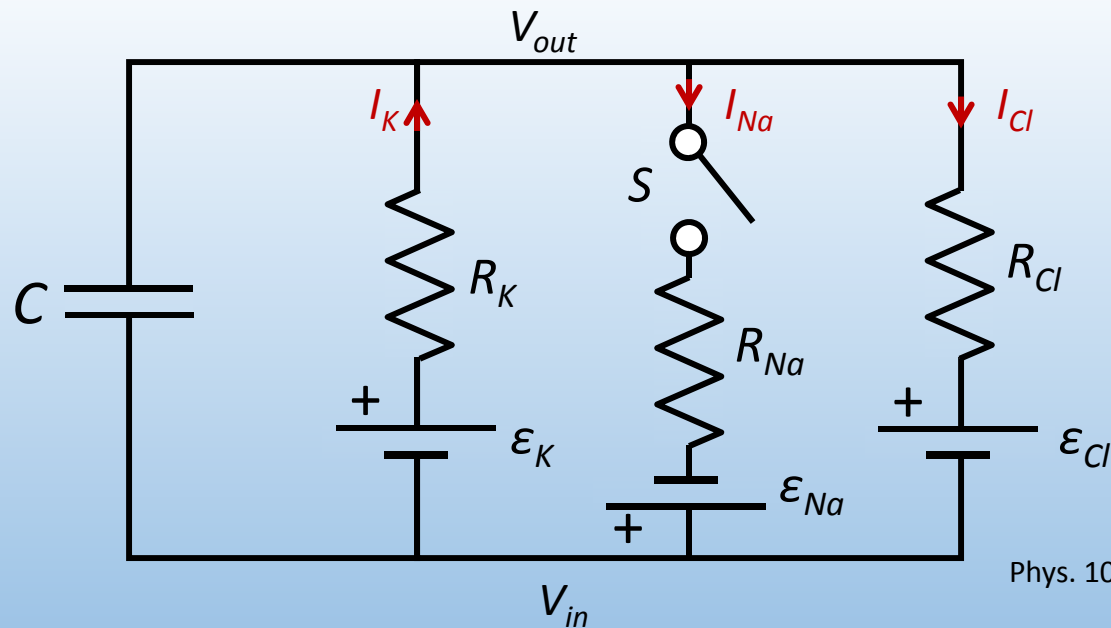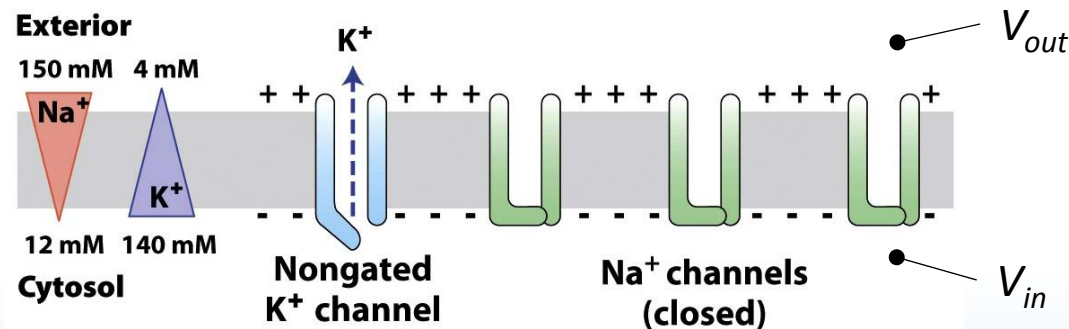
Neurons have different types of ion channels (K^+ , Na^+ , and Cl^-) that pump current into and out of cell – act like batteries!





ACT: loop

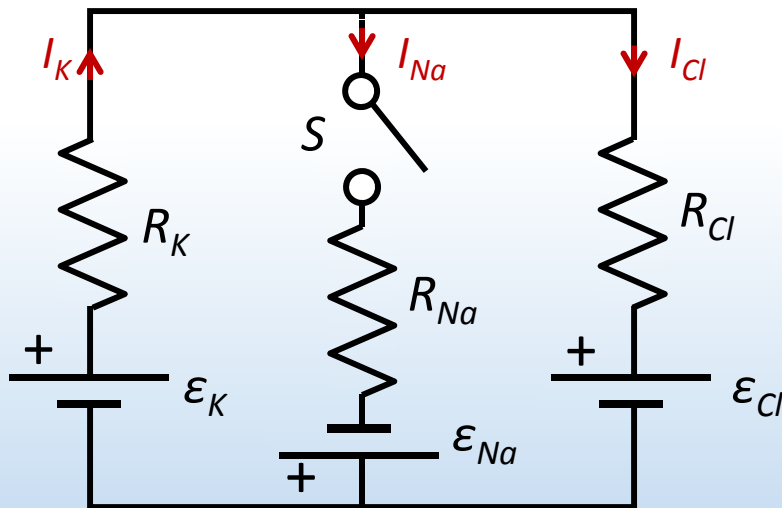Na^+ channels have a “gate” (represented by the switch S) that allows or blocks ion flow. In its resting state, a Na^+ channel is shut (i.e. switch S is open). Which equation is correct?



A. $+\epsilon_K - I_K R_K - I_K R_{Cl} - \epsilon_{Cl} = 0$


B. $+\epsilon_K - I_K R_K - I_{Na} R_{Na} - \epsilon_{Na} = 0$

C. $+\epsilon_K + I_K R_K - I_{Cl} R_{Cl} - \epsilon_{Cl} = 0$

Calculation: electric potential


Find the electric potential difference across the cell $V_{in} - V_{out}$
(Assume $V_{out} = 0$ for reference)
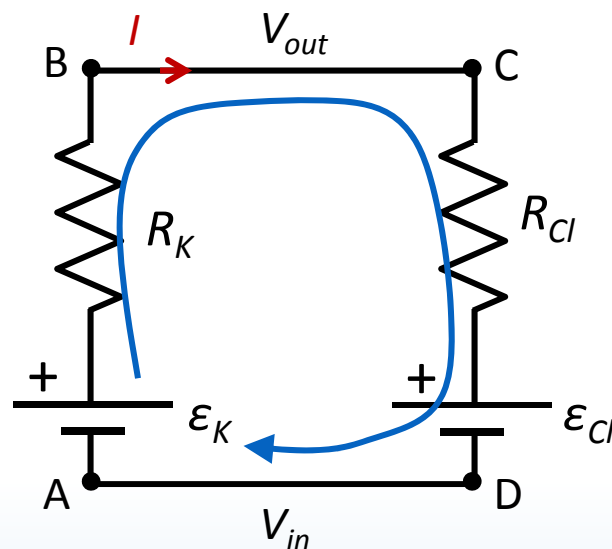
$$\mathcal{E}_K - IR_K - IR_{Cl} - \mathcal{E}_{Cl} = 0$$



$$V_{in} + \mathcal{E}_K - IR_K = V_{out}$$
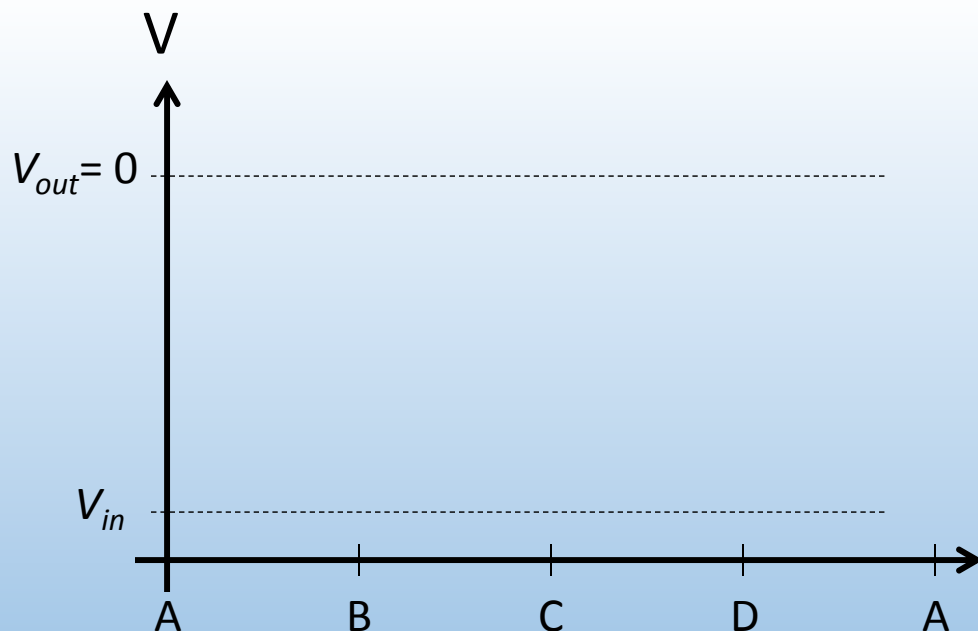
$$\text{or: } V_{out} - IR_{Cl} - \mathcal{E}_{Cl} = V_{in}$$




Kirchhoff's junction rule

The sum of currents into a junction equals the sum of currents out of a junction

$$\sum I_{in} = \sum I_{out}$$

Example:

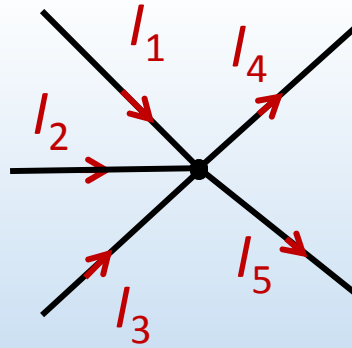




ACT: Checkpoint 1.3

Calculate the current through the battery I_B .

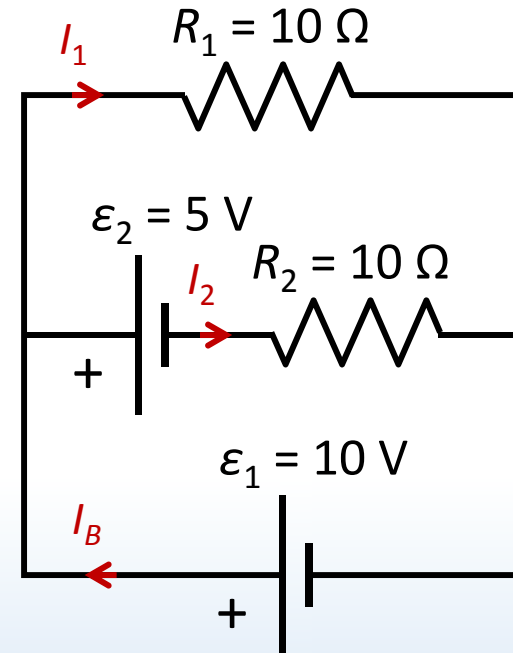
- A. $I_1 = 0.5 \text{ A}$
- B. $I_1 = 1.0 \text{ A}$
- C. $I_1 = 1.5 \text{ A}$



Calculation: Kirchhoff's laws



In the circuit, the current through R_C is 0. What is the current through R_3 and the value of R_x ?

From EX1 FA13

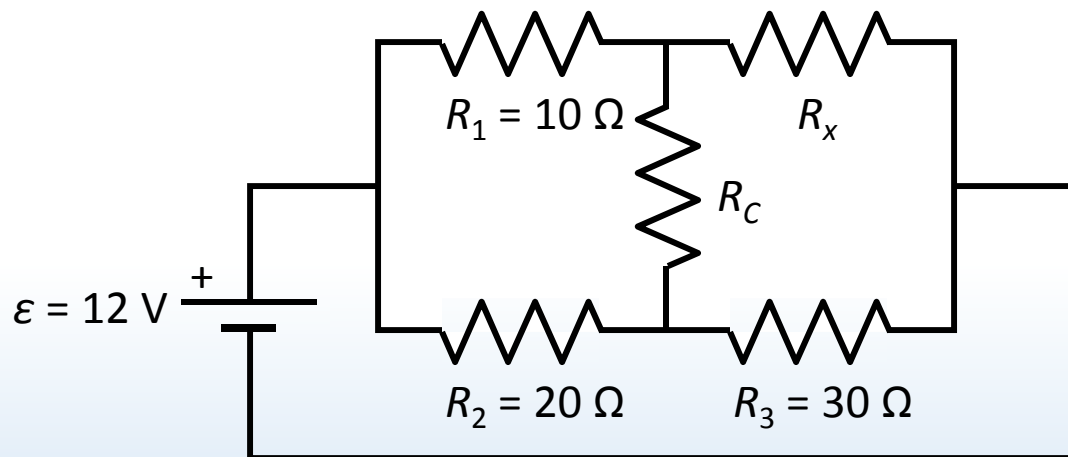

Nerve cell equivalent circuit

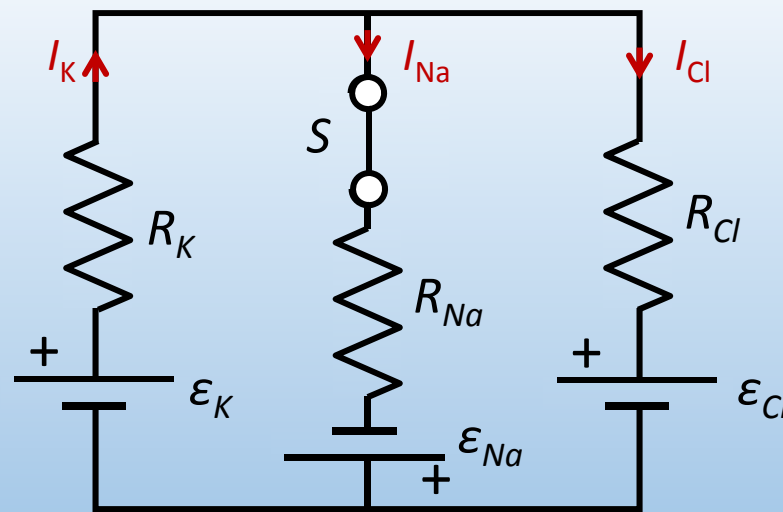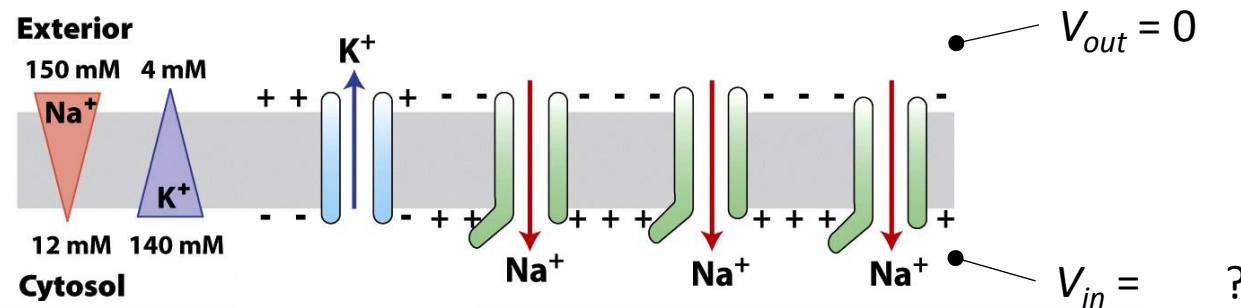
During nerve impulse, Na^+ channels open (i.e. switch S closes) and allow Na^+ to enter the cell



Calculation: two loop circuit

Given the circuit to the right,
find I_K , I_{Na} and I_{Cl} and $V_{in} - V_{out}$.
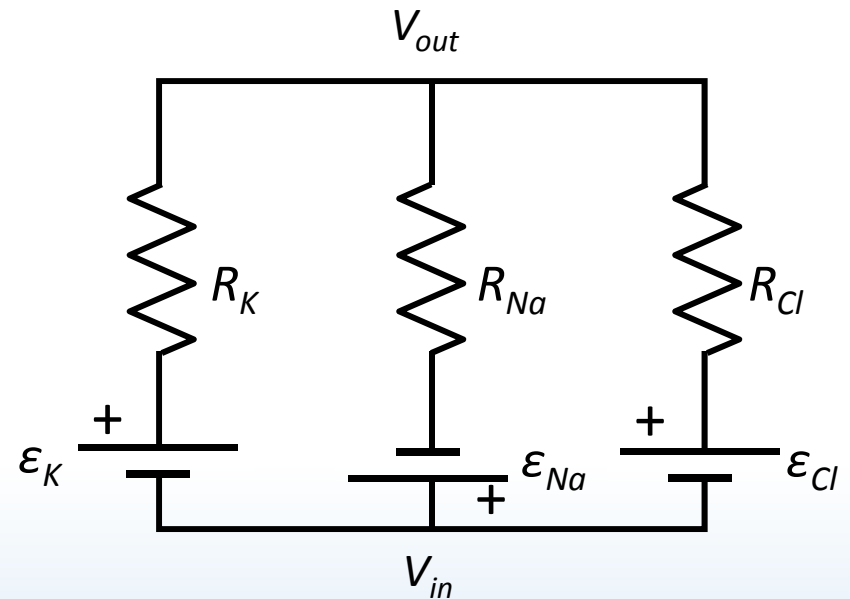
$$\begin{aligned}\varepsilon_K &= 80 \text{ mV}, \varepsilon_{Na} = 60 \text{ mV}, \varepsilon_{Cl} = 50 \text{ mV} \\ R_K &= 2 \text{ M}\Omega, R_{Na} = 0.2 \text{ M}\Omega, R_{Cl} = 5 \text{ M}\Omega\end{aligned}$$




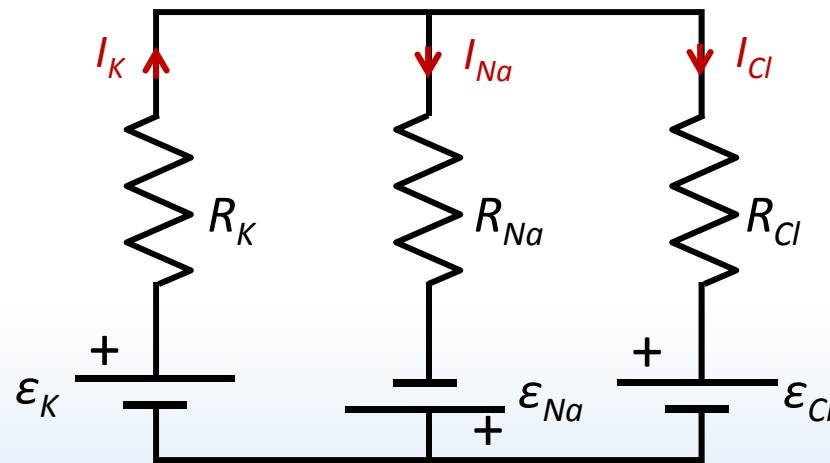1. Label all currents
2. Label +/– for all elements
3. Choose loop and direction
4. Write down voltage differences



ACT: Kirchhoff loop rule

What is the correct expression for “Loop 3” in the circuit below?



- A. $+\epsilon_{Cl} - I_{Cl}R_{Cl} - I_{Na}R_{Na} + \epsilon_{Na} = 0$
- B. $+\epsilon_{Cl} - I_{Cl}R_{Cl} + I_{Na}R_{Na} + \epsilon_{Na} = 0$
- C. $+\epsilon_{Cl} + I_{Cl}R_{Cl} - I_{Na}R_{Na} + \epsilon_{Na} = 0$

Calculation: two loop circuit

Given the circuit to the right,
find I_K , I_{Na} and I_{Cl} and $V_{in} - V_{out}$.

$$\begin{aligned}\epsilon_K &= 80 \text{ mV}, \epsilon_{Na} = 60 \text{ mV}, \epsilon_{Cl} = 50 \text{ mV} \\ R_K &= 2 \text{ M}\Omega, R_{Na} = 0.2 \text{ M}\Omega, R_{Cl} = 5 \text{ M}\Omega\end{aligned}$$


We have 3 unknowns, need 3 equations

Loop 1:

Loop 2:

Loop 3:


5. Write down junction rule

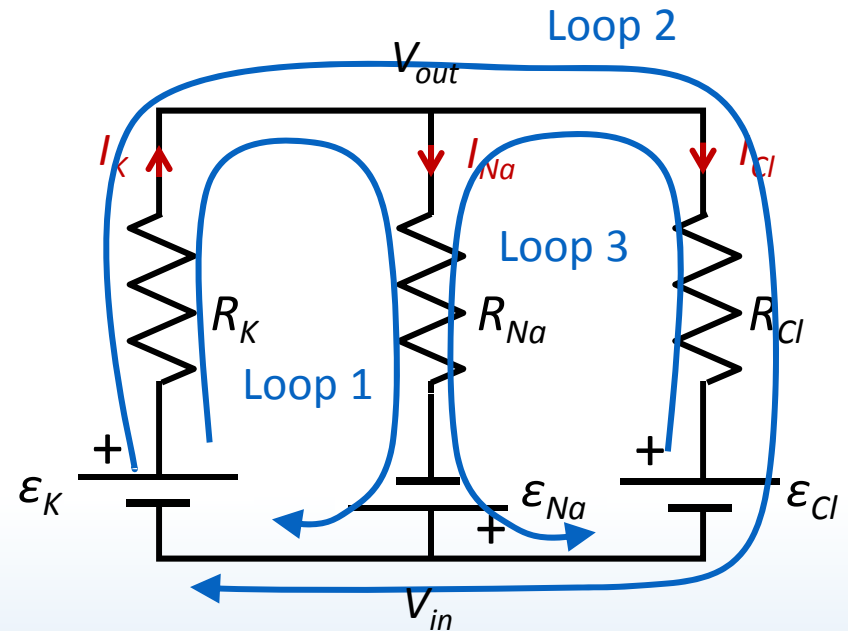



ACT: Kirchhoff junction rule

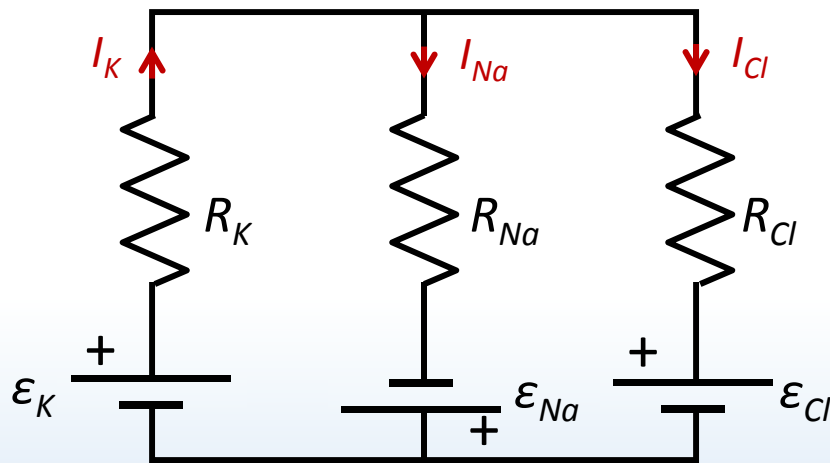What is the correct expression for junction in the circuit?




- A. $I_K + I_{Na} = I_{Cl}$
- B. $I_{Na} + I_{Cl} = I_K$
- C. $I_{Cl} + I_K = I_{Na}$

Calculation: two loop circuit

Given the circuit to the right,
find I_K , I_{Na} and I_{Cl} and $V_{in} - V_{out}$.

$$\begin{aligned}\varepsilon_K &= 80 \text{ mV}, \varepsilon_{Na} = 60 \text{ mV}, \varepsilon_{Cl} = 50 \text{ mV} \\ R_K &= 2 \text{ M}\Omega, R_{Na} = 0.2 \text{ M}\Omega, R_{Cl} = 5 \text{ M}\Omega\end{aligned}$$

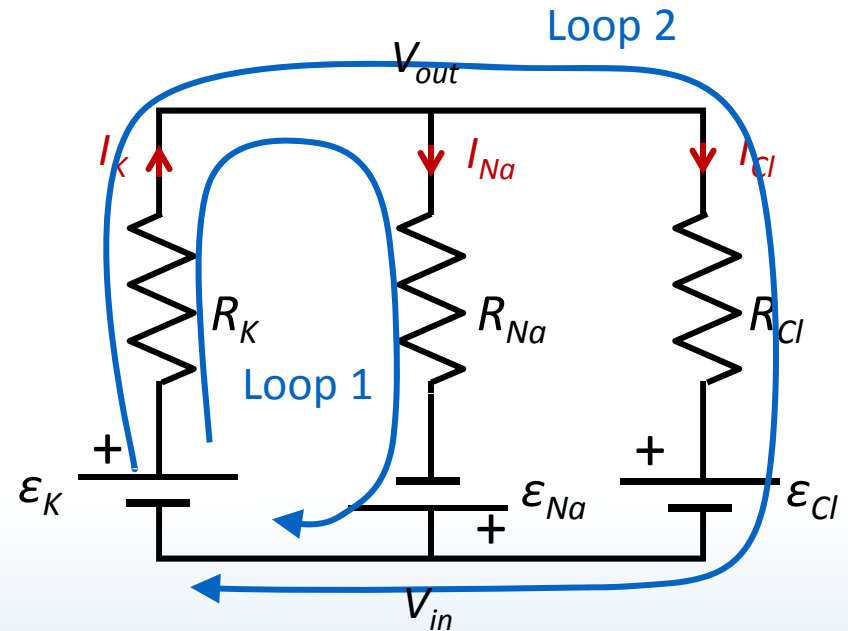3 equations, 3 unknowns,
the rest is algebra!



$$(1) \quad +\varepsilon_K - I_K R_K - I_{Na} R_{Na} + \varepsilon_{Na} = 0 \quad +80 - 2I_K - 0.2I_{Na} + 60 = 0$$

$$(2) \quad +\varepsilon_K - I_K R_K - I_{Cl} R_{Cl} - \varepsilon_{Cl} = 0 \quad +80 - 2I_K - 5I_{Cl} - 50 = 0$$

$$(3) \quad I_{Na} + I_{Cl} = I_K \quad +80 - 2I_K - 5(I_K - I_{Na}) - 50 = 0$$

Substitute Eq. (3) into Eq. (2) and rearrange

$$(2') \quad +30 - 7I_K + 5I_{Na} = 0$$

Calculation: two loop circuits

Now 2 equations (1 and 2'), 2 unknowns (I_K and I_{Na})

$$(1) \quad +70 - I_K - 0.1I_{Na} = 0$$

$$I_K = 70 - 0.1I_{Na}$$

$$(2') \quad +30 - 7I_K + 5I_{Na} = 0$$

$$+30 - 7(70 - 0.1I_{Na}) + 5I_{Na} = 0$$

Substitute I_K in Eq. (1) into Eq. (2') and rearrange

$$-460 + 5.7I_{Na} = 0 \quad I_{Na} = \frac{460 \text{ mV}}{5.7 \text{ M}\Omega} = 81 \text{ nA}$$

Plug solution into Eq. (2') to get I_K

$$+30 - 7I_K + 5 \cdot 81 = 0 \quad I_K = \frac{435 \text{ mV}}{7 \text{ M}\Omega} = 62 \text{ nA}$$


Use junction Eq. (3) to get I_{Cl}

$$I_{Cl} = 62 - 81 = -19 \text{ nA}$$



ACT: Kirchhoff junction rule



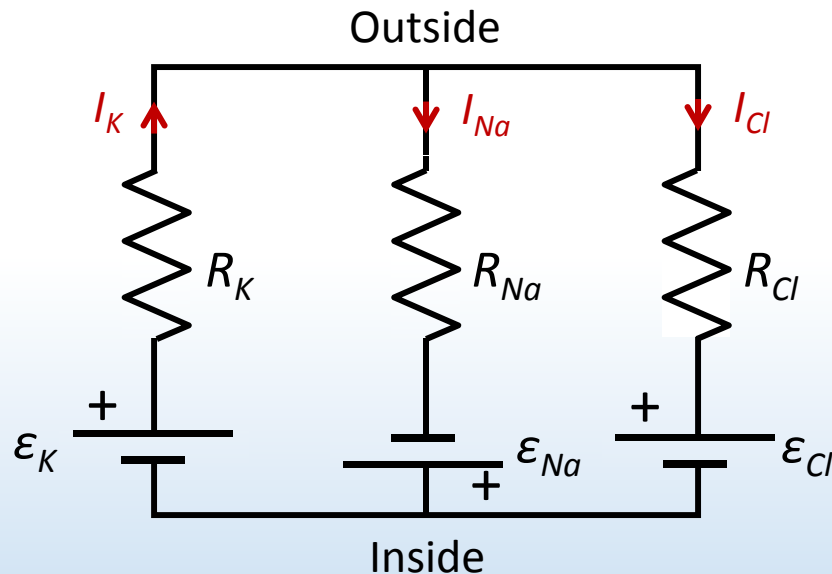
We found that $I_K = 81$ nA, $I_{Na} = 62$ nA and $I_{Cl} = -19$ nA. Which of the following statements is FALSE?



- A. I_K flows out of the cell
- B. I_{Na} flows into the cell
- C. I_{Cl} flows into the cell

Calculation: two loop circuit

Find the new $V_{in} - V_{out}$:

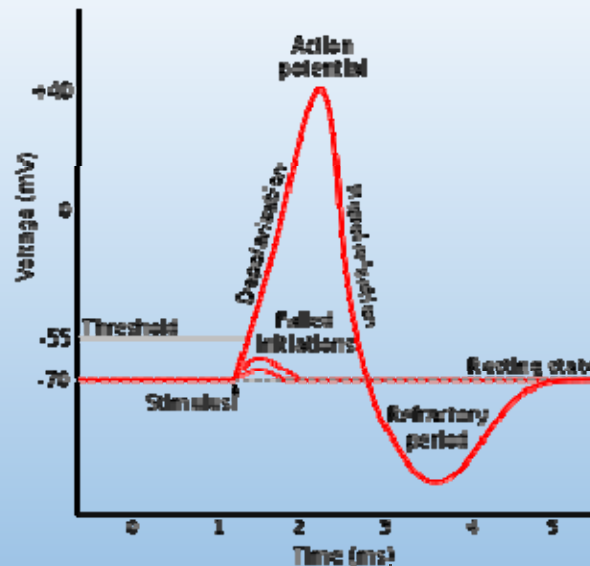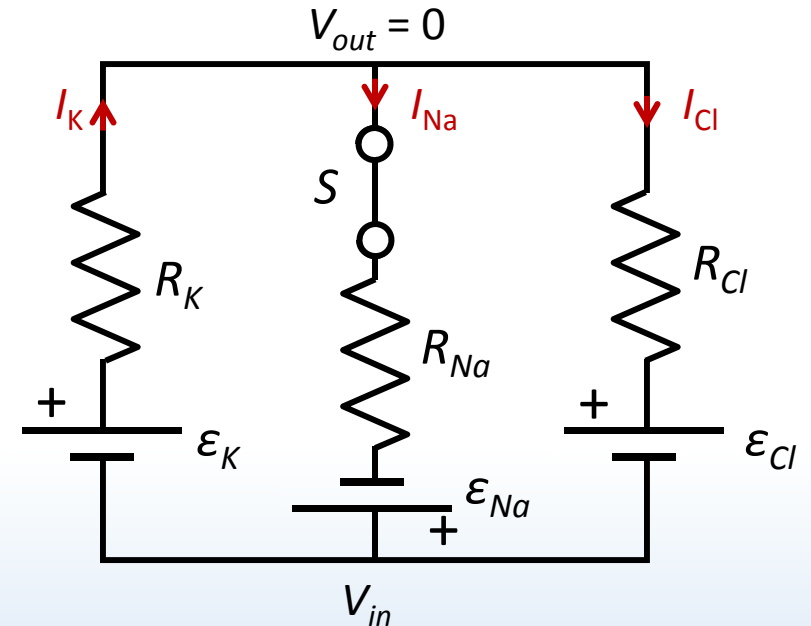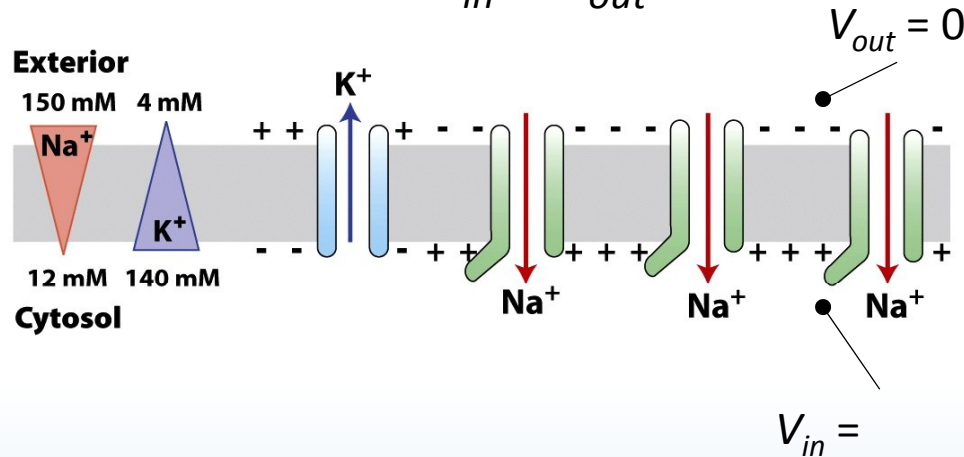

Summary of today's lecture

- Two basic principles:
- Kirchhoff loop rule

Voltages around circuit loop sum to zero (based on conservation of energy)

$$\sum \Delta V = 0$$

- Kirchhoff junction rule

Currents into a circuit branch equal currents out (based on conservation of charge)

$$\sum I_{in} = \sum I_{out}$$

Summary of today's lecture

- Basic approach to solving complex circuits:
 1. Label all currents
 2. Label $+/-$ for all elements
 3. Choose loop(s) and direction(s)
 4. Write down voltage differences
 5. Write down junction ruleThe rest is algebra!