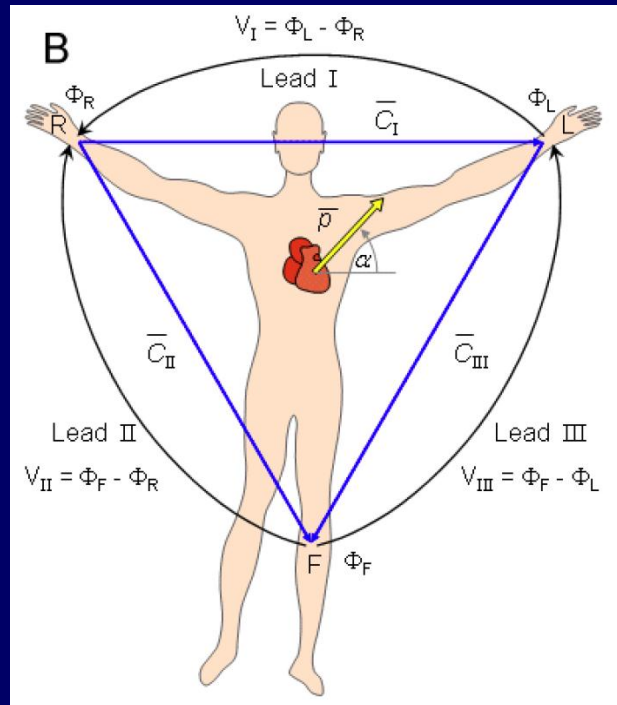


Physics 102: Lecture 06

Kirchhoff's Laws



Last Time

Last Lecture

- **Resistors in series:** $R_{eq} = R_1 + R_2 + R_3 + \dots$

Current through each is same; Voltage drop is IR_i




- **Resistors in parallel:** $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$

Voltage drop across each is the same; Current through each is V/R_i



- **Solved Circuits**

Today

- **What about this one?**

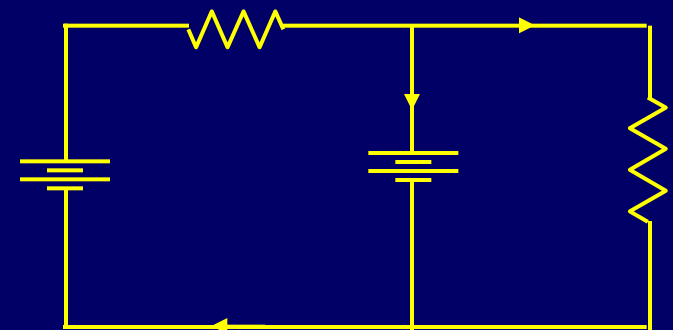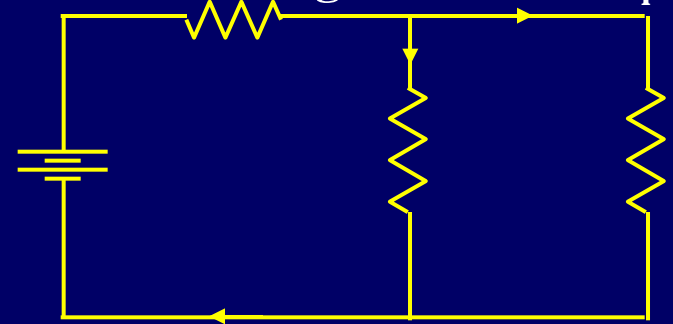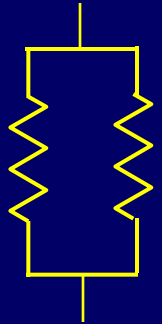

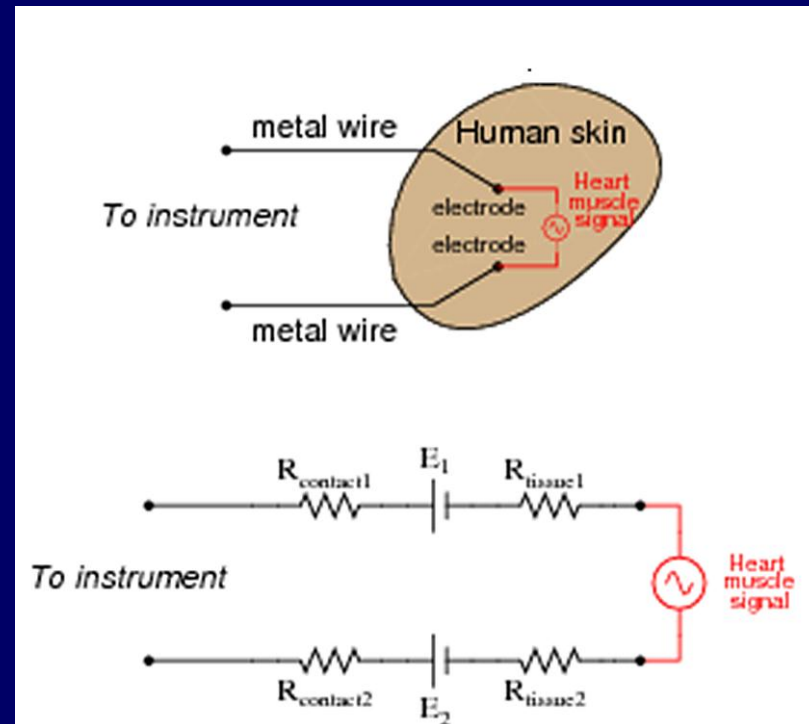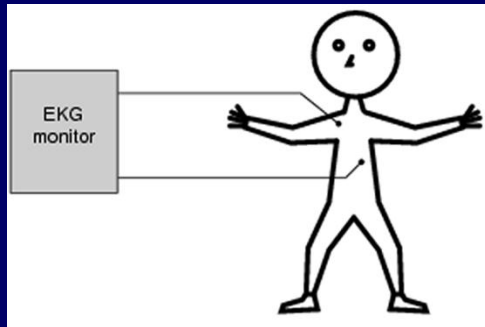When would you ever find a circuit like this?!?!



ϵ_1 and ϵ_2 arise from surface
electrochemistry...so what does the EKG
monitor really measure?

Kirchhoff's Rules

- Kirchhoff's Junction Rule (KJR):
 - Current going in equals current coming out.
- Kirchhoff's Loop Rule (KLR):
 - Sum of voltage drops around a loop is zero.


Kirchhoff's Junction Rule (KJR)

- Conceptual basis: **conservation of charge**
- At any junction in a circuit, the current that enters the junction equals the current that leaves the junction

- Example:

At junction:

$$I_1 + I_2 = I_3$$

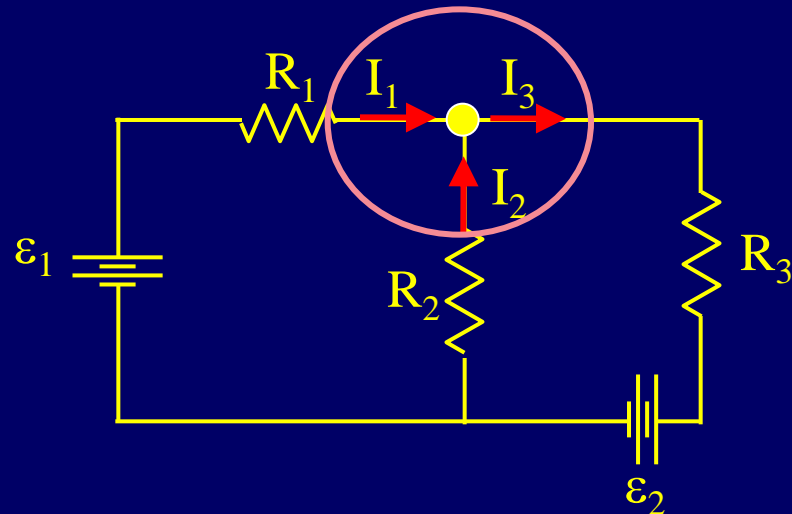


Kirchhoff's Loop Rule (KLR)

- Conceptual basis: **conservation of energy**
- Going around any complete loop in a circuit, the sum total of all the potential differences is zero
- Example:

Around the right loop:
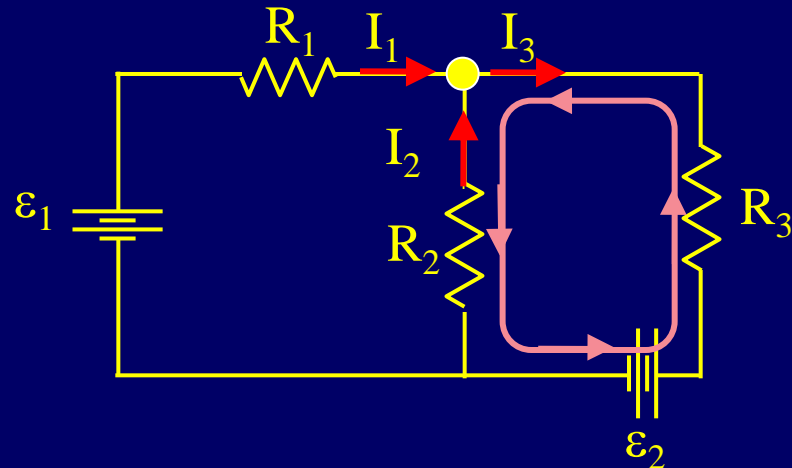
$$\varepsilon_2 + I_3 R_3 + I_2 R_2 = 0$$



Using Kirchhoff's Rules

(1) Label all currents

Choose any direction


(2) Label +/– for all elements

Current goes $+$ \Rightarrow $-$ (for resistors)

(3) Choose loop and direction

(4) Write down voltage drops

Be careful about signs

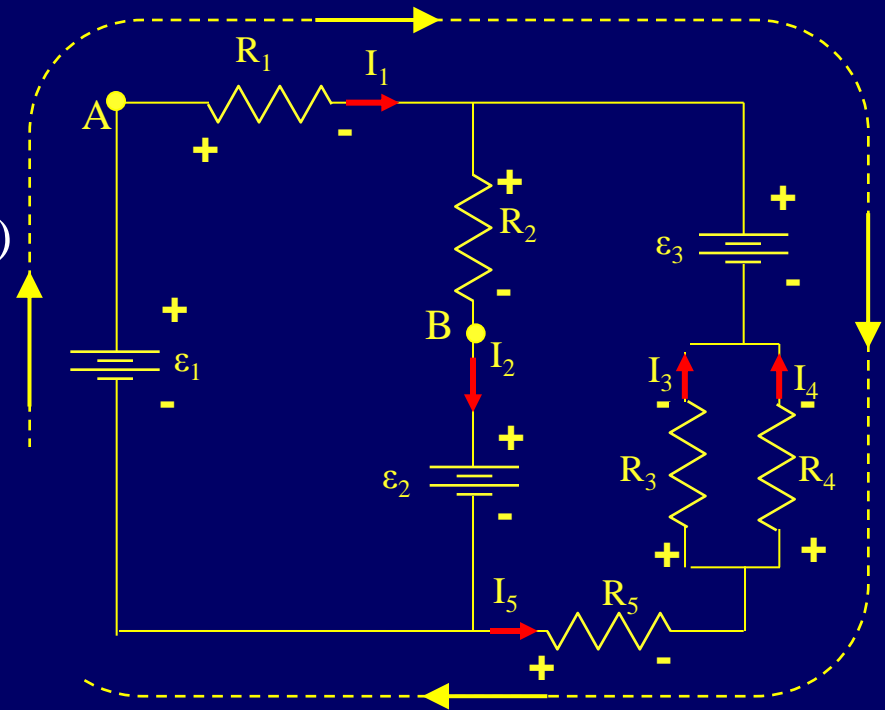


Example



Loop Rule Practice

Find I:

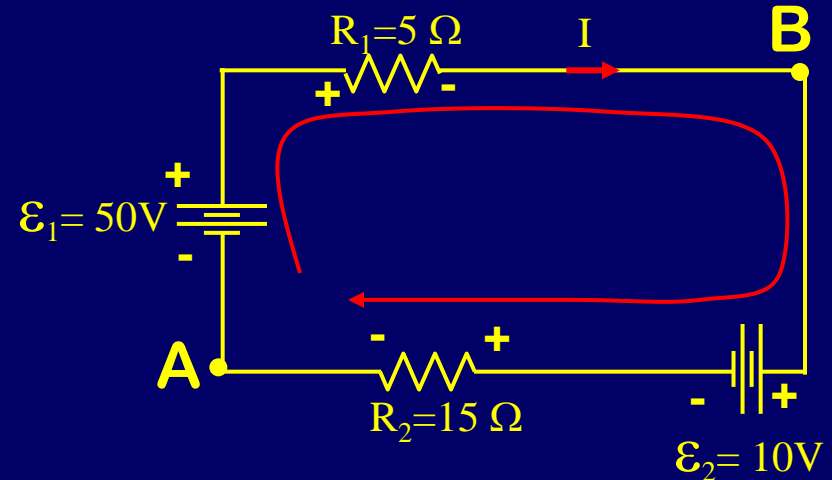1. Label currents
2. Label elements +/-
3. Choose loop
4. Write KLR



$$\begin{aligned} +\mathcal{E}_1 - IR_1 - \mathcal{E}_2 - IR_2 &= 0 \\ +50 - 5I - 10 - 15I &= 0 \\ I &= +2 \text{ Amps} \end{aligned}$$


What is the electric potential at V_B (assume $V_A = 0$):

$$\begin{aligned} V_A + \mathcal{E}_1 - IR_1 &= V_B \\ 0 + 50 - 2 \times 5 &= 40V = V_B \end{aligned}$$

Checkpoint 1

Calculate the current through R_1 .


1) $I_1 = 0.5 \text{ A}$ 2) $I_1 = 1.0 \text{ A}$ 3) $I_1 = 1.5 \text{ A}$

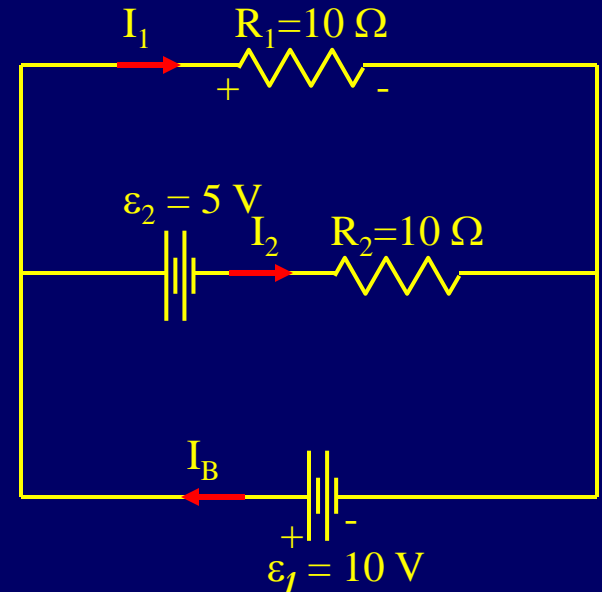

Checkpoint 2

Calculate the current through R_1 .

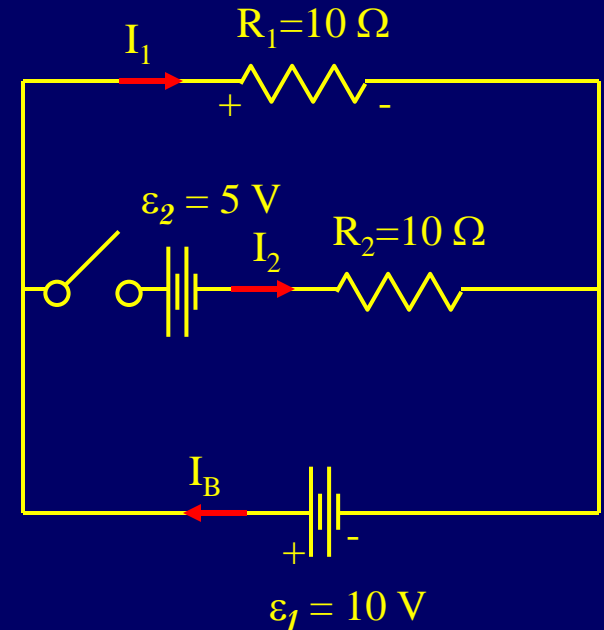- 1) $I_1 = 0.5 \text{ A}$ 2) $I_1 = 1.0 \text{ A}$ 3) $I_1 = 1.5 \text{ A}$



ACT: Voltage Law

How would I_1 change if the switch was opened?


- 1) Increase 2) No change 3) Decrease



ACT/Checkpoint 2

Calculate the current through R_2 .

A) $I_2 = 0.5 \text{ A}$ B) $I_2 = 1.0 \text{ A}$ C) $I_2 = 1.5 \text{ A}$

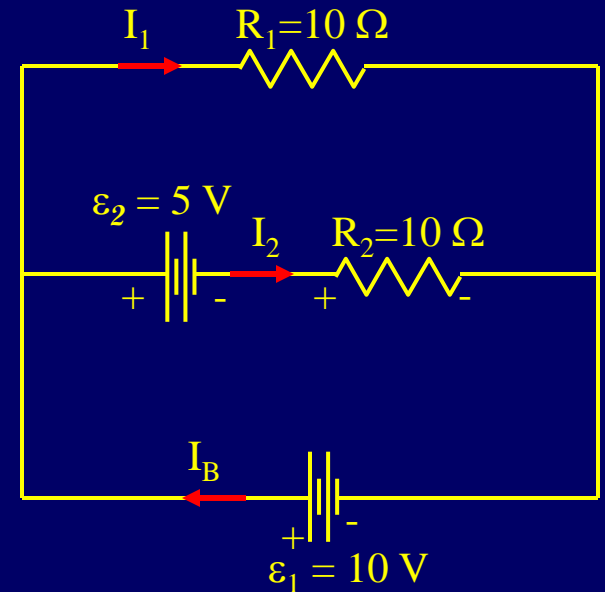


Checkpoint 2

How do I know the direction of I_2 ?

It doesn't matter. Choose whatever direction you like. Then solve the equations to find I_2 . If the result is positive, then your initial guess was correct. If result is negative, then actual direction is opposite to your initial guess.

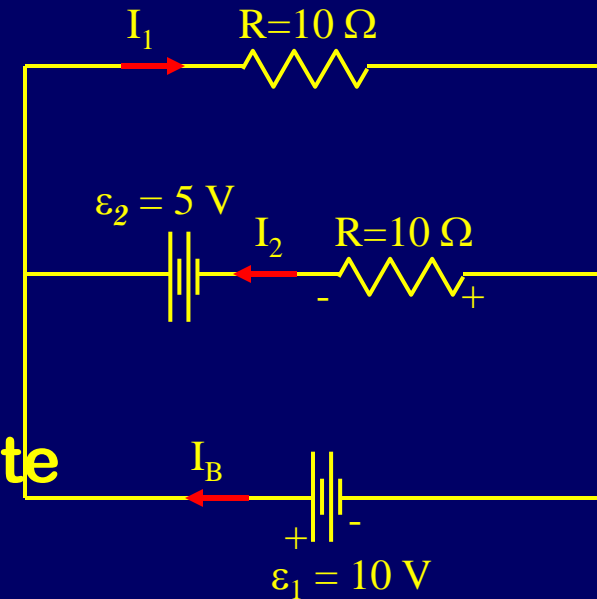
Work through Checkpoint with opposite sign for I_2 :



Kirchhoff's Junction Rule

Current Entering = Current Leaving


$$I_1 = I_2 + I_3$$

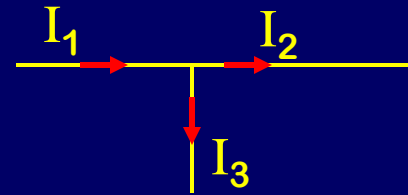


ACT/Checkpoint 3

Calculate the current through battery.

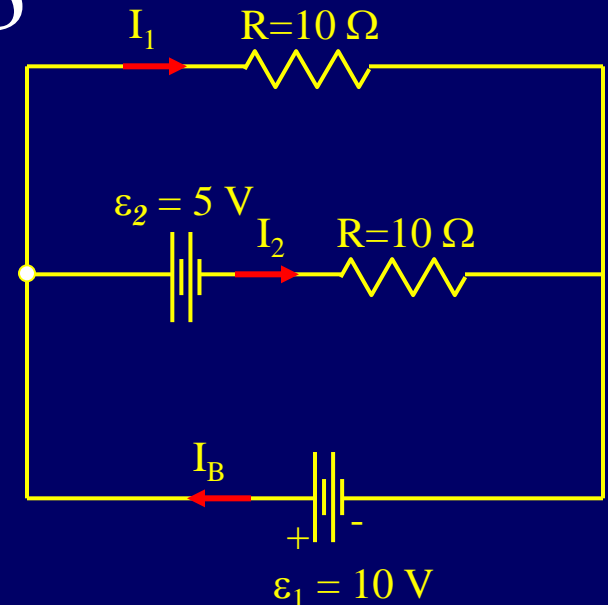- 1) $I_B = 0.5 \text{ A}$ 2) $I_B = 1.0 \text{ A}$ 3) $I_B = 1.5 \text{ A}$



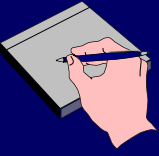

Kirchhoff's Laws

(1) Label all currents

Choose any direction

(2) Label +/– for all elements

Current goes $+$ \Rightarrow $-$ (for resistors)

(3) Choose loop and direction


Your choice!

(4) Write down voltage drops

Follow any loops

(5) Write down junction equation

$$I_{\text{in}} = I_{\text{out}}$$

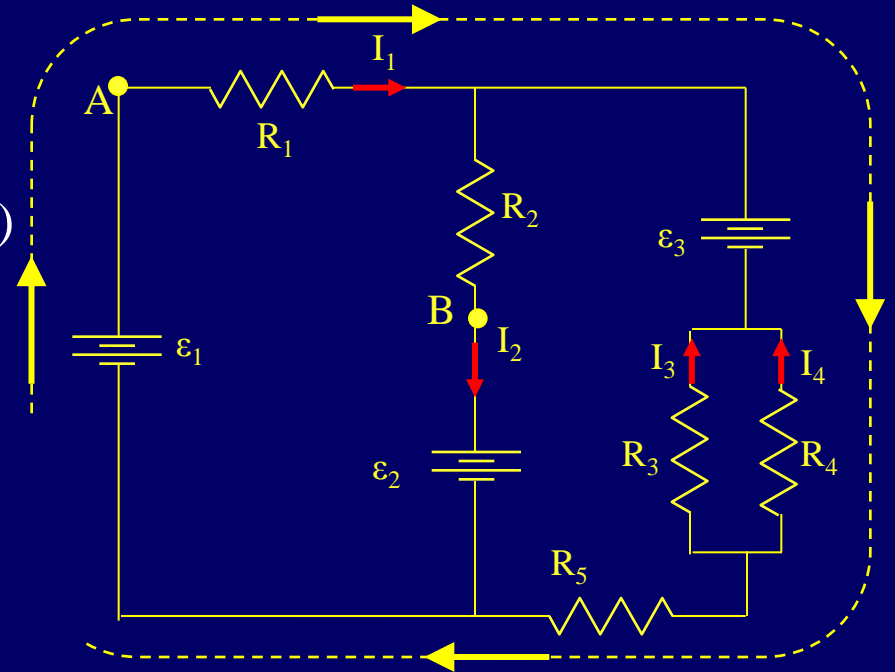


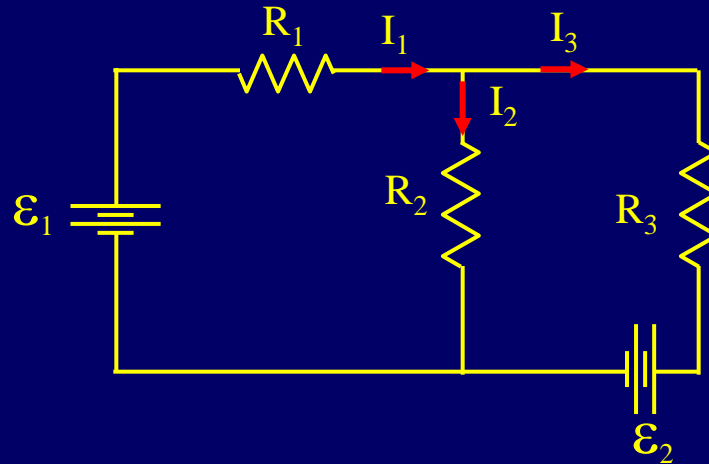Example




You try it!

In the circuit below you are given \mathcal{E}_1 , \mathcal{E}_2 , R_1 , R_2 and R_3 . Find I_1 , I_2 and I_3 .



Example

You try it!

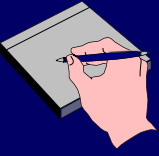

In the circuit below you are given \mathcal{E}_1 , \mathcal{E}_2 , R_1 , R_2 and R_3 . Find I_1 , I_2 and I_3 .


- ✓ 1. Label all currents (Choose any direction)
- ✓ 2. Label +/- for all elements (Current goes + \Rightarrow - for resistor)
- ✓ 3. Choose loop and direction (Your choice!)
- ✓ 4. Write down voltage drops (Potential increases or decreases?)

Loop 1: $+\mathcal{E}_1 - I_1 R_1 + I_2 R_2 = 0$

Loop 2: $+\mathcal{E}_1 - I_1 R_1 - I_3 R_3 - \mathcal{E}_2 = 0$

- ✓ 5. Write down junction equation

Node: $I_1 + I_2 = I_3$

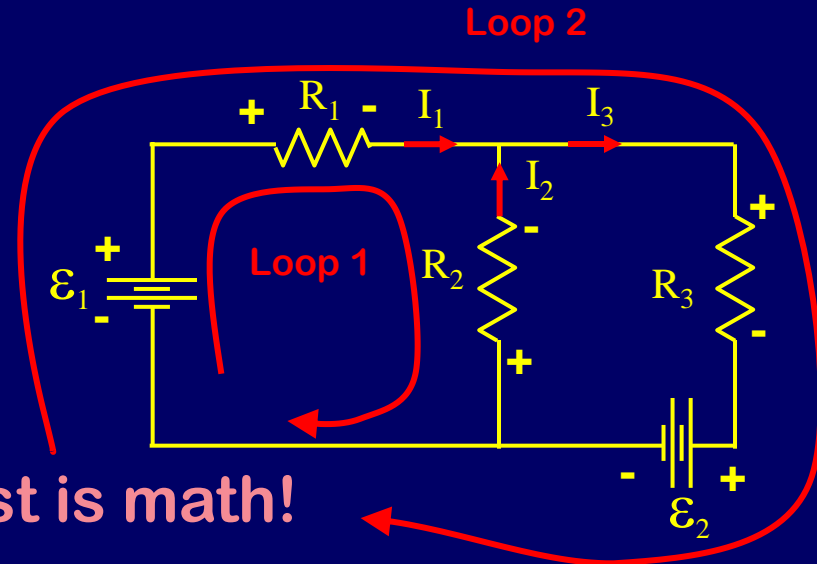


3 Equations, 3 unknowns the rest is math!



ACT: Kirchhoff loop rule

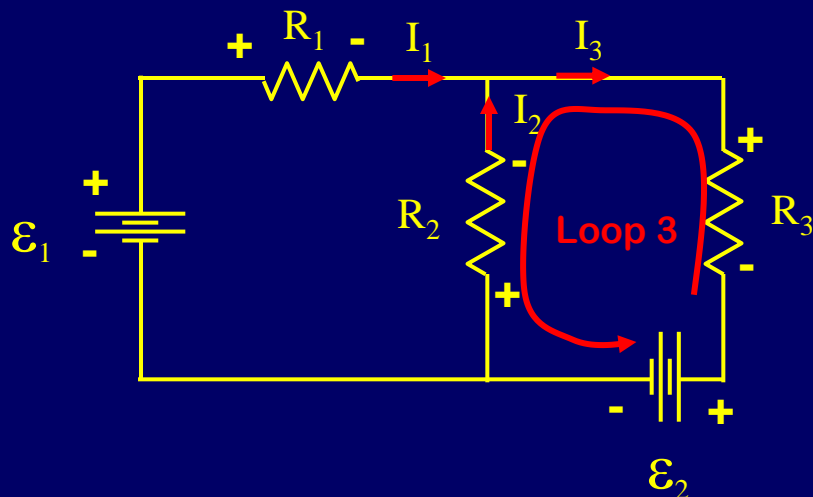What is the correct expression for “Loop 3” in the circuit below?




1) $+\mathcal{E}_2 - I_3 R_3 - I_2 R_2 = 0$

2) $+\mathcal{E}_2 - I_3 R_3 + I_2 R_2 = 0$


3) $+\mathcal{E}_2 + I_3 R_3 + I_2 R_2 = 0$

Example

Let's put in real numbers

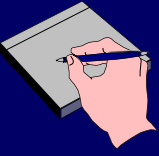

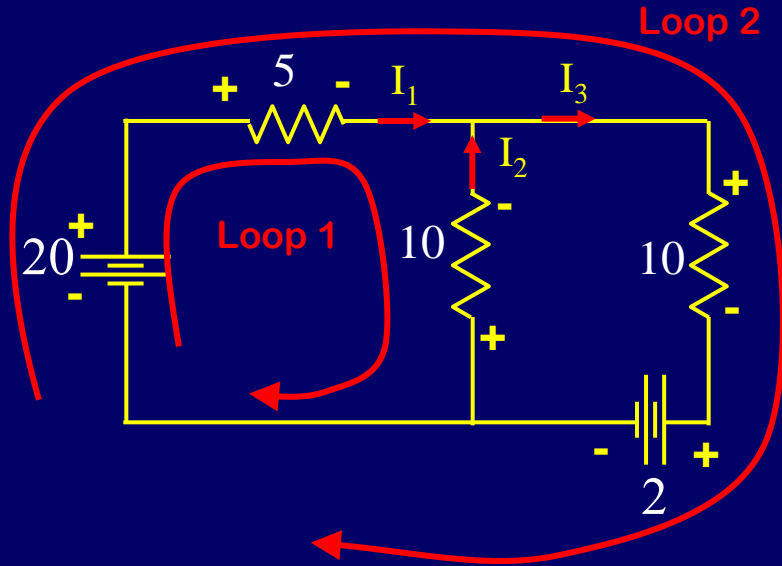In the circuit below you are given \mathcal{E}_1 , \mathcal{E}_2 , R_1 , R_2 and R_3 . Find I_1 , I_2 and I_3 .



1. Loop 1: $20 - 5I_1 + 10I_2 = 0$
2. Loop 2: $20 - 5I_1 - 10I_3 - 2 = 0$
3. Junction: $I_3 = I_1 + I_2$

solution: substitute Eq.3 for I_3 in Eq. 2:

$$20 - 5I_1 - 10(I_1 + I_2) - 2 = 0$$

rearrange: $15I_1 + 10I_2 = 18$

rearrange Eq. 1: $5I_1 - 10I_2 = 20$

Now we have 2 eq., 2 unknowns. Continue on next slide

$$15I_1 + 10I_2 = 18$$
$$5I_1 - 10I_2 = 20$$

Now we have 2 eq., 2 unknowns.

Add the equations together:

$$20I_1 = 38 \quad I_1 = 1.90 \text{ A}$$

Plug into bottom equation:

$$5(1.90) - 10I_2 = 20 \quad I_2 = -1.05 \text{ A}$$

note that this means direction of I_2 is opposite to that shown on the previous slide


Use junction equation (eq. 3 from previous page)

$$I_3 = I_1 + I_2 = 1.90 - 1.05$$

$$I_3 = 0.85 \text{ A}$$

We are done!

Back to where we started...

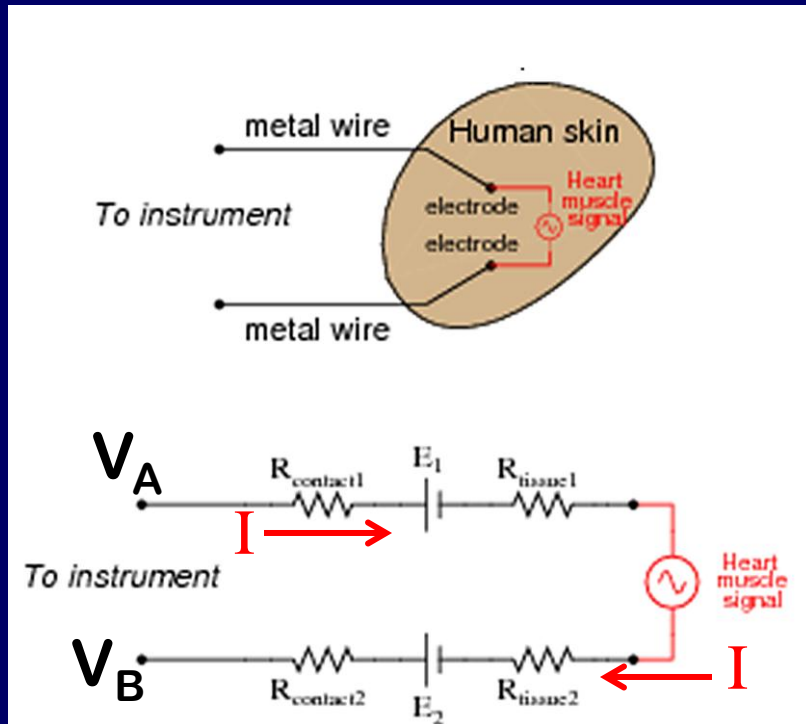

$$V_{EKG} = V_A - V_B$$

$$V_A - IR_{c1} - \epsilon_1 - IR_{t1} + V_{sig} - IR_{t2} + \epsilon_2 - IR_{c2} = V_B$$

$$V_A - V_B = IR_{c1} + \epsilon_1 + IR_{t1} - V_{sig} + IR_{t2} - \epsilon_2 + IR_{c2}$$

Surface potentials tend to cancel!