
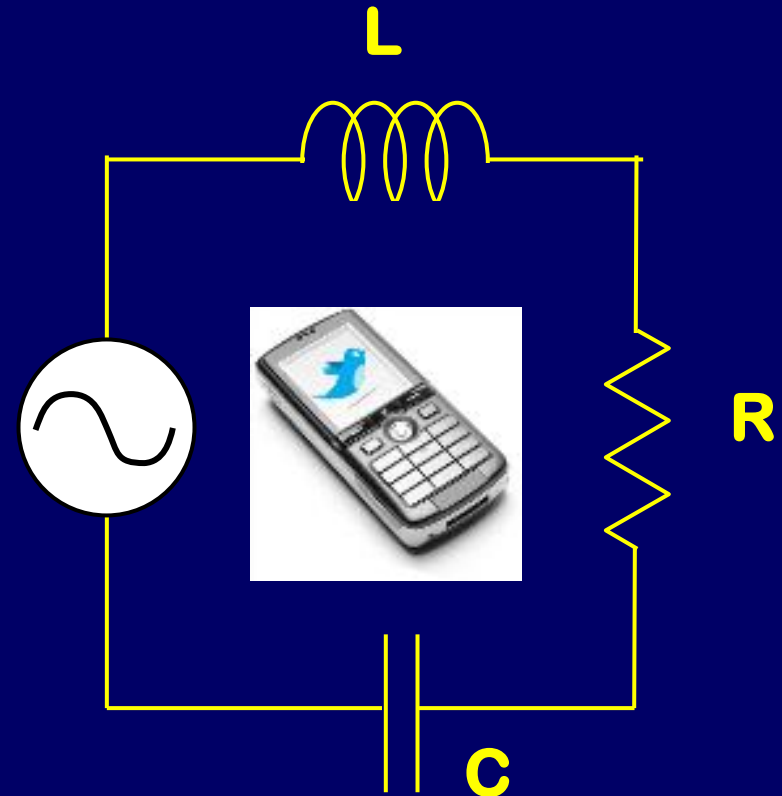


Physics 102: Lecture 12



AC & RLC Circuits

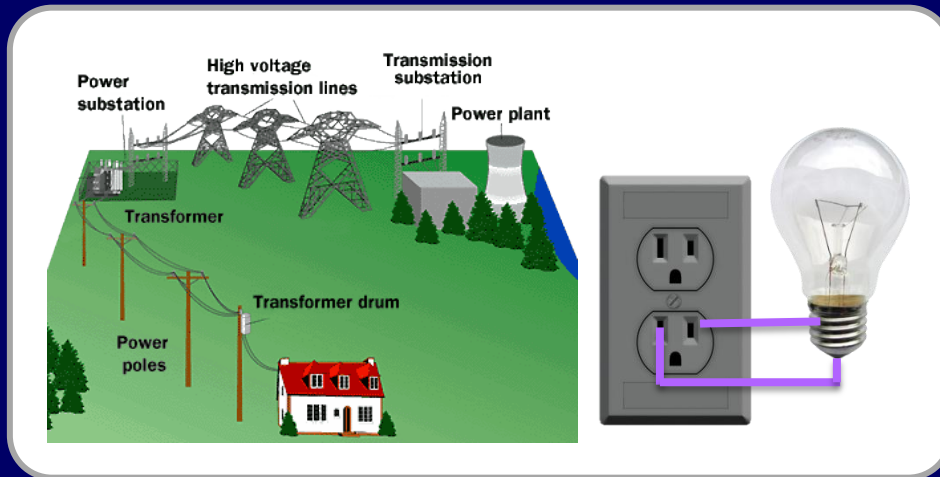

DC vs. AC circuits

DC




Direct Current

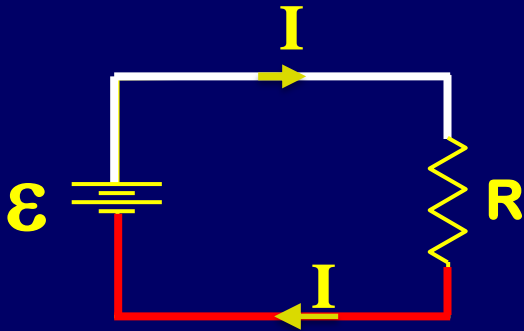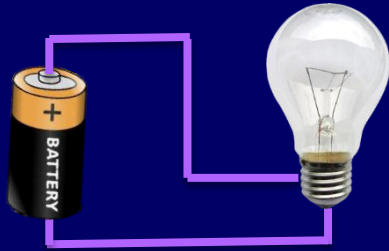

**Direction
of current is fixed**


AC

Alternating Current

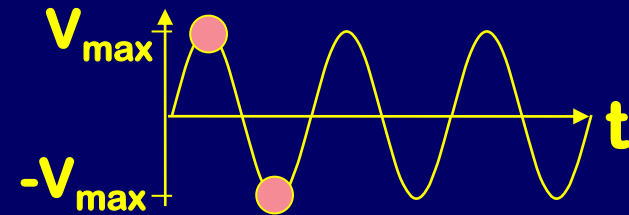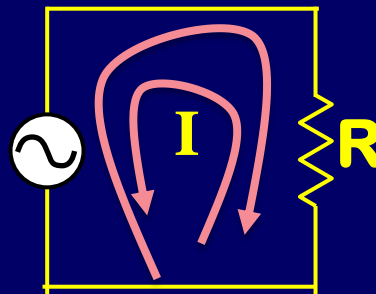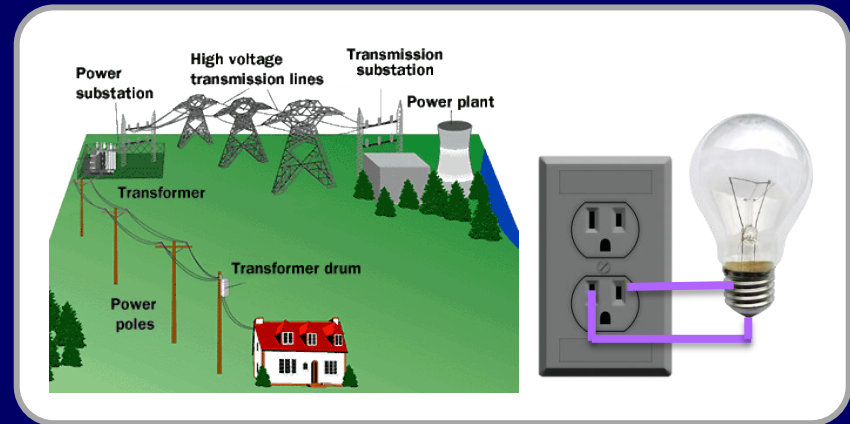

**Direction of current
alternates!**

Review: Generators and EMF

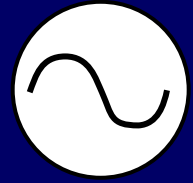


Voltage across generator:

$$\varepsilon = \omega A B \sin(\theta)$$


$$\varepsilon = \omega A B \sin(\omega t)$$
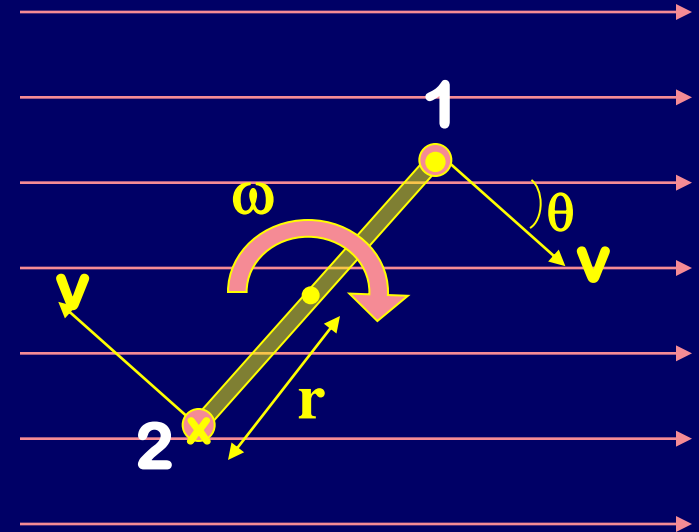
$$\varepsilon = V_{\max} \sin(\omega t)$$




Frequency = How fast its spinning

Amplitude = Maximum voltage

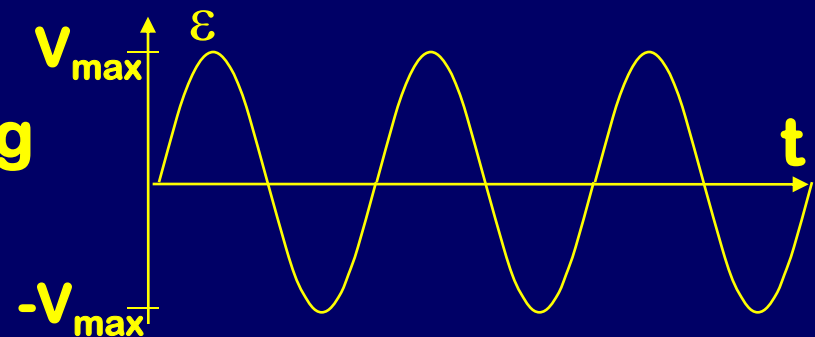

Example

AC Source

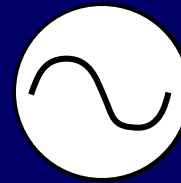

$$V(t) = V_{\max} \sin(\omega t) = V_{\max} \sin(2\pi f t)$$

V_{\max} = maximum voltage


f = frequency (cycles/second)

$$V(t) = 24 \sin(8\pi t)$$

$$2\pi f t =$$

$$f =$$



$$T = (\quad) \text{seconds/cycle}$$

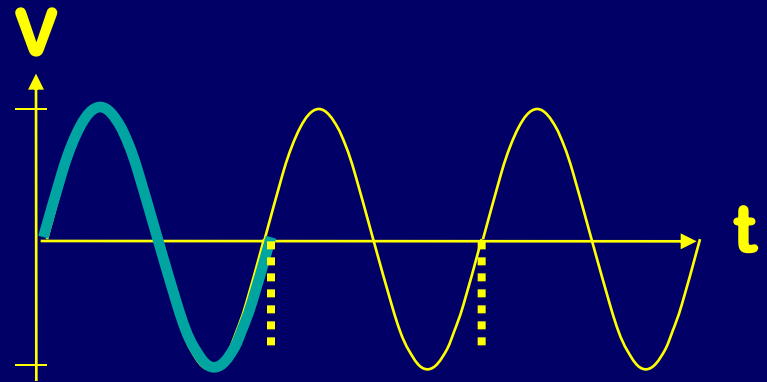


RMS: Root Mean Square

$$V_{\text{rms}} = V_{\max} / \sqrt{2}$$


RMS?

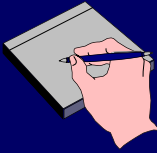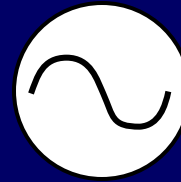

$$V(t) = V_{\max} \sin(2\pi f t)$$

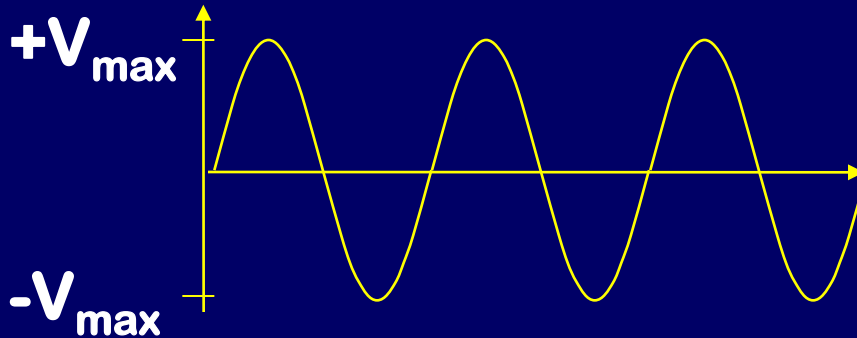

Square:

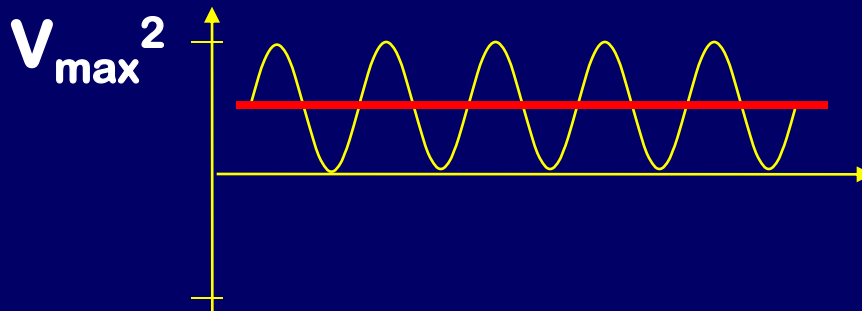

Mean:


$$V_{\max}^2 / 2$$

square Root: $V_{\max} / \sqrt{2}$

RMS: Root Mean Square $V_{\text{rms}} = V_{\max} / \sqrt{2}$

CheckPoint 2.1, 2.2
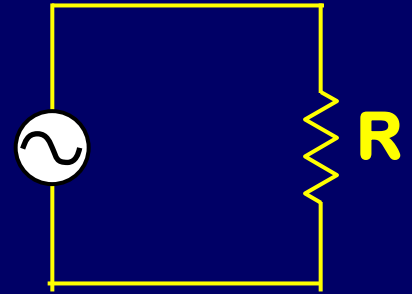
$$I(t) = \frac{V_{max}}{R} \sin(377t) = 10 \sin(377t)$$



Find I_{max}

Find I_{rms}

Average power dissipated: $P = I_{rms}V_{rms} = \frac{1}{2}I_{max}V_{max}$
(Only for an AC circuit with a resistor)



ACT: AC power dissipation

When your hair dryer is plugged in and running, it uses 1200 W of average power. If the rms voltage delivered by the wall outlet is 120 V, what is the rms current delivered to the hair dryer?




(A) 0.1 A

(B) 5 A

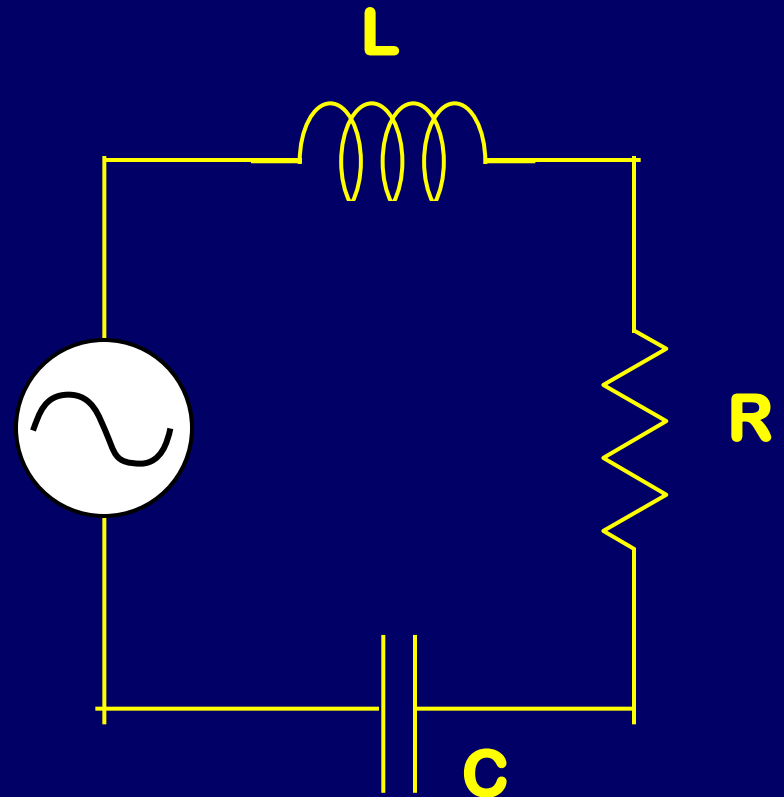(C) 10 A

Inductors

Inductors: a solenoid
used as a circuit element



**Inductors enable circuits to
have special properties...**

Self-Inductance

Recall from last time the solenoid cannon

- Changing current
- Changing B_{sol} field
- Changing Φ through itself!

– Φ proportional to I :

$$\Phi = LI$$

“Inductance”


- Induced EMF (voltage)

– Recall Faraday’s law:

- Direction


- Given by Lenz’s Law
- Opposes change in current!
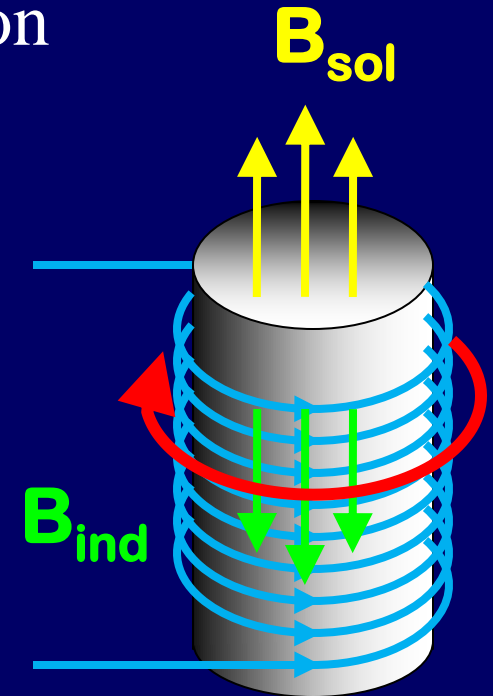
$$\varepsilon = -\frac{\Delta\Phi}{\Delta t} = -L \frac{\Delta I}{\Delta t} = -L \frac{I_f - I_i}{t_f - t_i}$$



Units: $L = \varepsilon t / I$
 $1 \text{ H} = 1 \text{ V-sec/amp}$

Physical Inductor

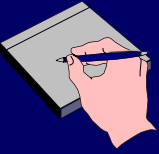


$$L \equiv \frac{\Phi}{I} \quad \text{Recall: } \Phi = NBA$$

$$L = \frac{NBA}{I} \quad \text{Recall: } B = \mu_0 n I$$

$$L = \frac{N \mu_0 n I A}{I}$$

$$L = N \mu_0 n A$$

$$L = \mu_0 n^2 l A$$

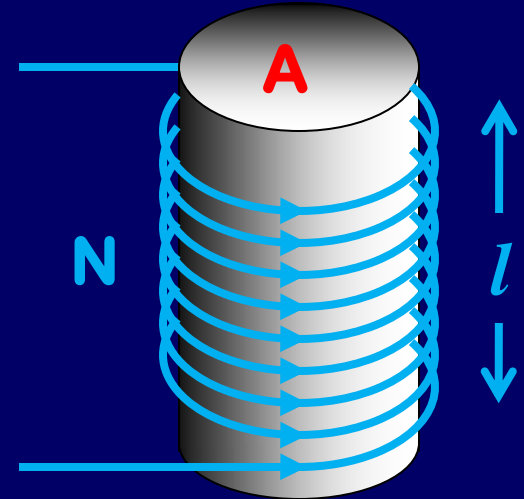

(# turns) = (# turns/meter) x (# meters)

$$N = n l$$

Energy stored:


$$U = \frac{1}{2} L I^2$$



ACT: Inductors

A $10\ \Omega$ resistor is wired in series with a $10\ \text{V}$ battery and a $1\ \text{H}$ inductor. What is the voltage across the inductor?

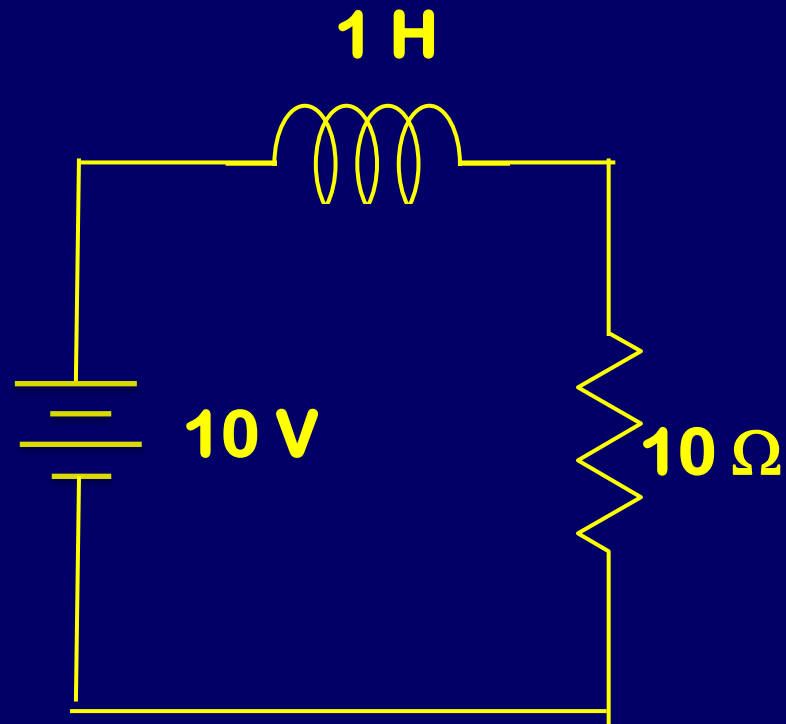- (A) $0\ \text{V}$ (B) $9\ \text{V}$ (C) $10\ \text{V}$




RLC circuits

A circuit with an inductor, resistor, and capacitor in series!

Used in:

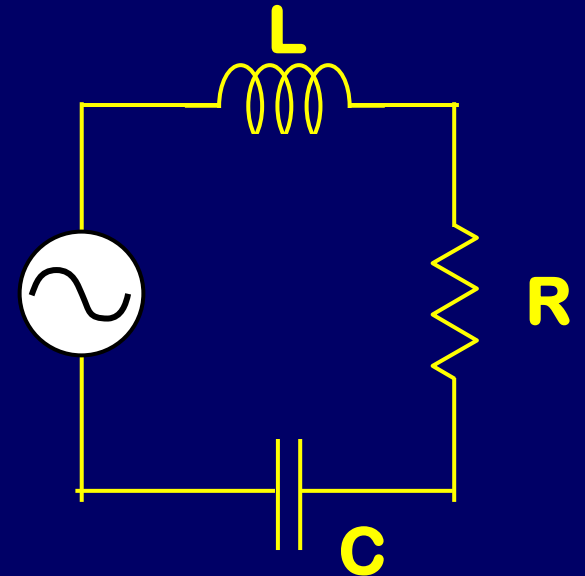- **Cell phones / radios**
- **Computers**
- **Watches / clocks**






First: Understand each element individually

Resistors in AC circuit



$V_R = I R$ always true – Ohm's Law

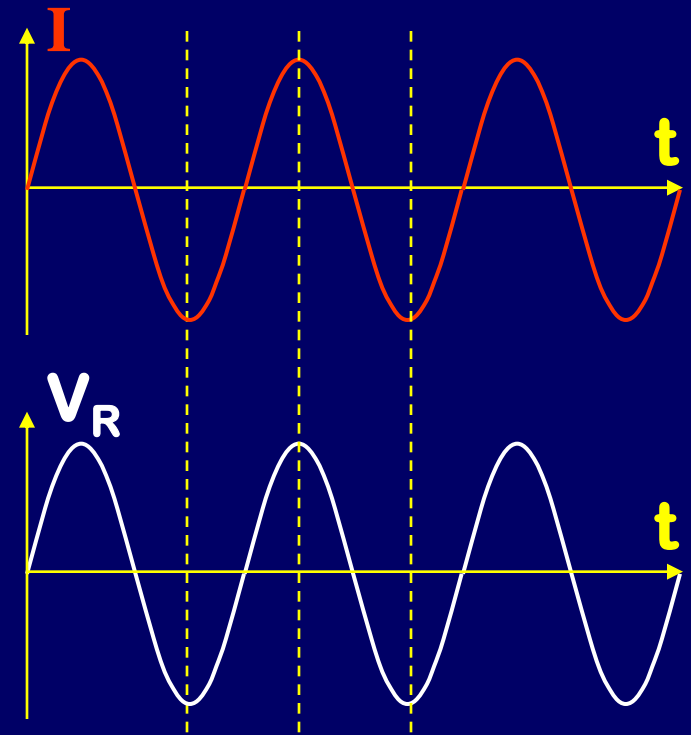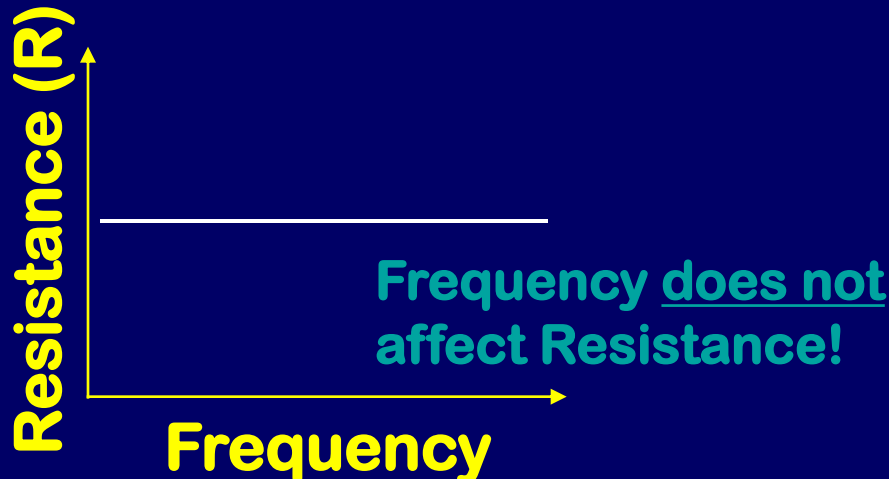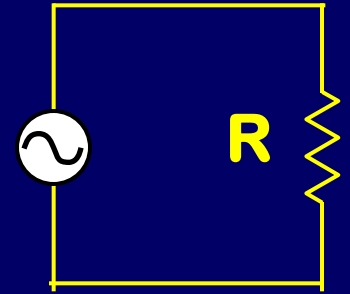- $V_{R,\max} = I_{\max} R$
- Voltage across resistor is “IN PHASE” with current.
 - V_R goes up and down at the same times as I does.




Capacitors in AC circuit





$$V_C = Q/C \text{ always true}$$

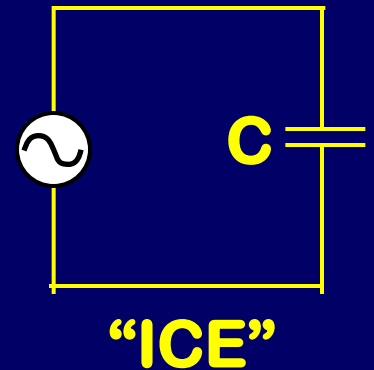- $V_{C,\max} = I_{\max} X_C$
- Capacitive Reactance: $X_C = 1/(2\pi fC)$
- Voltage across capacitor “LAGS” current.



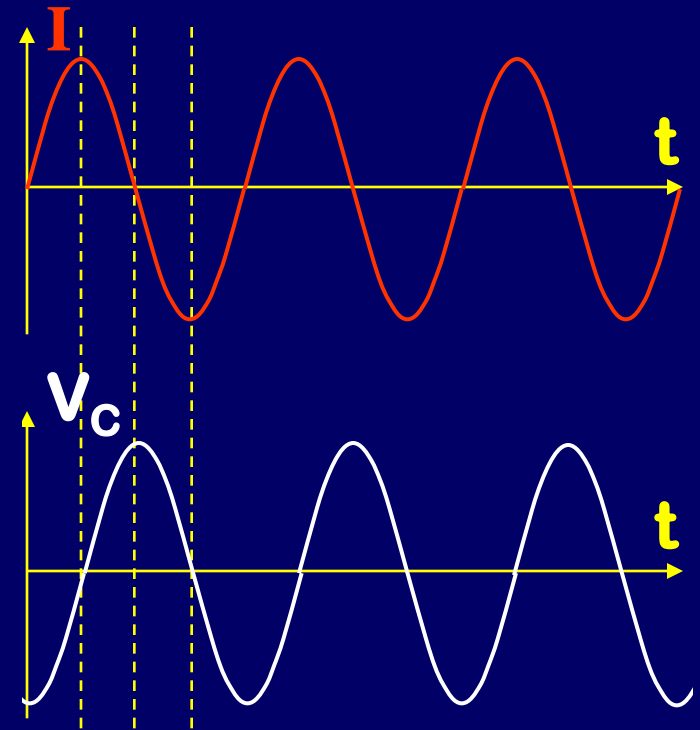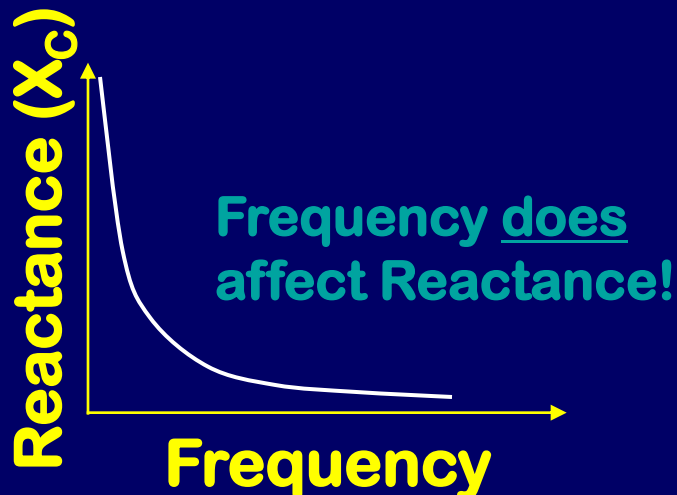- V_C goes up and down just after I does.




Inductors in AC circuit





$$V_L = +L(\Delta I)/(\Delta t) \text{ always true}$$

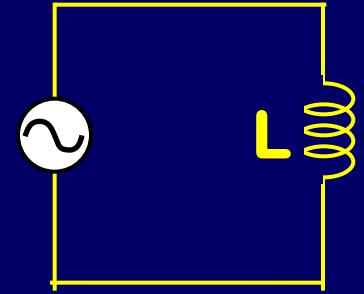- $V_{L,\max} = I_{\max} X_L$
- Inductive Reactance: $X_L = 2\pi fL$
- Voltage across inductor “LEADS” current.




“ELI”

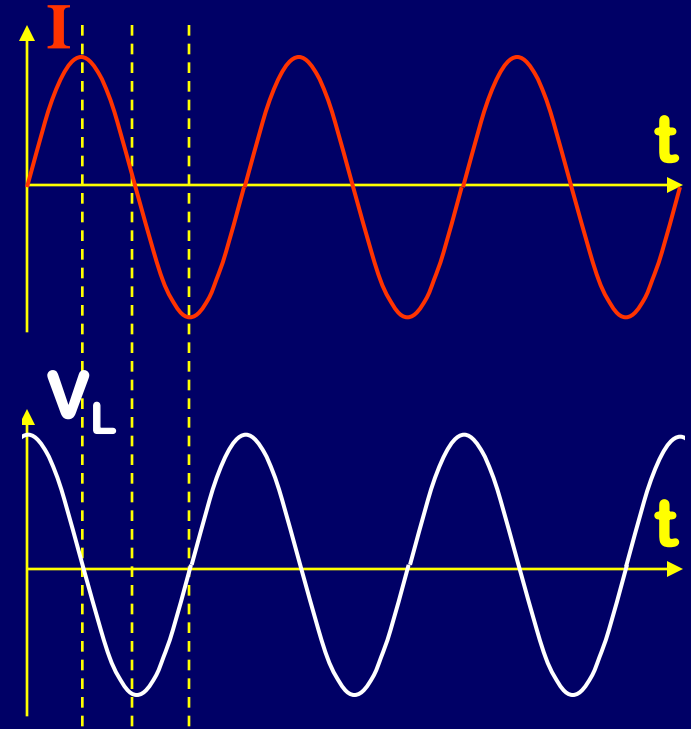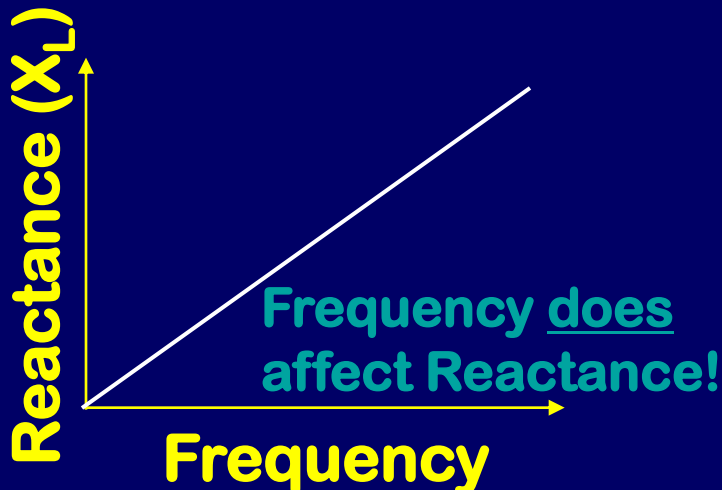- V_L goes up and down just before I does.





ACT/CheckPoints 3.1, 3.2

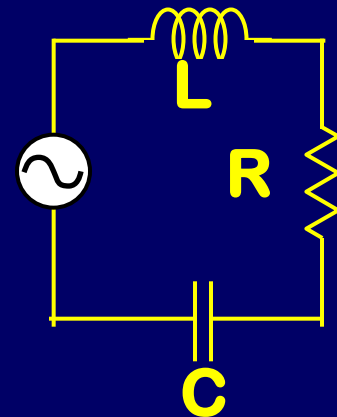

The **capacitor** can be ignored when...

- (a) frequency is very large
- (b) frequency is very small

The **inductor** can be ignored when...


- (a) frequency is very large
- (b) frequency is very small

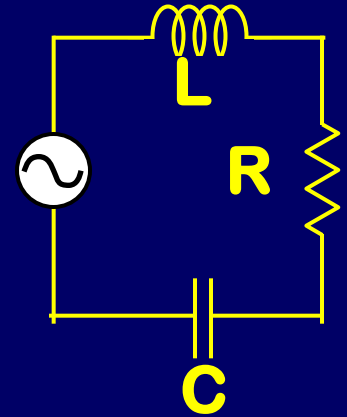Example



AC Circuit Voltages

An AC circuit with $R = 2 \Omega$, $C = 15 \text{ mF}$, and $L = 30 \text{ mH}$ has a current $I(t) = 0.5 \sin(8\pi t)$ amps. Calculate the maximum voltage across R , C , and L .



$$V_{R,\max} = I_{\max} R =$$

$$V_{C,\max} = I_{\max} X_C =$$

$$V_{L,\max} = I_{\max} X_L =$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{\omega C}$$


$$X_L = 2\pi f L = \omega L$$



ACT: AC Circuit Voltages



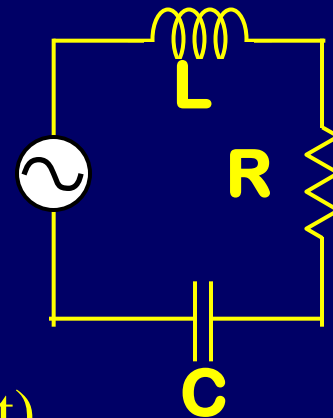An AC circuit with $R = 2\ \Omega$, $C = 15\ \text{mF}$, and $L = 30\ \text{mH}$ has a current $I(t) = 0.5 \sin(8\pi t)$ amps. Calculate the maximum voltage across R , C , and L .



Now the frequency is increased so $I(t) = 0.5 \sin(16\pi t)$. Which element's maximum voltage decreases?

- 1) $V_{R,\text{max}}$
- 2) $V_{C,\text{max}}$
- 3) $V_{L,\text{max}}$

Summary so far...

- $I = I_{\max} \sin(2\pi ft)$
- $V_R = I_{\max} R \sin(2\pi ft)$
 - V_R in phase with I
- $V_C = I_{\max} X_C \sin(2\pi ft - \pi/2)$
 - V_C lags I $X_C = \frac{1}{2\pi f C} = \frac{1}{\omega C}$

“ICE”

- $V_L = I_{\max} X_L \sin(2\pi ft + \pi/2)$
 - V_L leads I $X_L = 2\pi f L = \omega L$

“ELI”

