

Name: \_\_\_\_\_

DISC: \_\_\_\_\_


Score: \_\_\_\_ / 20

Instructions:

- Do your own work.
- Answer the questions below in the space provided.
- Make sure you show all your work and any equations that you use.
- Please place a box around your answers.
- Remember to give the correct units with all numerical answers

Q1	Q2	Q3	Q4
5	5	10	5

1. Consider the resistor network:

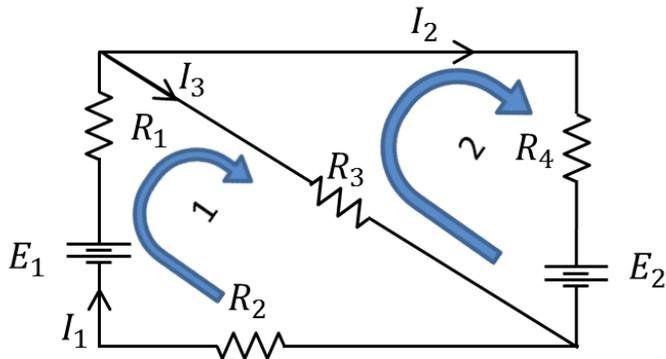

SERIES	$R_{eq} = R_1 + R_2$
PARALLEL	$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$
OHM'S LAW	$V = IR$
CONTINUITY OF CURRENT AT A JUNCTION	$I_3 = I_1 + I_2$
<b>Useful Information</b>	

a. The table contains the values for the resistors and batteries. Now let's use this information to find the current  $I_1$ :

$R_1$	$R_2$	$R_3$	$R_4$	$E_1$	$E_2$
20 $\Omega$	20 $\Omega$	10 $\Omega$	10 $\Omega$	40 V	20 V

Loop 1 (1 pts):  
 Loop 2 (1 pts):  
 $I_1$  (3 pts):

i. Write the loop rule for loop 1:

$$E_1 - I_1(R_1 + R_2) - I_3R_3 = 0$$

ii. Write the loop rule for loop 2:

$$I_3R_3 - I_2R_4 - E_2 = 0$$


iii. Using your loop rules above, solve for  $I_1$ :

$$I_1 = \frac{2}{3} A$$

(Use the attached scratch paper, but put you answer in the box above.)

See Work on Last Page


2. A simple RC circuit is shown below:

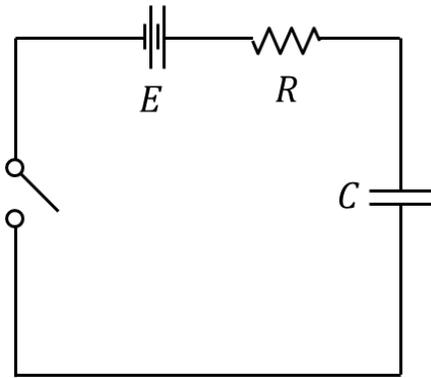

TIME CONSTANT	$\tau = RC$
$R$	$5 \Omega$
$C$	$3 \mu F$
$E$	$9 V$
CAPACITANCE	$C = Q/V$
$Q(t) = Q_0 \left(1 - e^{-\frac{t}{\tau}}\right)$	$Q(t) = Q_0 \left(e^{-\frac{t}{\tau}}\right)$
<b>Useful Information</b>	

- a. Initially the switch is open and the capacitor is uncharged. After the switch is closed, the capacitor starts charging. Sketch the current through the circuit as a function of time. Don't forget to correctly label your sketch.

Labels (1 pt):  
Form (1 pt):

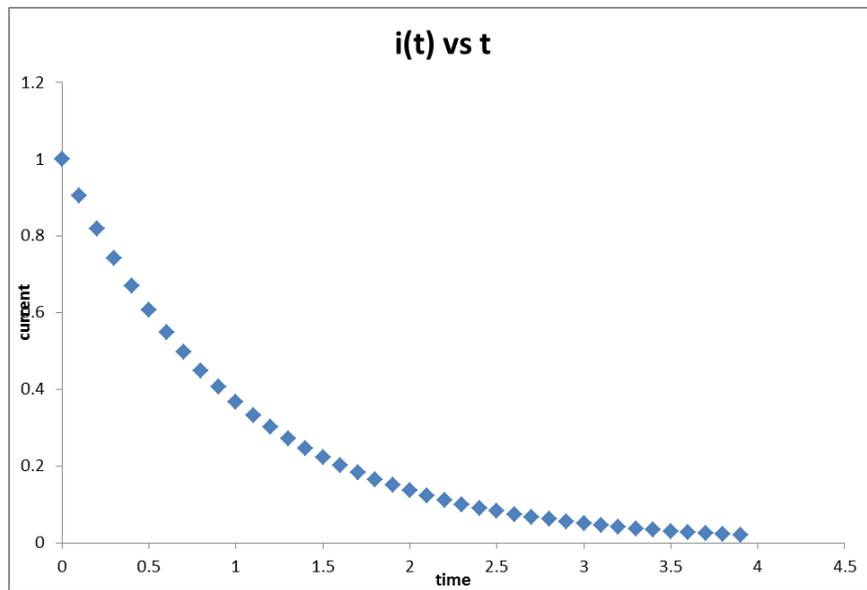


- b. After the capacitor is fully charged, what is the maximum charge  $Q$  the capacitor will achieve?

$$CV = Q = 3 \times 10^{-6} \times 9 = 27 \mu C$$

Set-up (1 pt):  
Algebra (1 pt):  
Charge (1 pt):

3. Consider the resistor network:

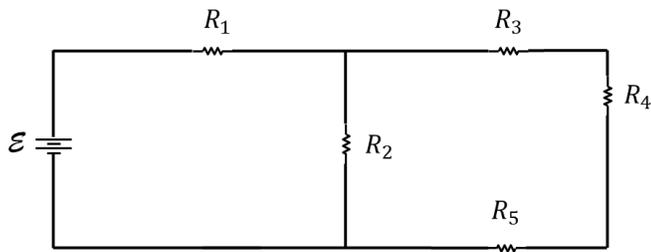

SERIES	$R_{eq} = R_1 + R_2$
PARALLEL	$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$
OHM'S LAW	$V = I R$
CONTINUITY OF CURRENT AT A JUNCTION	$I_3 = I_1 + I_2$
<b>Useful Information</b>	

a. Let all resistors have resistance  $R = 5 \Omega$  and  $\varepsilon = 6 V$ . Find the effective resistances requested and calculate the current flowing through each:

STEP	ACTION	RESULT	CURRENT
1	EFFECTIVE RESISTANCE $R_{345} = R_{eq1}$ :	<b>15 Ω</b>	<b>0.171 A</b>
2	EFFECTIVE RESISTANCE $R_{2345} = R_{eq2}$ :	<b>3.75 Ω</b>	<b>0.686 A</b>
3	EFFECTIVE RESISTANCE $R_{12345} = R_{eq3}$ :	<b>8.75 Ω</b>	<b>0.686 A</b>

b. For each step in the above table, draw the effective circuit:

Step 1:

$R_{eq1} = 3 \times 5 = 15 \Omega$   $V_{eq1} = 6 V - 5 \Omega \times 0.686 = 2.57 V$ ;  
 $I_1 = \frac{V_{eq1}}{R_{eq1}} = \frac{2.57 V}{15 \Omega} = 0.171 A$

Step 2:

$\frac{1}{R_{eq2}} = \frac{1}{15 \text{ Ohms}} + \frac{1}{5 \text{ Ohms}} = \frac{4}{15 \text{ Ohms}}$   $R_{eq2} = 3.75 \Omega$ ;  $I_2$  is the same as  $I_3$  because  $R_1$  is in series with  $\varepsilon$ .

Step 1 (2 pts):  
 Step 2 (1 pts):  
 Step 3 (1 pts):

Step 3:

$R_{eq3} = 5 + 3.75 = 8.75 \Omega$ ;  $I_3 = \frac{6 V}{8.75 \Omega} = 0.686 A$

This page intentionally left blank

**Kirchhoff's Loop Rules:**

$$E_1 - I_1(R_1 + R_2) - I_3R_3 = 0$$

$$I_3R_3 - I_2R_4 - E_2 = 0$$

**(0.5 pts.) Junction Rule for this network (OK if this is in a combined step as long as it is done correctly)**

$$I_1 = I_2 + I_3.$$

[Note: This is a variation of the version given in the "Useful Information" box above]

**(0.5 pts) Making some value substitutions (see table in problem 1):**

$$40 V - I_1(20 \Omega + 20 \Omega) - I_3(10 \Omega) = 0$$

$$I_3(10 \Omega) - I_2(10 \Omega) - 20 V = 0$$

**Simplify the arithmetic a little bit:**

$$40 V - I_1(40 \Omega) - I_3(10 \Omega) = 0$$

$$I_3(10 \Omega) - I_2(10 \Omega) - 20 V = 0$$

**(1 pt) I will now use the junction rule to eliminate  $I_2$ :  $I_2 = I_1 - I_3$  (Full point for any other correct substitution, substituted correctly)**

$$40 V - I_1(40 \Omega) - I_3(10 \Omega) = 0$$

$$I_3(10 \Omega) - (I_1 - I_3)(10 \Omega) - 20 V = 0$$

**Simplify again:**

$$40 V - I_1(40 \Omega) - I_3(10 \Omega) = 0$$

$$I_3(20 \Omega) - I_1(10 \Omega) - 20 V = 0$$

**And reorganize terms:**

$$-I_1(40 \Omega) - I_3(10 \Omega) = -40 V$$

$$-I_1(10 \Omega) + I_3(20 \Omega) = 20 V$$

**(1 pt) I'm now going to multiply the top equation by 2 and add the two equations to each other to eliminate  $I_3$ : (or any other acceptable technique, done correctly, for 2 equations and 2 unknowns)**

$$-I_1(80 \Omega) - I_3(20 \Omega) = -80 V$$

$$(+)\quad -I_1(10 \Omega) + I_3(20 \Omega) = 20 V$$

$$\hline -I_1(90 \Omega) = -60 V$$

**So we finish the arithmetic and find that  $I_1 = \frac{2}{3} A$**