

Name: _____

DISC: _____


Score: ____ / 20

Instructions:

- Do your own work.
- Answer the questions below in the space provided.
- Make sure you show all your work and any equations that you use.
- Please place a box around your answers.
- Remember to give the correct units with all numerical answers

Q1	Q2	Q3	Q4
5	5	10	5

1. Consider the resistor network:

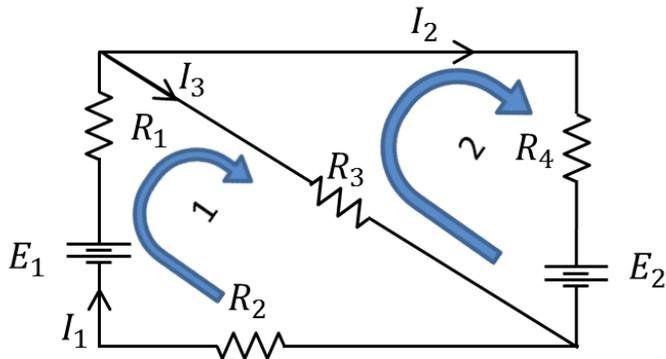

SERIES	$R_{eq} = R_1 + R_2$
PARALLEL	$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$
OHM'S LAW	$V = I R$
CONTINUITY OF CURRENT AT A JUNCTION	$I_3 = I_1 + I_2$
Useful Information	

a. The table contains the values for the resistors and batteries. Now let's use this information to find the current I_1 :

R_1	R_2	R_3	R_4	E_1	E_2
30 Ω	30 Ω	20 Ω	20 Ω	50 V	30 V

Loop 1 (1 pts):
 Loop 2 (1 pts):
 I_1 (3 pts):


i. Write the loop rule for loop 1:

ii. Write the loop rule for loop 2:

iii. Using your loop rules above, solve for I_1 :

(Use the attached scratch paper, but put your answer in the box above.)

2. A simple RC circuit is shown below:

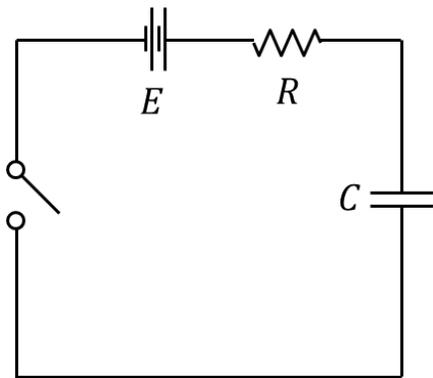

TIME CONSTANT	$\tau = RC$
R	9Ω
C	$7 \mu F$
E	$13 V$
CAPACITANCE	$C = Q/V$
$Q(t) = Q_0 \left(1 - e^{-\frac{t}{\tau}}\right)$	$Q(t) = Q_0 \left(e^{-\frac{t}{\tau}}\right)$
Useful Information	


- a. Initially the switch is open and the capacitor is uncharged. After the switch is closed, the capacitor starts charging. Sketch the current through the circuit as a function of time. Don't forget to correctly label your sketch.

Labels (1 pt):
Form (1 pt):

- b. After the capacitor is fully charged, what is the maximum charge Q the capacitor will achieve?

Set-up (1 pt):
Algebra (1 pt):
Charge (1 pt):

3. Consider the resistor network:

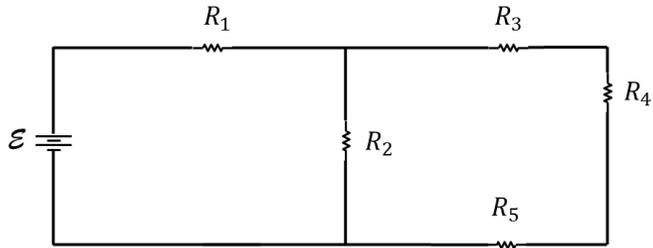

SERIES	$R_{eq} = R_1 + R_2$
PARALLEL	$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$
OHM'S LAW	$V = I R$
CONTINUITY OF CURRENT AT A JUNCTION	$I_3 = I_1 + I_2$
Useful Information	

a. Let all resistors have resistance $R = 9 \Omega$ and $\varepsilon = 10 V$. Find the effective resistances requested and calculate the current flowing through each:

Table (6 pts):

STEP	ACTION	RESULT	CURRENT
1	EFFECTIVE RESISTANCE $R_{345} = R_{eq1}$:		
2	EFFECTIVE RESISTANCE $R_{2345} = R_{eq2}$:		
3	EFFECTIVE RESISTANCE $R_{12345} = R_{eq3}$:		

b. For each step in the above table, draw the effective circuit:

Step 1:

Step 2:

Step 3:

Step 1 (2 pts):
 Step 2 (1 pts):
 Step 3 (1 pts):

This page intentionally left blank