

# Week 3 Solutions


## 1. Equivalent Resistance ... and fun with topology

All resistors have the same resistance  $R = 3\ \Omega$ .

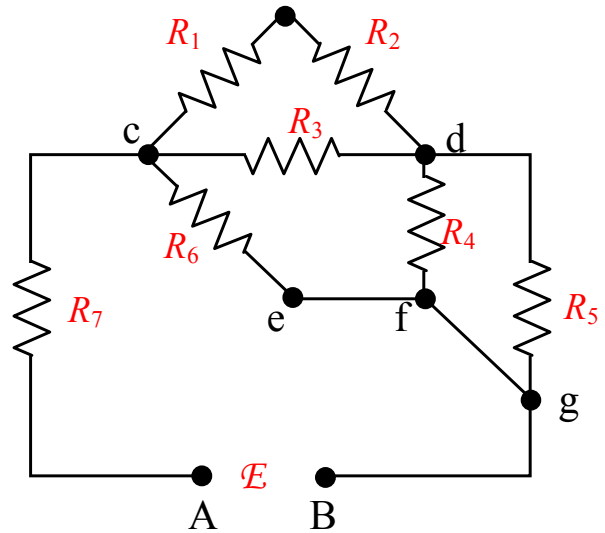- a) Simplify this resistor network and then compute the equivalent resistance between points A and B.

See my labels for the resistors.

- $R_1$  and  $R_2$  are in series, so  $R_{12} = 2R$ .
- $R_3$  and  $R_{12}$  are in parallel, so  $R_{123} = 2R/3$ .
- $R_4$  and  $R_5$  are in parallel, so  $R_{45} = R/2$ .
- $R_{45}$  and  $R_6$  are in series, so  $R_{456} = 3R/2$ .
- $R_{123}$  and  $R_{456}$  are in series, so  $R_{123456} = 7R/6$ .
- $R_{123456}$  and  $R_7$  are in parallel, so  $R_{1234567} = 7R/13$ .
- $R_{1234567}$  is in series with  $R_7$ , so  $R_{eq} = 20R/13 = 4.615\ \Omega$ .



- b) Suppose a 15 V power supply was connected between A and B. What power would be dissipated in this network of resistors?

$$\mathcal{E} = IR_{eq}, \text{ so } I = \mathcal{E}/R_{eq} = (15\text{ V})/(4.615\ \Omega) = 3.25\text{ A}.$$

$$\text{The power is voltage times current: } P = \mathcal{E}I = \mathcal{E}^2/R_{eq} = 48.8\text{ W}.$$

- c) What is the potential difference between points c and g, i.e.,  $V_c - V_g$ ?

You don't need to worry about  $R_1$  through  $R_6$ .

$$V_{cg} = \mathcal{E} - IR_7 \text{ (} IR_7 \text{ is the voltage drop across } R_7 \text{)} = 15\text{ V} - (3.25\text{ A}) \cdot (3\ \Omega) = 5.25\text{ V}$$

- d) If these resistors were all identical light bulbs, which one would be brightest? Which one would be the least bright?


All the current flows through  $R_7$ . All of the other resistors have other resistors in parallel, so none of them carry all the current. Therefore bulb #7 will be the brightest.

The dimmest is more complicated: (B is brightness)

- $B_1 = B_2 < B_3$  ( $R_1$  and  $R_2$  in series, and  $R_{12} > R_3$ .)
- $B_4 = B_5 < B_3$  and  $> B_1$ . ( $R_{45}$  in series with  $R_{123}$ .  $R_4$  and  $R_5$  each get half the current,  $R_3$  gets more than half, and  $R_1$  and  $R_2$  each get less than half.)
- $B_6 >$  any of  $B_1 - B_5$ , because  $V_6$  is the entire voltage across that part of the network. So, bulbs #1 and #2 are the dimmest.

# Week 3 Solutions

## 2: Kirchhoff Double Loop Problem

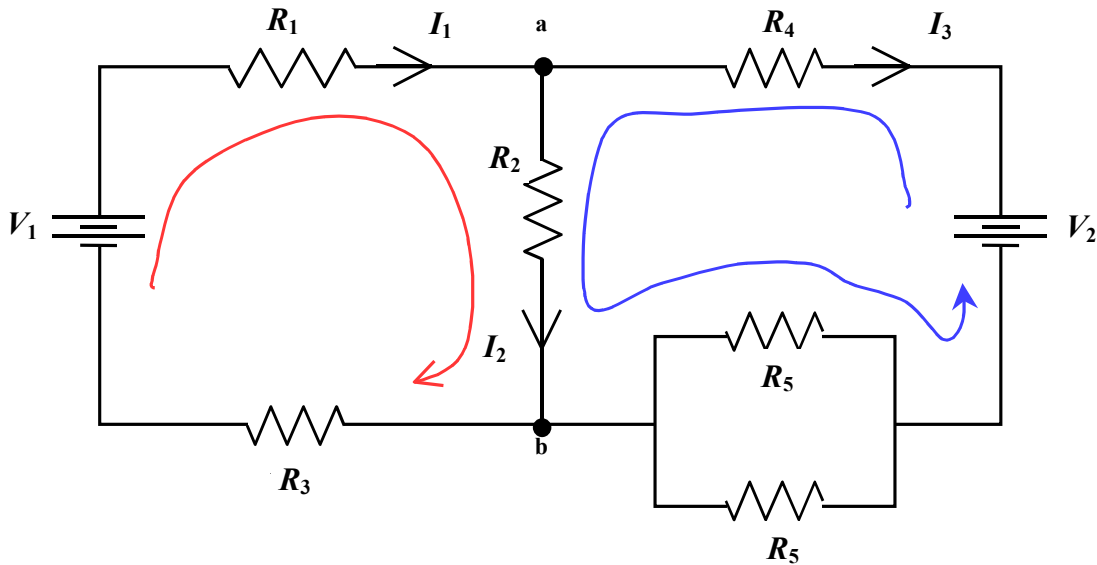

- a) Write down the junction rule for the currents that meet at **b**.

$I_1$  flows out of **b**;  $I_2$  and  $I_3$  flow in. The current out must equal the current in, so  $I_1 = I_2 + I_3$ .

- b) Write an algebraic expression for the Loop Rule for the **red** (left) loop.

The sum of the voltage changes around a loop must be zero. That's conservation of energy. So (starting at **b** and going clockwise):  $-I_1 R_3 + V_1 - I_1 R_1 - I_2 R_2 = 0$

- c) Now do the same for the **blue** (right) loop. First simplify the resistance of the two  $R_5$  resistors into an equivalent resistance. Be careful of which way the "positive" current goes here through the resistors and the battery.


As suggested by the blue arrow, start at **b** and go counterclockwise. It actually doesn't matter which way you go. Reversing direction just puts a minus sign on every term, and it cancels out.  $+I_3(R_5/2) + V_2 + I_3 R_4 - I_2 R_2 = 0$  The  $I_3 R$  terms are positive, because we are "swimming upstream" (against the current).  $V_2$  doesn't depend on the direction of current flow.

If you are now given the values of  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ ,  $R_5$ ,  $V_1$ , and  $V_2$ , you are left with three equations for three unknown currents. You could now solve for each current  $I_1$ ,  $I_2$  and  $I_3$ . (You do not need to solve for the currents in this problem.)

# Week 3 Solutions
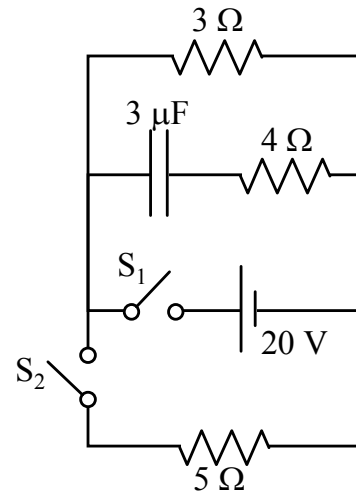
## 3. Circuit with resistors and capacitance

Initially,  $S_1$  and  $S_2$  are open, and the capacitor is discharged.



- a) At time  $t_0$ , switch  $S_1$  is closed (while  $S_2$  remains open).  
 What is the current drawn from the battery at the instant  $t_0$ ?  
 The capacitor is discharged, so there is no voltage across it. Therefore, the  $3\ \Omega$  and  $4\ \Omega$  resistors each have  $20\ \text{V}$  across them, because each is connected between the battery's terminals. The  $5\ \Omega$  resistor does not participate.  
 Therefore,  $I_{\text{batt}} = I_3 + I_4 = (20\ \text{V})/(3\ \Omega) + (20\ \text{V})/(4\ \Omega) = 6.67\ \text{A} + 5\ \text{A} = 11.67\ \text{A}$ .
- b) What is the current through the battery a long time later?  
 After the capacitor charges up, no current flows through it. Therefore,  $I_{\text{batt}} = I_3 = 6.67\ \text{A}$ .
- c) How much energy is stored on the capacitor a long time after the switch is closed?  
 No current means no voltage change across the resistor. Therefore,  $V_{\text{cap}} = 20\ \text{V}$ .  
 The energy stored in a capacitor is  $U = \frac{1}{2}CV^2 = 0.5(3 \times 10^{-6}\ \text{F})(20\ \text{V})^2 = 6 \times 10^{-4}\ \text{J}$ .
- d) Would your answer to c) change if the  $3\ \Omega$  resistor at the top of the circuit were removed? Explain.  
 No. The calculation in c) does not depend on anything having to do with the  $3\ \Omega$  resistor.
- e) Now  $S_1$  is opened and  $S_2$  is closed at exactly the same instant. How much current goes through the  $4\ \Omega$  resistor immediately after this event?  
 The battery is disconnected, but the capacitor is charged up and, for a short time, acts like a  $20\ \text{V}$  battery. To find the total current calculate the equivalent resistance:  
 $R_3$  and  $R_5$  are in parallel:  $R_{35} = 15/8\ \Omega$ .  $R_{35}$  is in series with  $R_4$ , so  $R_{\text{eq}} = 5.875\ \Omega$ .  
 $I_{\text{tot}} = (20\ \text{V})/(5.875\ \Omega) = 3.40\ \text{A}$ . That's  $I_4$ , because all the current flows through  $R_4$ .
- f) Which direction does the current go through the  $4\ \Omega$  resistor, to the left or to the right?  
 The left side of the capacitor is the positive side, because it was charged up by the battery. Therefore current flows from left to right through the resistor.
- g) How long does it take for the current to fall to  $1/e$  of the value you obtained in e)?  
 The time constant of the circuit is  $\tau = R_{\text{eq}}C = (5.875\ \Omega)(3 \times 10^{-6}\ \text{F}) = 1.76 \times 10^{-5}\ \text{s}$ .  
 It takes one time constant to fall to  $1/e$ , so  $t = \tau$ .