

Physics 212

Lecture 10

Today's Concept:

Kirchhoff's Rules

Your Comments

Your Comments

please go over the connecting a and b problem

current direction seems to arbitrary why does it sometimes come from the positive side of the battery and why does it sometimes go into the positive side

I like this new stuff so far :) please don't make me hate it...

I am really confused when there is a wire between a parallel circuit(CHECKPOINT 3), Can you explain?



Woah...how exactly did they pick where the current flows in two-loop circuits?

The objectification of batteries is all too real today. Physics Homework and tests portray what they claim to be the "ideal" battery by setting such unreasonable standards such as the "EMF". Its time to face the truth. Real batteries have resistance.

A homework assignment due after the midterm :(((((((((((((((((((((I guess bad planning on my part)

When will the test scores be posted? Any will the scores be scaled?

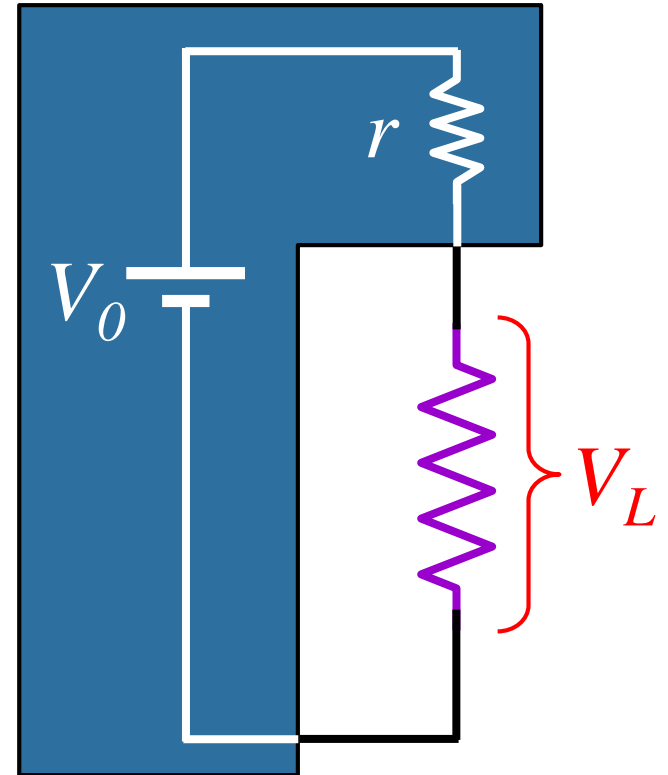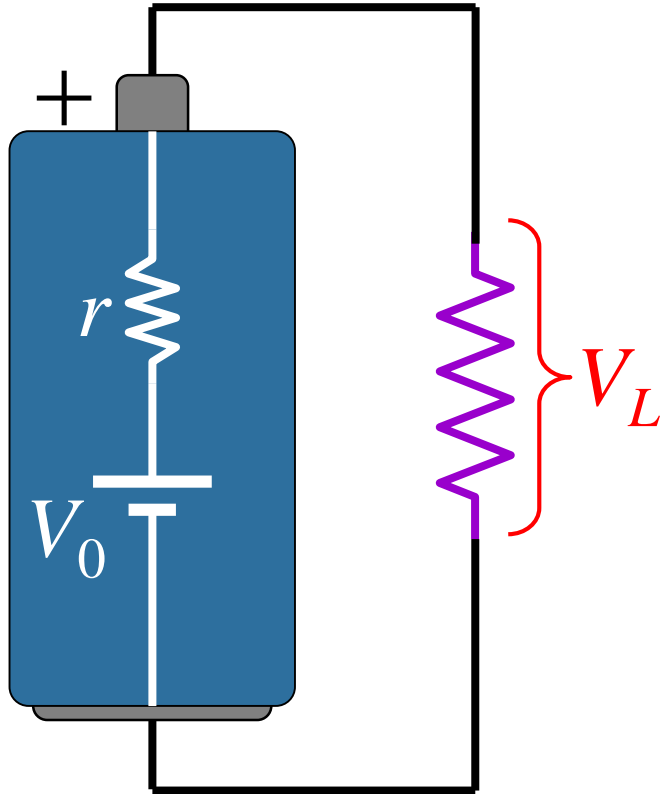Model for Real Battery: Internal Resistance



Usually can't supply too much current to the load
without voltage "sagging"

Last Time

Resistors in series:

Current through is same.

Voltage drop across is IR_i




$$R_{\text{effective}} = R_1 + R_2 + R_3 + \dots$$

Resistors in parallel:


Voltage drop across is same.

Current through is V/R_i

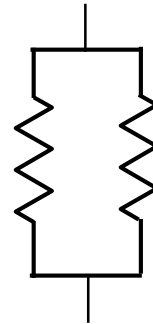


$$\frac{1}{R_{\text{effective}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$


Solved Circuits

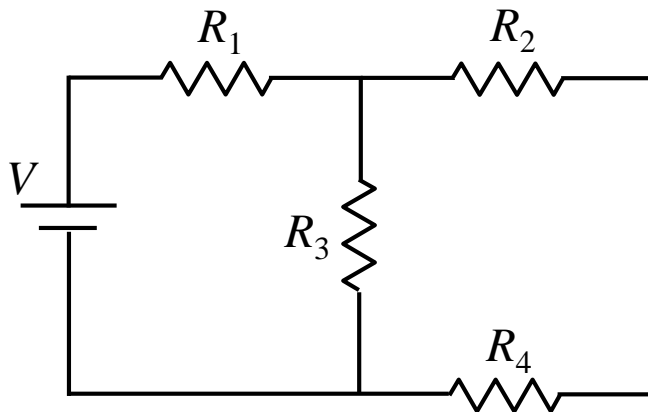


=

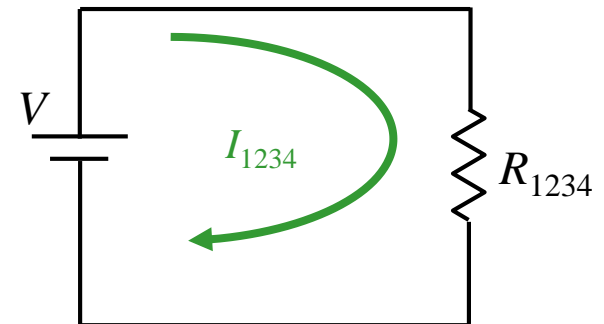

New Circuit

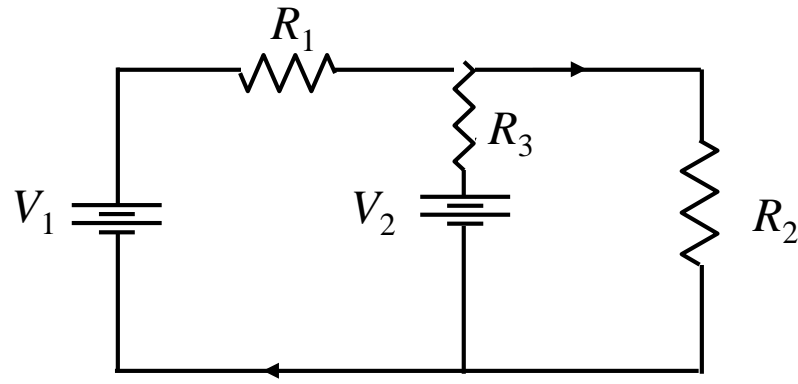

How Can We Solve This One?

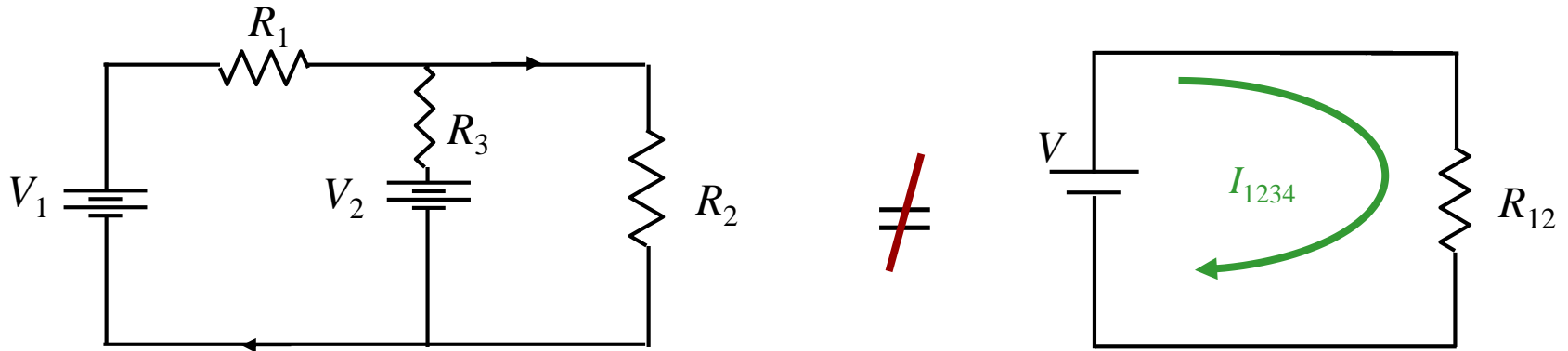

THE ANSWER: Kirchhoff's Rules

Kirchhoff's Voltage Rule

$$\sum \Delta V_i = 0$$

Kirchhoff's Voltage Rule states that the sum of the voltage changes caused by any elements (like wires, batteries, and resistors) around a circuit must be zero.

WHY?

The potential difference between a point and itself is zero!

Kirchhoff's Current Rule

$$\sum I_{in} = \sum I_{out}$$

Kirchhoff's Current Rule states that the sum of all currents entering any given point in a circuit must equal the sum of all currents leaving the same point.

WHY?

Electric Charge is Conserved

Applying Kirchhoff's Laws in 5 easy steps

1) Label all currents

Choose any direction

2) Label +/– for all elements

Current goes $+\Rightarrow -$ (for resistors)
Long side is + for battery

3) Choose loop and direction

Must start on wire, not element.

4) Write down voltage drops


First sign you hit is sign to use.

5) Write down node equation $I_{\text{in}} = I_{\text{out}}$

We'll do calculation today

It's actually the easiest thing to do!

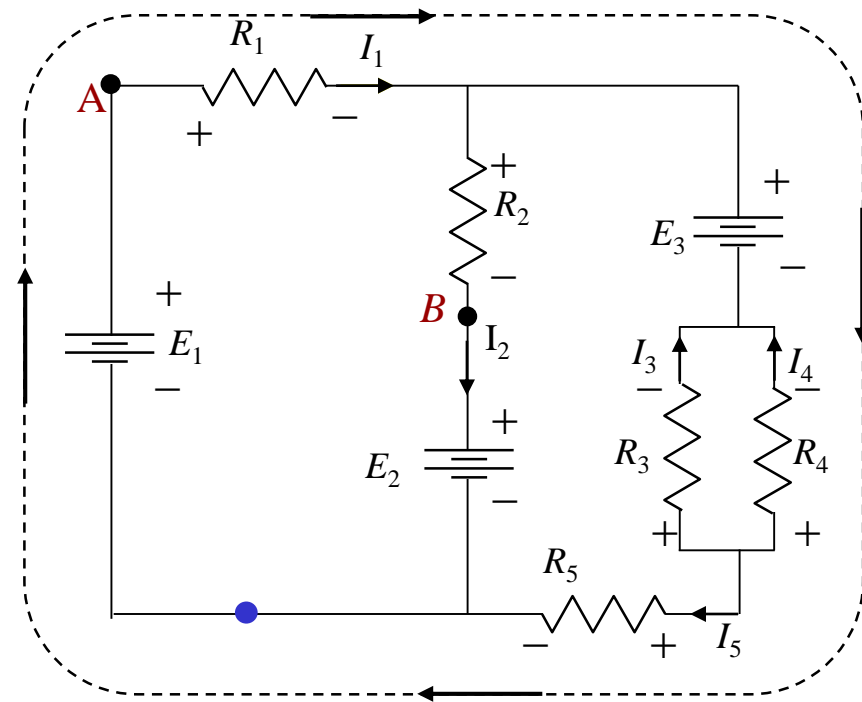
$$-E_1 + I_1 R_1 + E_3 - I_4 R_4 + I_5 R_5 = 0$$



Check Point 1



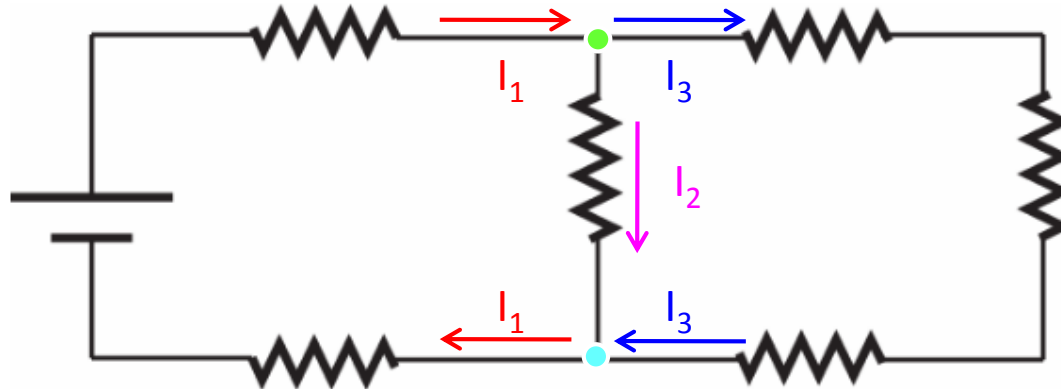How many potentially different currents are there in the circuit shown?



A. 3

B. 4

C. 5

D. 6

E. 7


Look at the nodes!

Top node: I_1 flows in, I_2 and I_3 flow out

Bottom node: I_2 and I_3 flow in, I_1 flows out


That's all of them!

Current Count: Question 1 (N = 733)

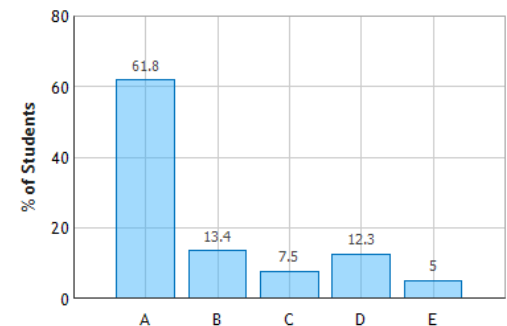

CheckPoint 2

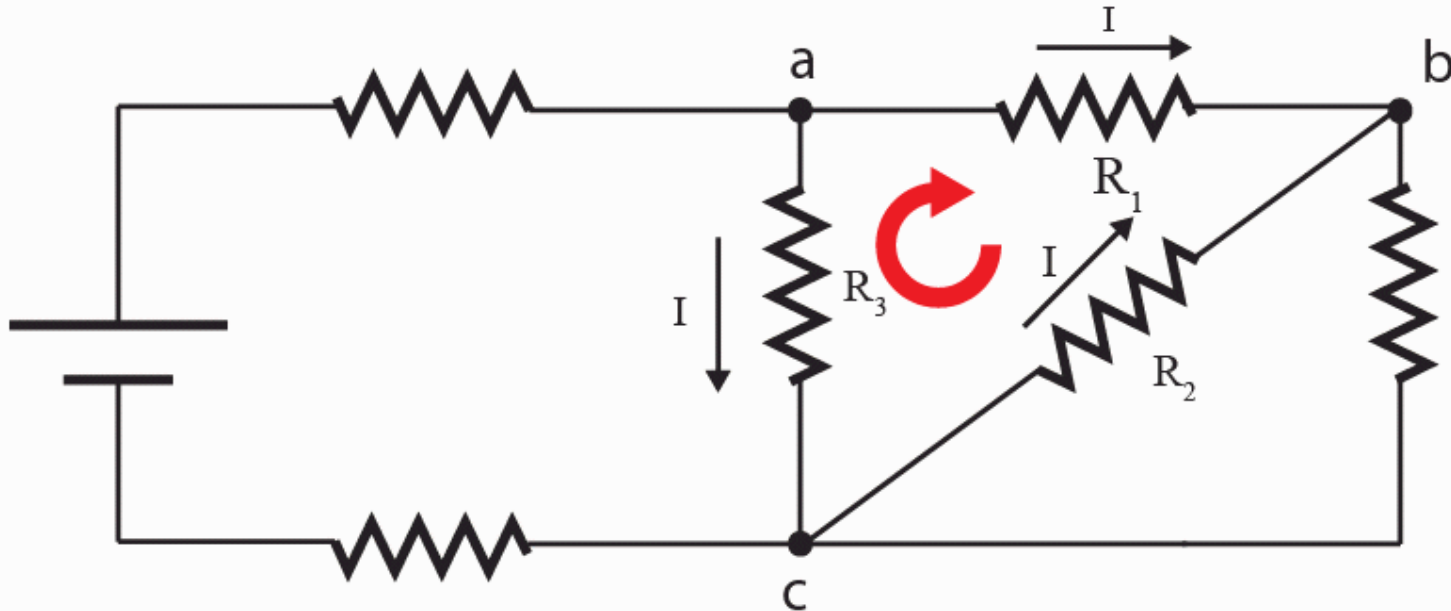In the following circuit, consider the loop abc. The direction of the current through each resistor is indicated by black arrows.



If we are to write Kirchhoff's voltage equation for this loop in the clockwise direction starting from point a , what is the correct order of voltage gains/drops that we will encounter for resistors R_1 , R_2 and R_3 ?

A. drop, drop, drop

B. gain, gain, gain

D. gain, drop, drop


E. drop, drop, gain

C. drop, gain, gain


With the current  VOLTAGE DROP

Against the current  VOLTAGE GAIN

Gains and Drops: Question 1 (N = 733)

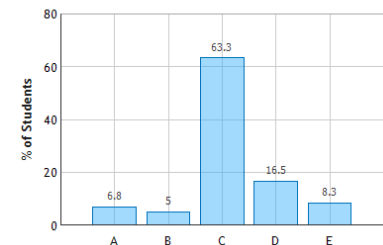

Calculation

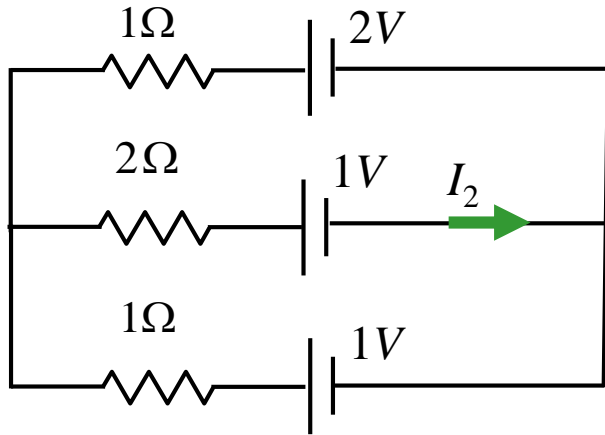

In this circuit, assume V_i and R_i are known.

What is I_2 ?


Conceptual Analysis:

- Circuit behavior described by Kirchhoff's Rules:
 - KVR: $\sum V_{drops} = 0$
 - KCR: $\sum I_{in} = \sum I_{out}$

Strategic Analysis

- Write down Loop Equations (KVR)
- Write down Node Equations (KCR)
- Solve

Calculation

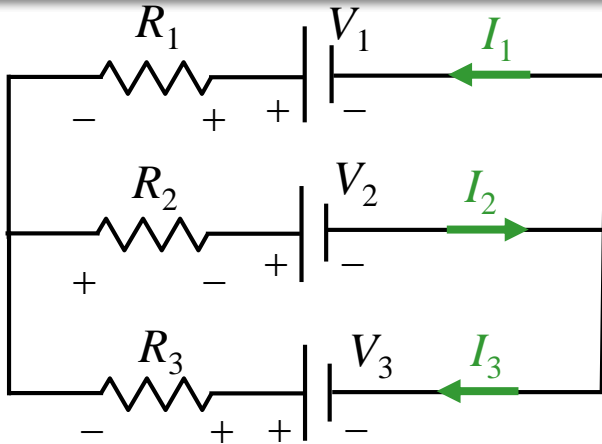

In this circuit, assume V_i and R_i are known.


What is I_2 ?

- 1) Label and pick directions for each current
- 2) Label the $+$ and $-$ side of each element

This is easy for batteries Long side is $+$


For resistors, the “upstream” side is $+$

Now write down loop and node equations

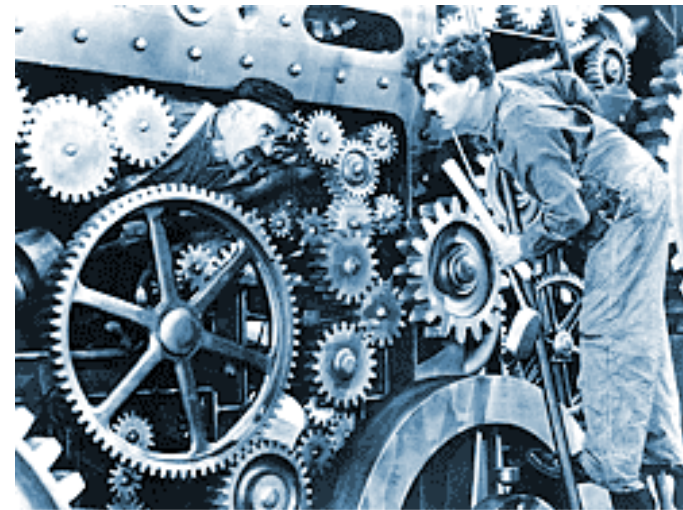

Just turn the crank.

Calculation

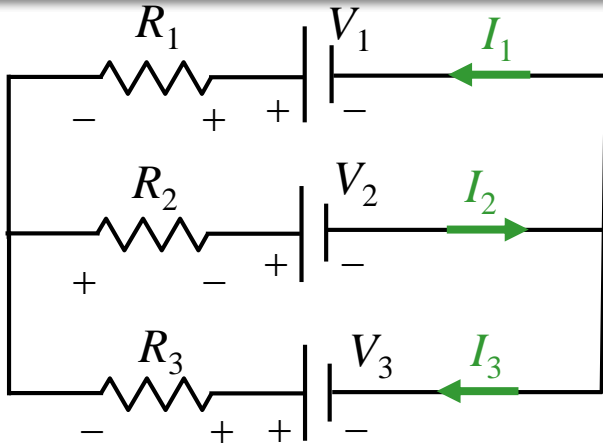

In this circuit, assume V_i and R_i are known.

What is I_2 ?

How many equations do we need to write down in order to solve for I_2 ?

A) 1

B) 2

C) 3

D) 4


E) 5

Why?

- We have 3 unknowns: I_1 , I_2 , and I_3
- We need 3 independent equations to solve for these unknowns

3) Choose Loops and Directions

Calculation

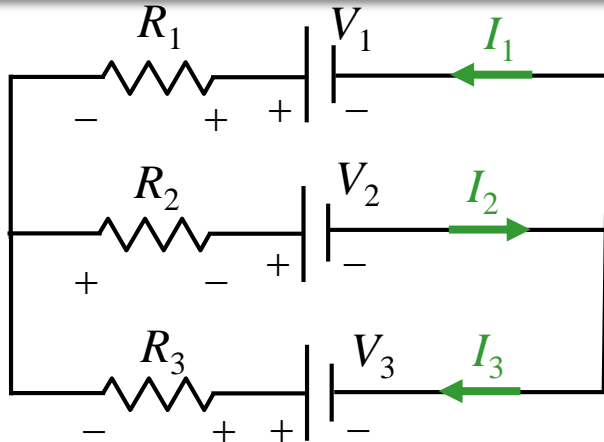

In this circuit, assume V_i and R_i are known.

What is I_2 ?

Which of the following equations is NOT correct?

- A) $I_2 = I_1 + I_3$
- B) $-V_1 + I_1 R_1 - I_3 R_3 + V_3 = 0$
- C) $-V_3 + I_3 R_3 + I_2 R_2 + V_2 = 0$
- D) $-V_2 - I_2 R_2 + I_1 R_1 + V_1 = 0$


4) Write down voltage drops

5) Write down node equation

Why?

- (D) is an attempt to write down *KVR* for the top loop
- Start at negative terminal of V_2 and go clockwise
 $V_{\text{gain}} (-V_2)$ then $V_{\text{gain}} (-I_2 R_2)$ then $V_{\text{gain}} (-I_1 R_1)$ then $V_{\text{drop}} (+V_1)$

Calculation

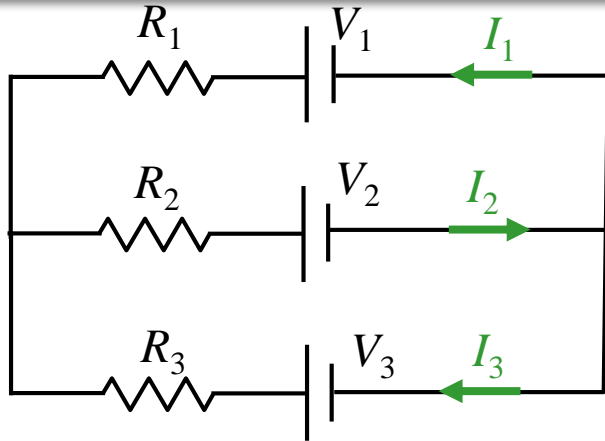

In this circuit, assume V_i and R_i are known.

What is I_2 ?

We need 3 equations:
Which 3 should we use?

1. $I_2 = I_1 + I_3$
2. $-V_1 + I_1 R_1 - I_3 R_3 + V_3 = 0$
3. $-V_3 + I_3 R_3 + I_2 R_2 + V_2 = 0$
4. $-V_2 - I_2 R_2 - I_1 R_1 + V_1 = 0$

Why?

- We need 3 INDEPENDENT equations
- Equations 2, 3, and 4 are NOT INDEPENDENT

$$\text{Eqn 2} + \text{Eqn 3} = -\text{Eqn 4}$$


- We must choose Equation 1 and any two of the remaining (2, 3, and 4)

A) Any 3 will do

B) 1, 2, and 4

C) 2, 3, and 4

Calculation

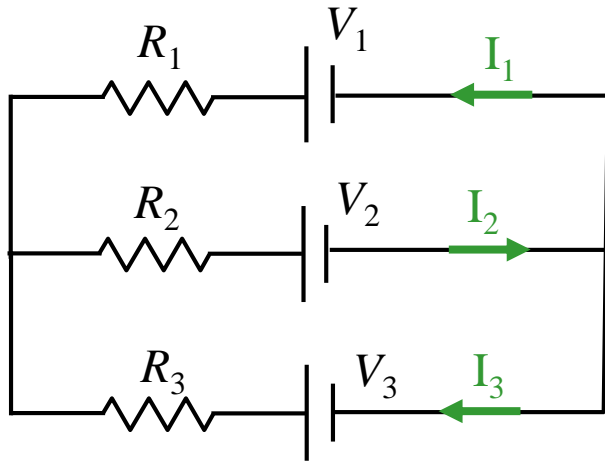

In this circuit, assume V_i and R_i are known.

What is I_2 ?

We have 3 equations and 3 unknowns.

$$I_2 = I_1 + I_3$$

$$V_1 + I_1 R_1 - I_3 R_3 + V_3 = 0$$

$$V_2 - I_2 R_2 - I_1 R_1 + V_1 = 0$$



Now just need to solve ☺


The solution will get very messy!

Simplify: assume $V_2 = V_3 = V$

$$V_1 = 2V$$

$$R_1 = R_3 = R$$


$$R_2 = 2R$$

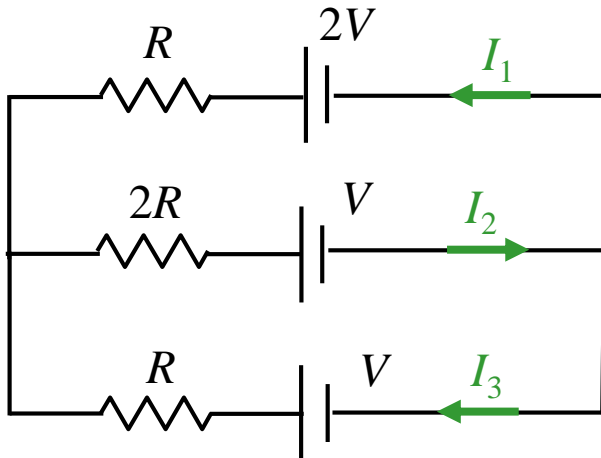

Calculation: Simplify

In this circuit, assume V and R are known.

What is I_2 ?

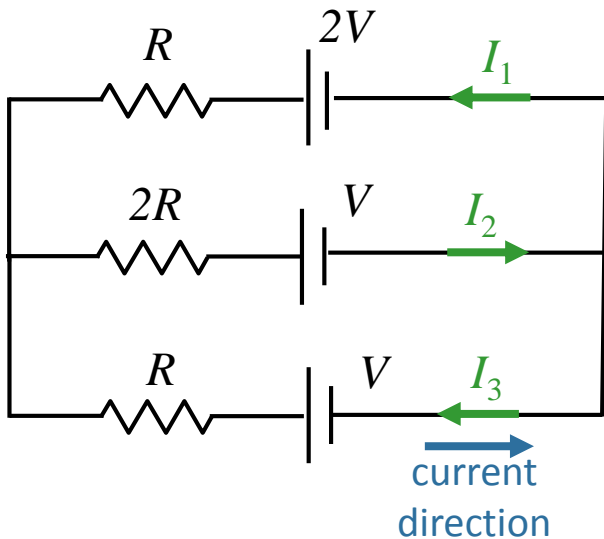

We have 3 equations and 3 unknowns.

$$I_2 = I_1 + I_3$$

$$-2V + I_1 R - I_3 R + V = 0 \quad (\text{outside})$$

$$-V - I_2(2R) - I_1 R + 2V = 0 \quad (\text{top})$$


With this simplification, you can verify:

$$I_2 = (1/5) V/R$$

$$I_1 = (3/5) V/R$$

$$I_3 = (-2/5) V/R$$

Follow Up

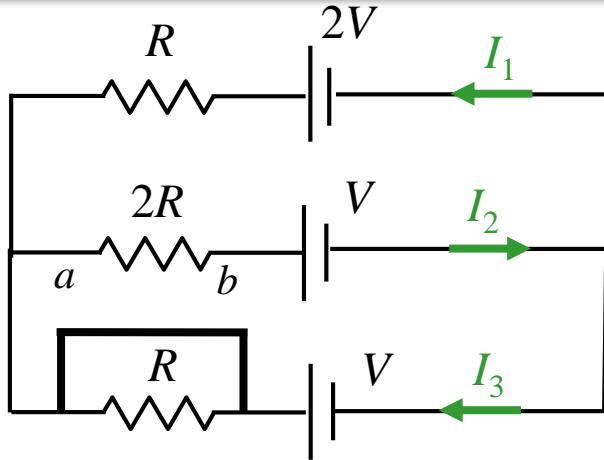

We know:

$$I_2 = (1/5) V/R$$

$$I_1 = (3/5) V/R$$

$$I_3 = (-2/5) V/R$$

Suppose we short R_3 : What happens to V_{ab} (voltage across R_2)?

- A) V_{ab} remains the same
- B) V_{ab} changes sign
- C) V_{ab} increases
- D) V_{ab} goes to zero**


Bottom Loop Equation:

$$V_{ab} + V - V = 0$$


↓
 $V_{ab} = 0$

Why?

Redraw:

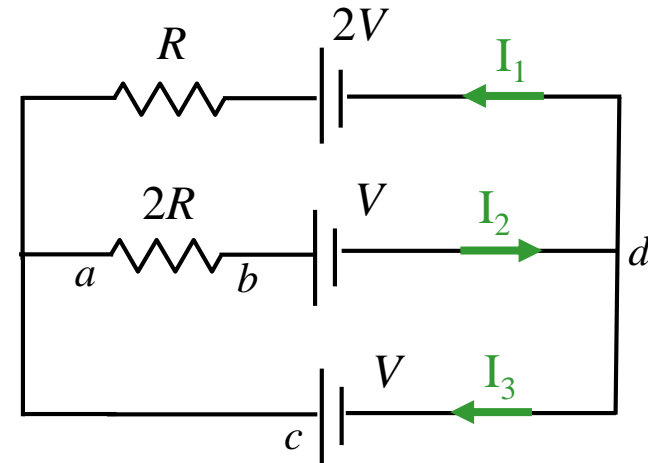

CheckPoint 3 Warm up

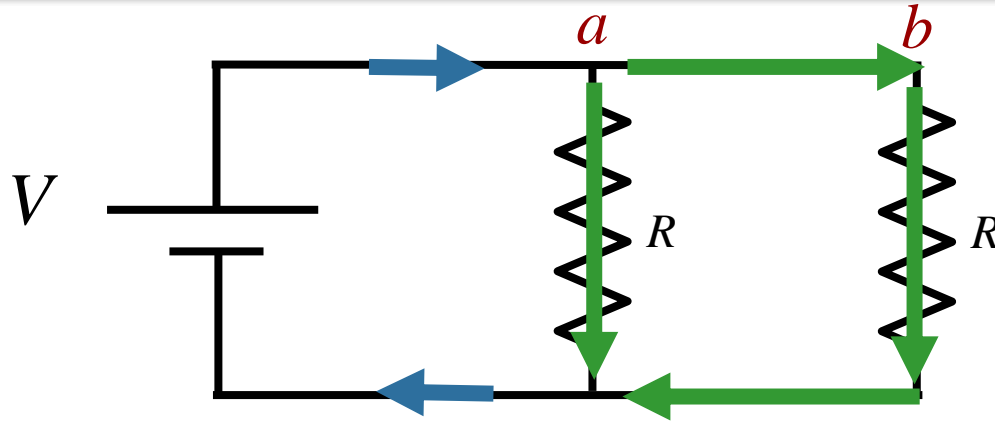

Is there a current flowing between *a* and *b* ?

A) Yes

B) No

a & *b* have the same potential

No current flows between *a* & *b*

Current flows from battery and splits at *a*



Some current flows down
Some current flows right

CheckPoint 3a



Consider the circuit shown below. Note that this question is *not* identical to the similar looking one you answered in the prelecture.

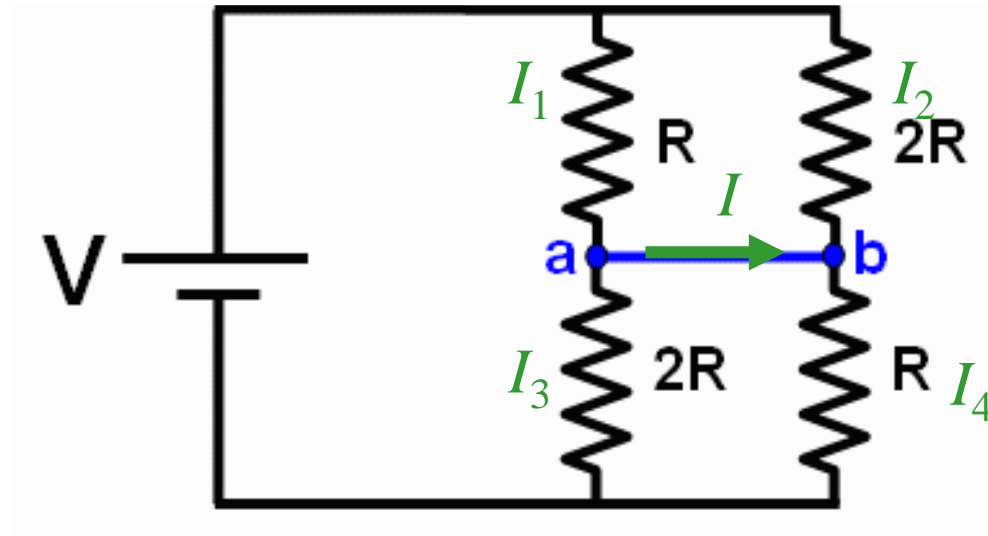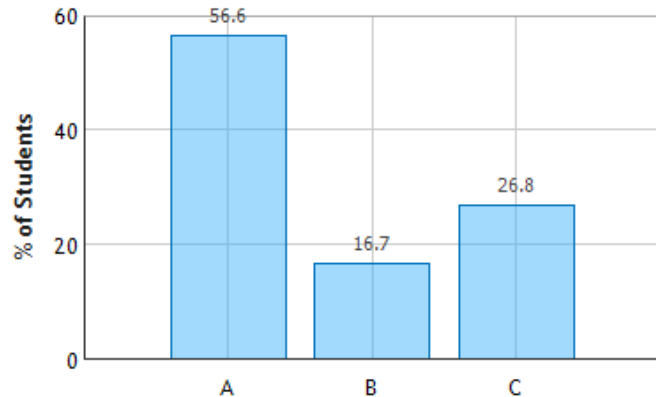Circuits with Resistors and a Battery: Question 1 (N = 732)



Which of the following best describes the current flowing in the blue wire connecting points **a** and **b**?

- A. Positive current flows from a to b**
- B. Positive current flows from b to a
- C. No current flows between a and b


$$I_1 R - I_2 (2R) = 0 \quad \rightarrow \quad I_2 = \frac{1}{2} I_1$$

$$I_4 R - I_3 (2R) = 0 \quad \rightarrow \quad I_4 = 2 I_3$$


$$I = I_1 - I_3$$

$$I + I_2 = I_4 \quad \rightarrow \quad I_1 - I_3 + \frac{1}{2} I_1 = 2 I_3 \quad \rightarrow \quad I_1 = 2 I_3 \quad \rightarrow \quad I = +I_3$$


Prelecture

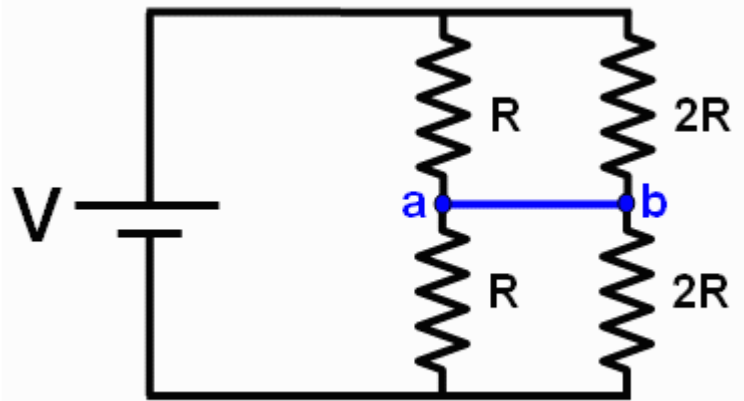


CheckPoint

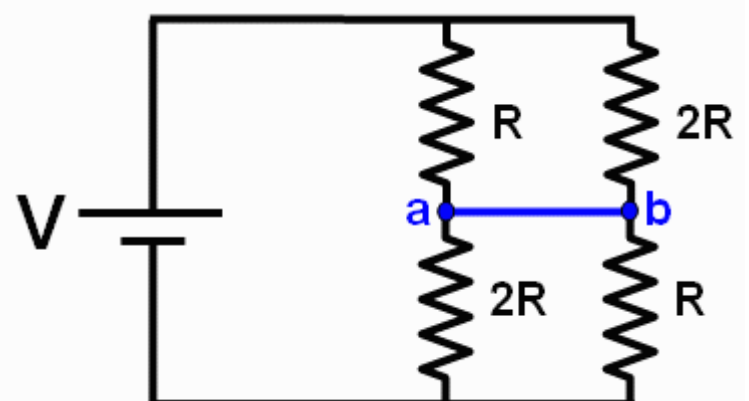


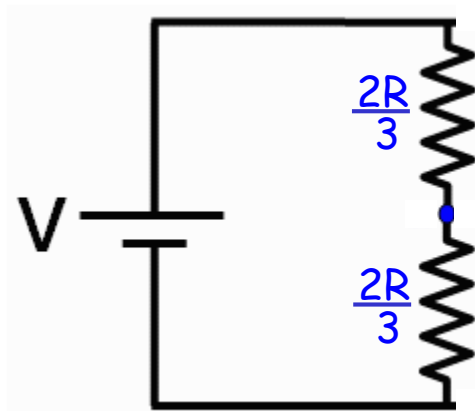
What is the same? Current flowing in and out of the battery.



What is different? Current flowing from a to b.

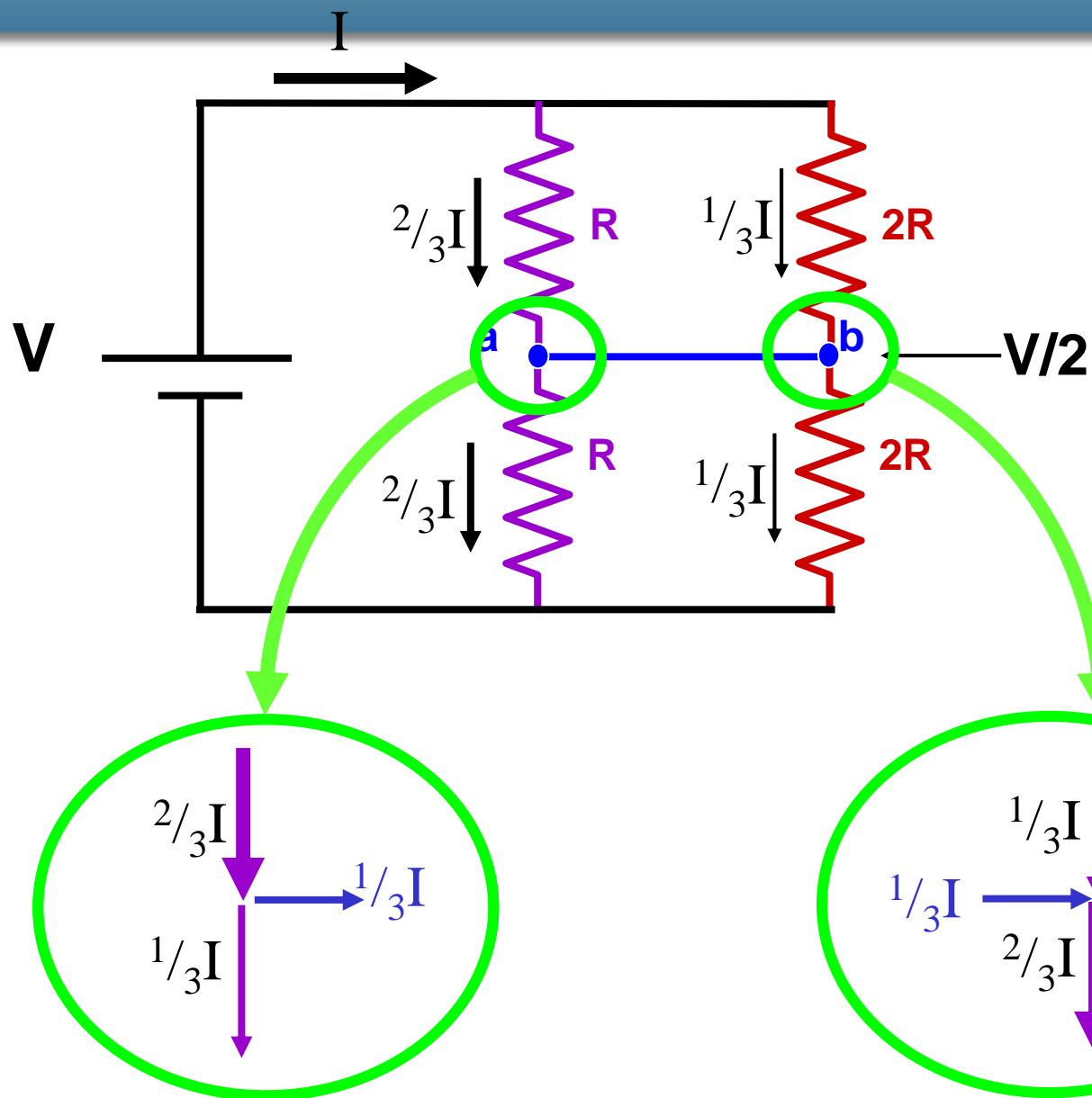

Checkpoint 3b

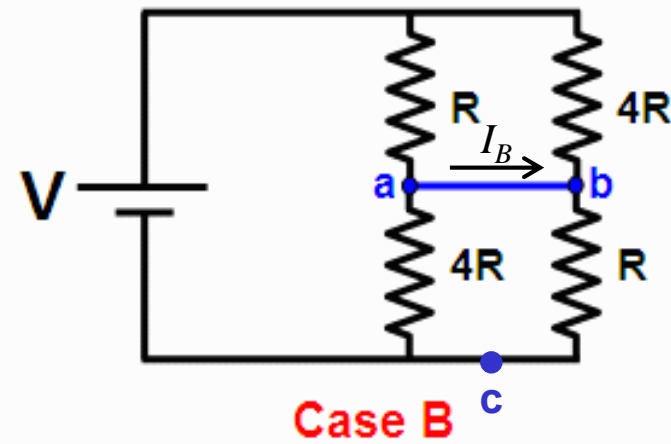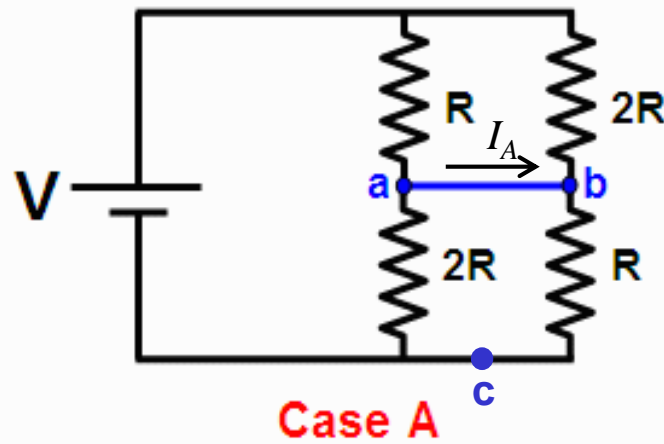

which case is the current flowing in the blue wire connecting points **a** and **b** the largest?

A. Case A

B. Case B

C. They are both the same

Current will flow from left to right in both cases.

In both cases, $V_{ac} = V/2$



$$I_{2R} = 2I_{4R}$$

$$\begin{aligned} I_A &= I_R - I_{2R} \\ &= I_R - 2I_{4R} \end{aligned}$$

$$I_B = I_R - I_{4R}$$

Circuits with Resistors and a Battery: Question 3 (N = 730)

