

Physics 212

Lecture 8

Today's Concept:

Capacitors

(Capacitors in a circuits, Dielectrics, Energy in capacitors)

Your Comments

Overall easy and fun pre-lecture!

I'm still pretty confused on how to do networks of capacitors where there are capacitors in parallel and in series. It would help a lot if we went over these in lecture!

Will we cover dielectric breakdown in this class? (I am not trying to prompt a dangerous experiment, but that sounds like the most direct answer to this question.)

Can charge only move through a dielectric if the capacitor is connected to a battery?

I'm allowed to say this because I'm an engineer too: It's not like we had Valentine's Day plans anyways.... Exam 1 here we come!

when in lecture please clearly distinguish the variable changes when the capacitor is isolated and not.

the capacitor in circuit, i have no idea which properties stay the same and which change. please explain it.

I don't have anything that I really didn't understand, so enjoy a (bad) joke: One capacitor punches another and gets charged with battery.

Please explain how to identify series and parallel capacitors base on the diagram.... I am a little confused about them..

Exam Logistics

1) EXAM 1: WED February 18th at 7pm

- Sign Up in Gradebook for Conflict Exam at 5:15pm if desired
- If you have double conflict please email Prof. Ben Hooberman
- MATERIAL: Lectures 1 - 8

2) EXAM 1 PREPARATION

- Study HW, Discussion
- Old Exams are a good
- See SmartPhysics for

3) Extra Office Hours (Tuesday/ V rooms/times)

Monday, February 9 | 2:03 PM

smartPhysics
Powered by smartFramework

PHYS 212 Spring 2015
University of Illinois

Home | Assignments | Grades | Instructor Links | Administrator Links

[+] Go to current unit

- Electricity [Edit Title](#)

- 1. Coulomb's Law
- 2. Electric Fields
- 3. Electric Flux and Field Lines
- 4. Gauss Law
- 5. Electric Potential Energy
- 6. Electric Potential
- 7. Conductors and Capacitance

+ DC Circuits


+ Magnetism

+ AC Circuits

+ Light and Optics


+ Exam Review Solutions

Simple Capacitor Circuit

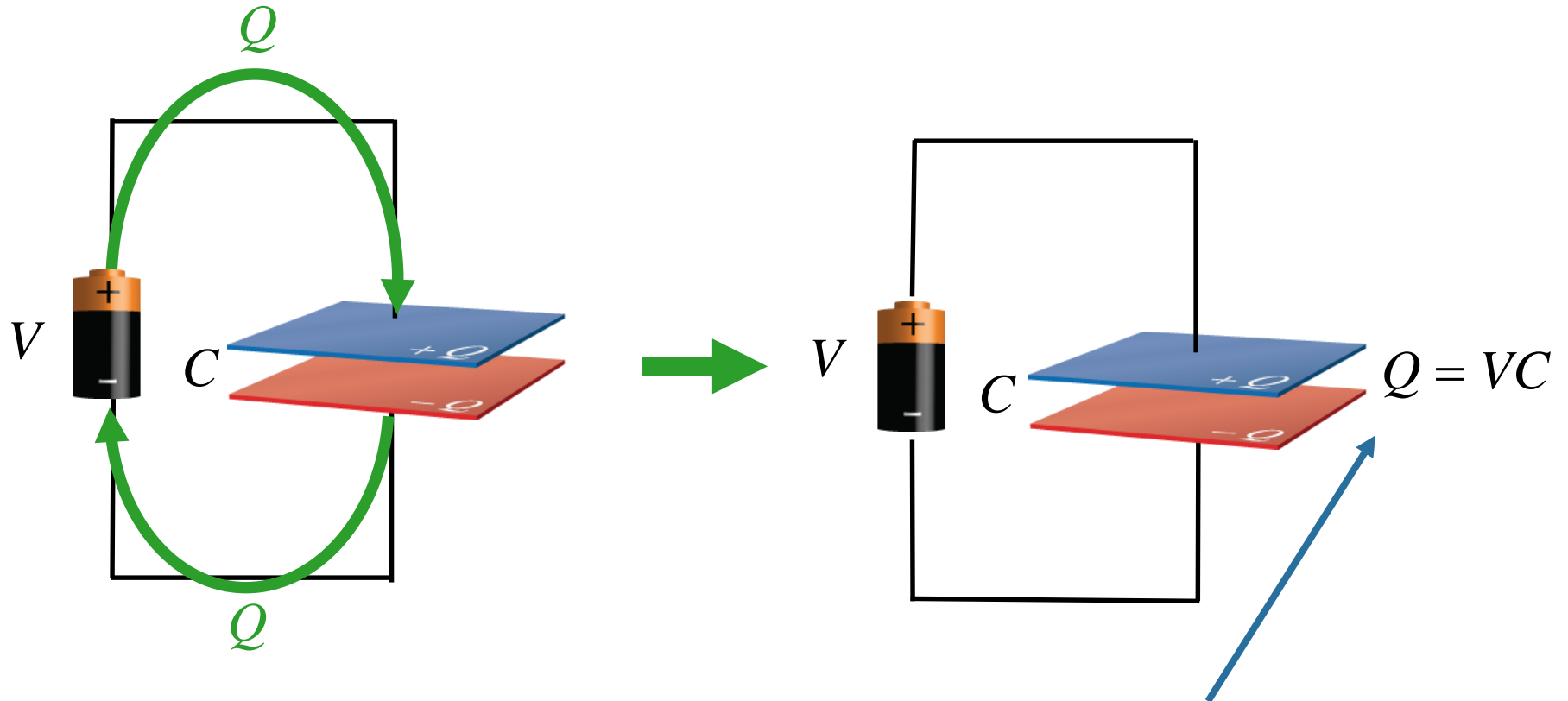

This “ Q ” really means that the battery has moved charge Q from one plate to the other, so that one plate holds $+Q$ and the other $-Q$.

Parallel Capacitor Circuit

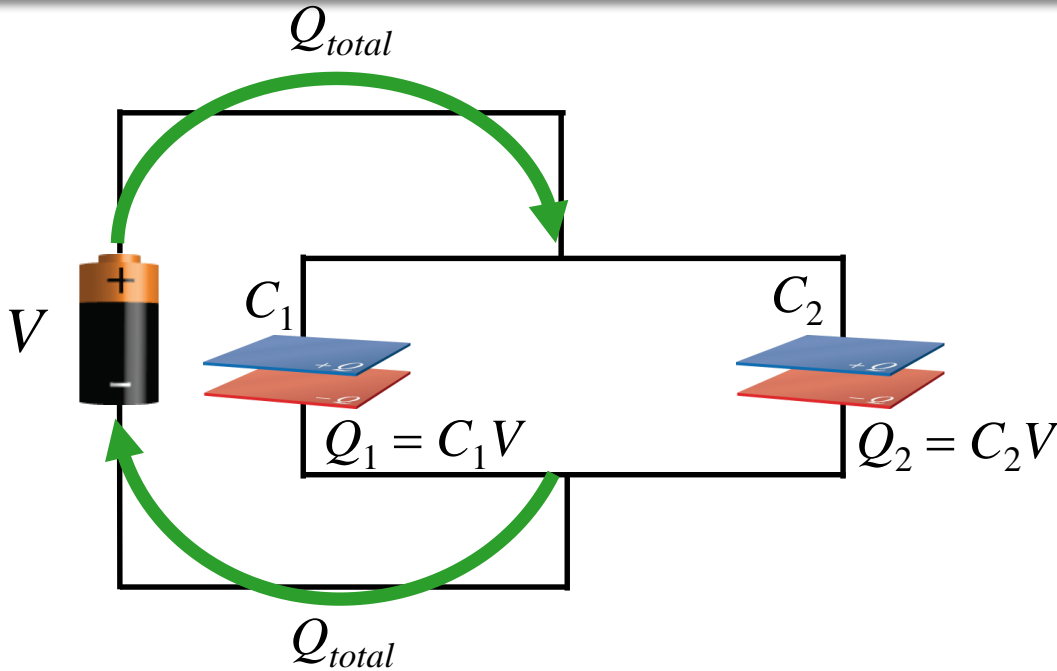


Key point: V is the same for both capacitors

Key Point: $Q_{total} = Q_1 + Q_2 = VC_1 + VC_2 = V(C_1 + C_2)$

$$C_{total} = C_1 + C_2$$

Series Capacitor Circuit

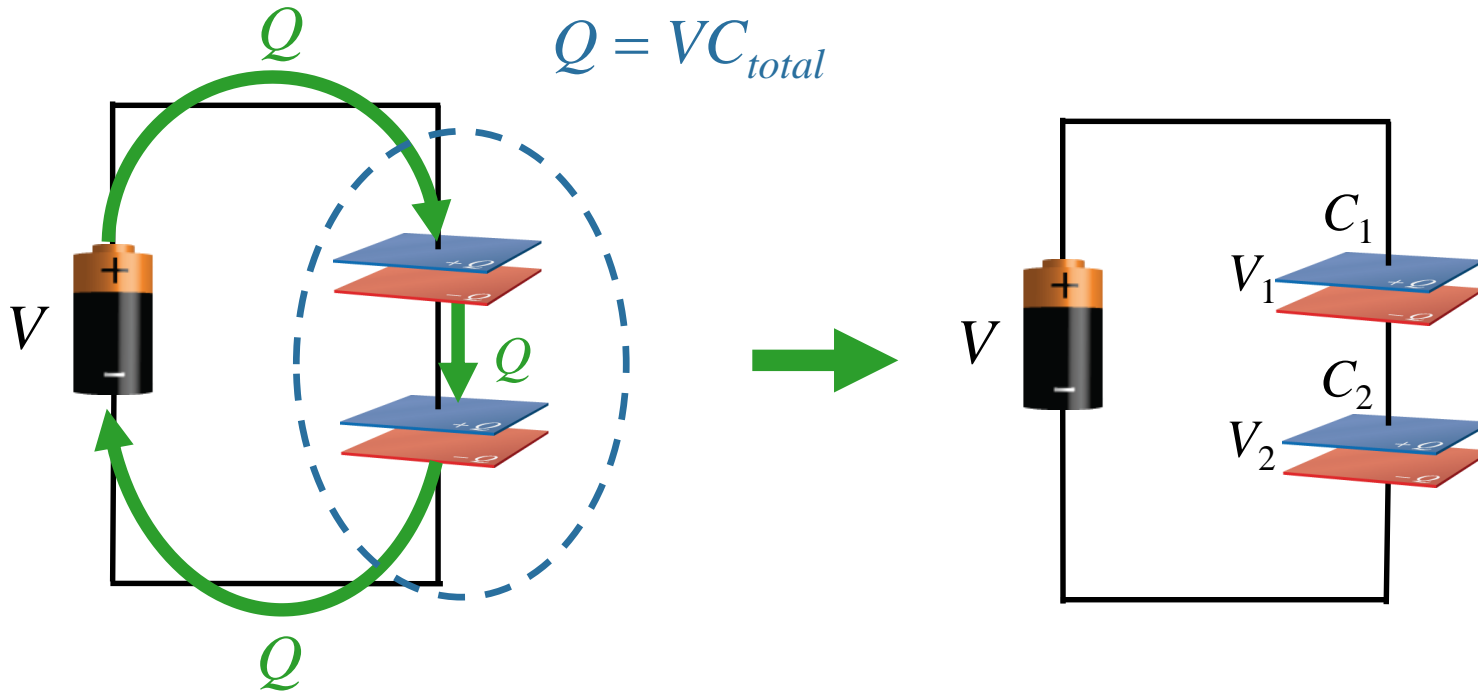

Key point: Q is the same for both capacitors


Key point: $Q = VC_{total} = V_1C_1 = V_2C_2$

Also: $V = V_1 + V_2$ $\longrightarrow Q/C_{total} = Q/C_1 + Q/C_2$


$$\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2}$$

CheckPoint 1

Which has lowest total capacitance:

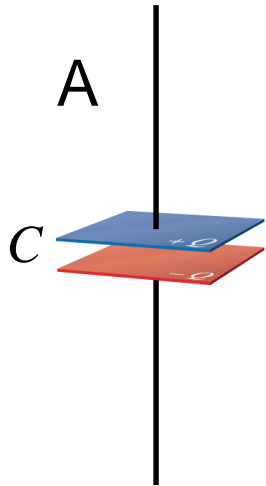



$$C_{total} = C$$

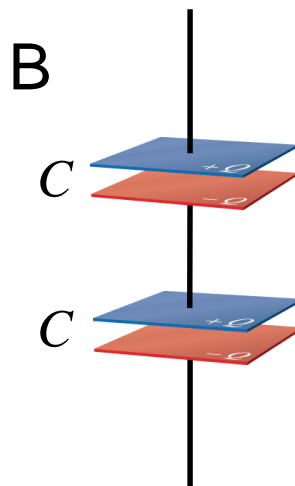

$$\begin{aligned} 1/C_{total} &= 1/C + 1/C \\ &= 2/C \end{aligned}$$

$$C_{total} = C/2$$

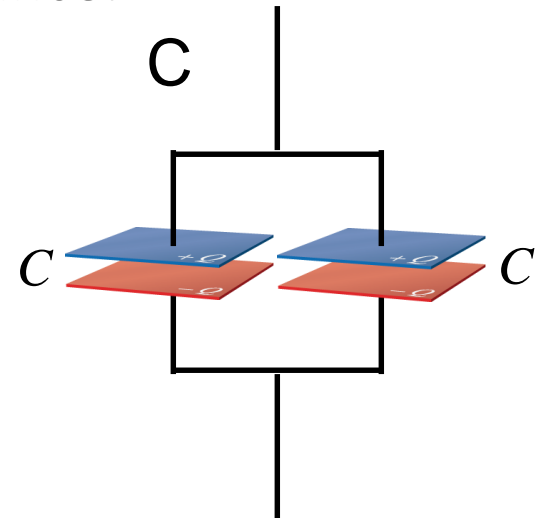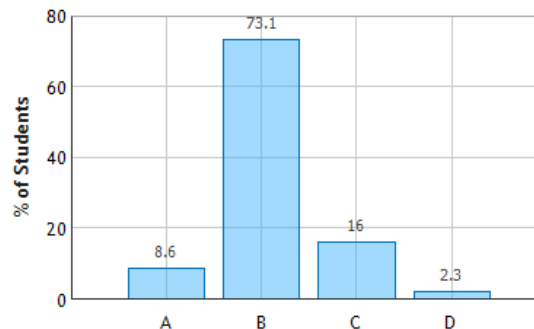Three Capacitor Configurations: Question 1 (N = 789)




$$C_{total} = 2C$$

CheckPoint 2


Which has lowest total capacitance?

A) Single Capacitor B) 4 Capacitors C) Same

:

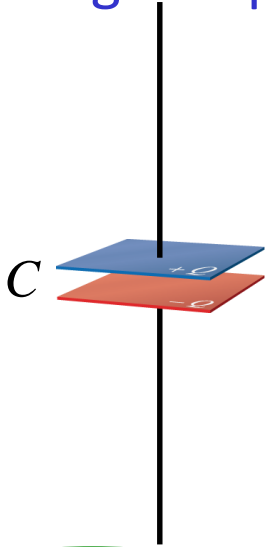

$$C_{total} = C$$

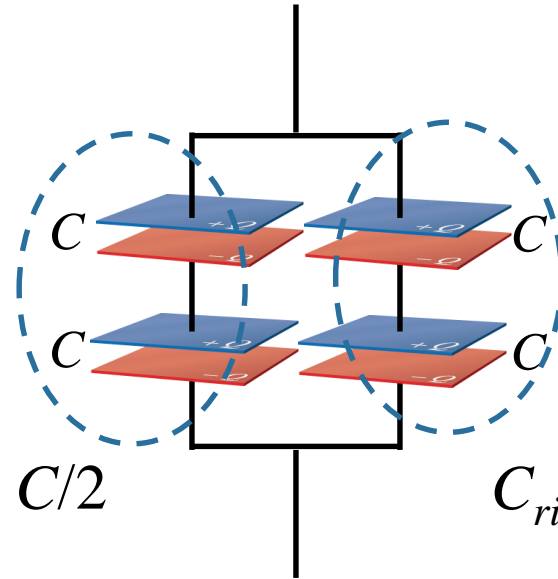


$$C_{left} = C/2$$


$$C_{right} = C/2$$

$$C_{total} = C_{left} + C_{right}$$

$$C_{total} = C$$

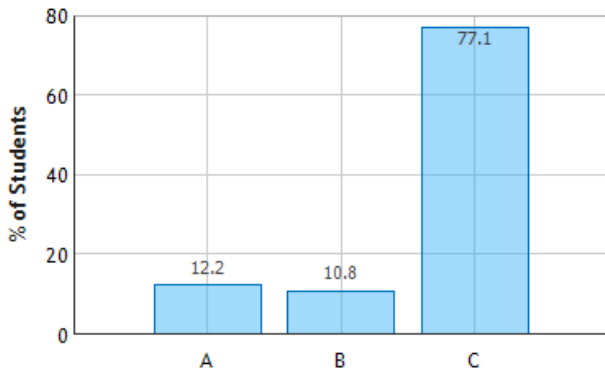

Similar to CheckPoint 3

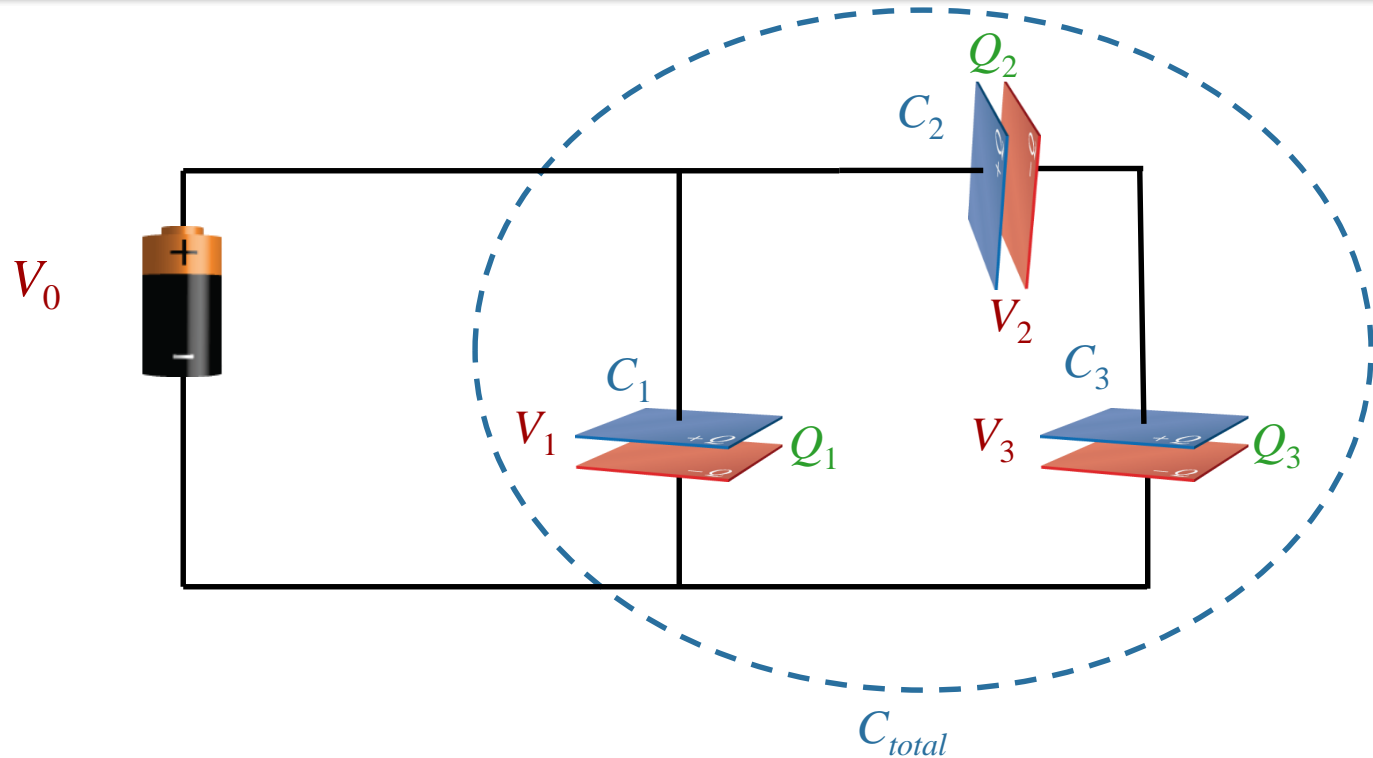



Which of the following is **NOT** necessarily true:

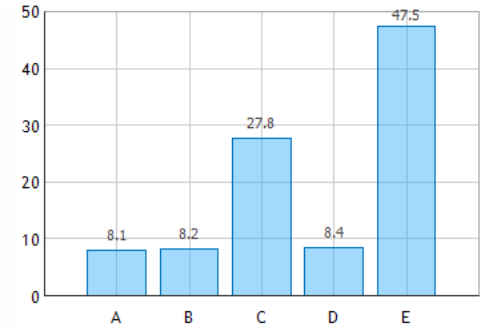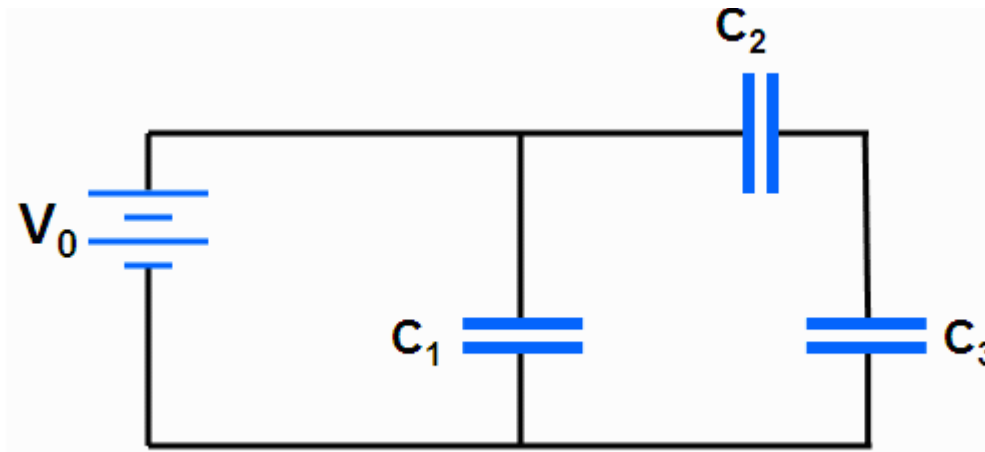- A) $V_0 = V_1$
- B) $C_{total} > C_1$
- C) $V_2 = V_3$
- D) $Q_2 = Q_3$
- E) $V_1 = V_2 + V_3$

CheckPoint 3



A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of voltage V_0 . The capacitance of C_2 is twice that of C_1 . The capacitance of C_3 is three times that of C_1 . The capacitors obtain charges Q_1 , Q_2 , and Q_3 .



~~A.~~ $Q_1 > Q_3 > Q_2$ ~~B.~~ $Q_1 > Q_2 > Q_3$ **C.** $Q_1 > Q_2 = Q_3$ **D.** $Q_1 = Q_2 = Q_3$ **E.** $Q_1 < Q_2 = Q_3$

1. $Q_2 = Q_3$ (capacitors in series)

2. How about Q_1 vs. Q_2 and Q_3 ? Calculate C_{23} first.

$$\frac{1}{C_{23}} = \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{2C_1} + \frac{1}{3C_1} = \frac{5}{6C_1}$$




$$C_{23} = \frac{6}{5} C_1$$



$$Q_1 = C_1 V_0$$

$$Q_{23} = Q_2 = Q_3 = C_{23} V_0 = \frac{6}{5} C_1 V_0$$


Dielectrics

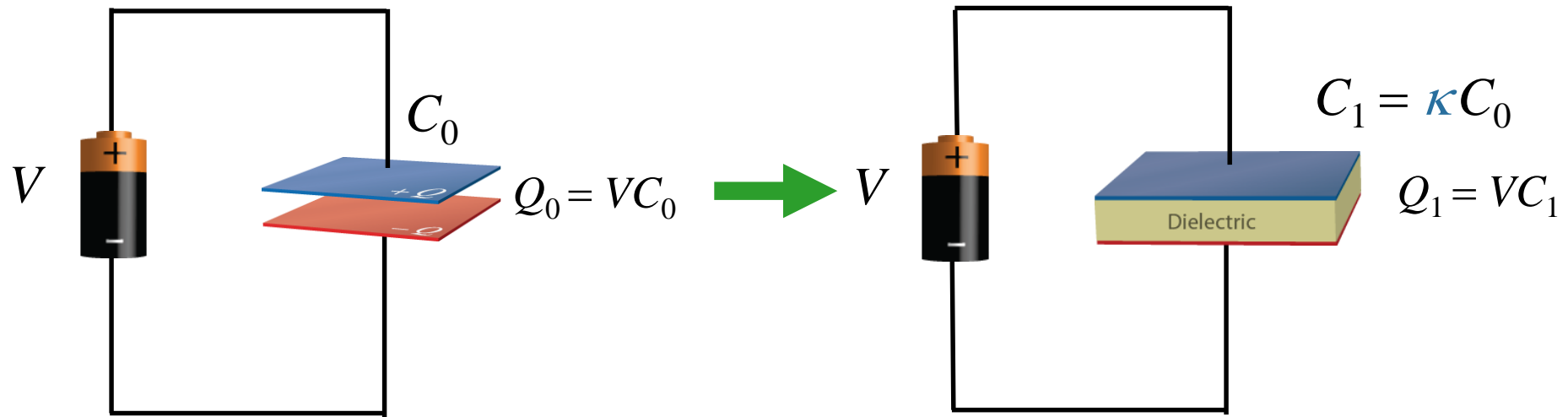

By adding a dielectric you are just making a new capacitor with larger capacitance (factor of κ)

Messing with Capacitors

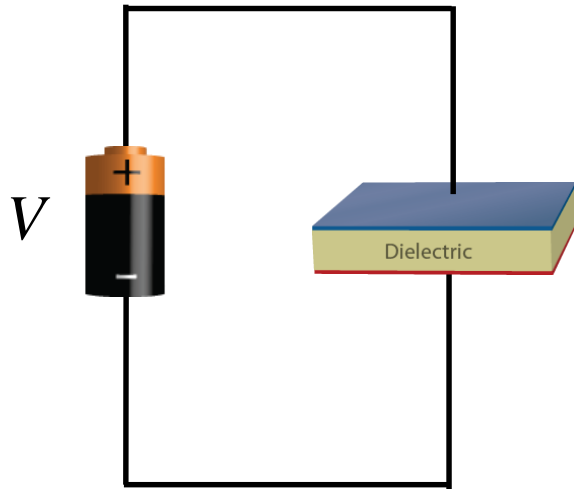If connected to a battery V stays constant




$$V_1 = V$$

$$C_1 = \kappa C$$

$$\left. \begin{array}{l} V_1 = V \\ C_1 = \kappa C \end{array} \right\} \rightarrow Q_1 = C_1 V_1$$

$$= \kappa C V = \kappa Q$$

If isolated then total Q stays constant

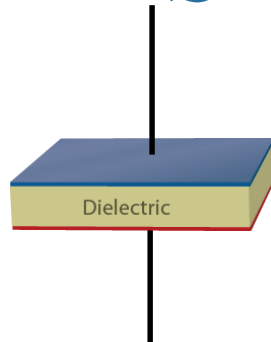

$$Q_1 = Q$$

$$C_1 = \kappa C$$


$$\left. \begin{array}{l} Q_1 = Q \\ C_1 = \kappa C \end{array} \right\} \rightarrow V_1 = Q_1 / C_1$$

$$= Q / \kappa C = V / \kappa$$

CheckPoint 4a



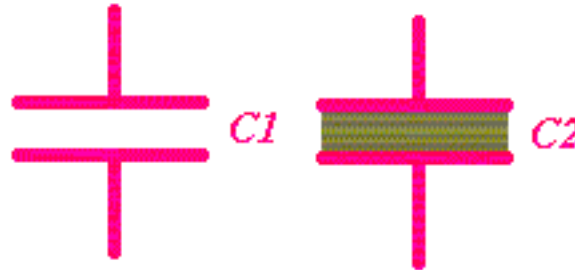Two identical parallel plate capacitors are given the same charge Q , after which they are disconnected from the battery. Then, a dielectric is placed between the plates of C_2




Compare the voltages of the two capacitors.

A $V_1 > V_2$ **B** $V_1 = V_2$ **C** $V_1 < V_2$

“The addition of a dielectric will increase the capacitance of C_2 , thereby decreasing its voltage b the equation $C=Q/V..$ ”

“ V remains constant through the addition of dielectrics. As foretold by the pre-lecture prophesy


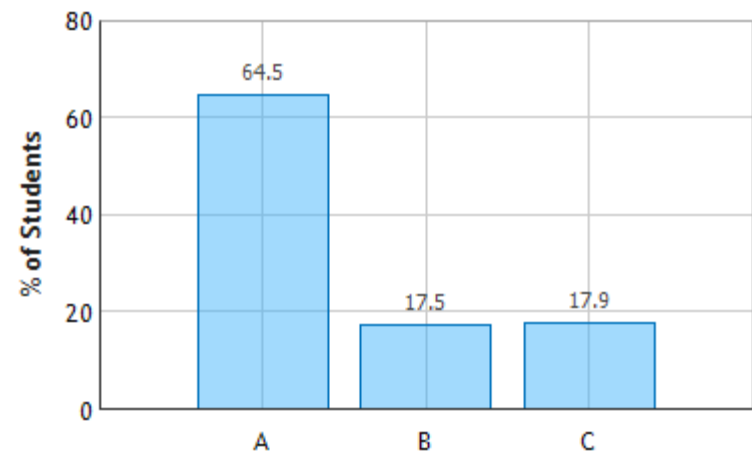
“By adding in the dielectric we are cutting down the distance between the two plates. a lower distance means the plates are higher in voltage.”



Messing with Capacitors Clicker Question



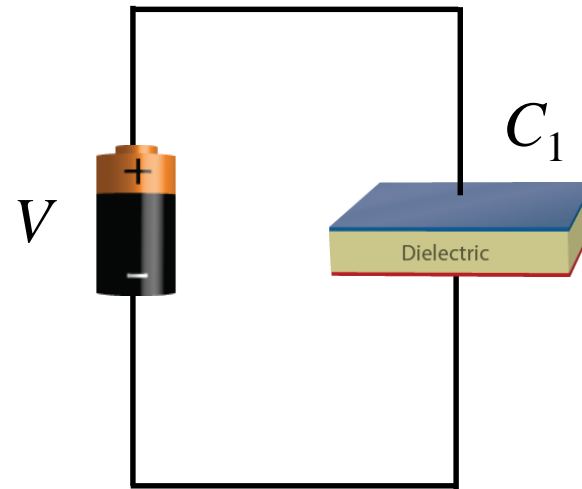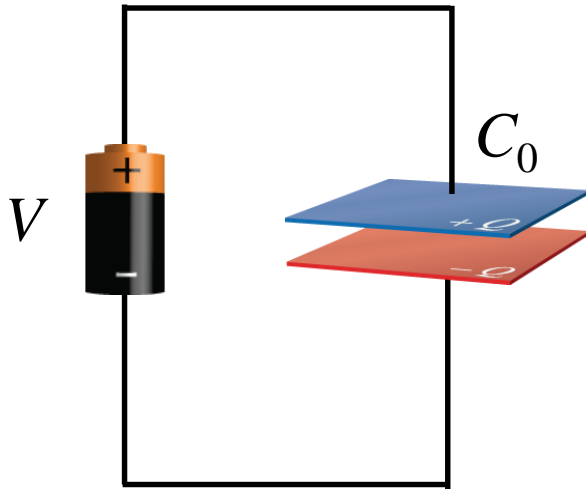Two identical parallel plate capacitors are connected to identical batteries. Then a dielectric is inserted between the plates of capacitor C_1 . Compare the energy stored in the two capacitors.



A) $U_1 < U_0$

B) $U_0 = U_1$

C) $U_1 > U_0$

Compare using $U = \frac{1}{2}CV^2$


$$U_1/U_0 = \kappa$$

→ Potential Energy goes UP

CheckPoint 4b



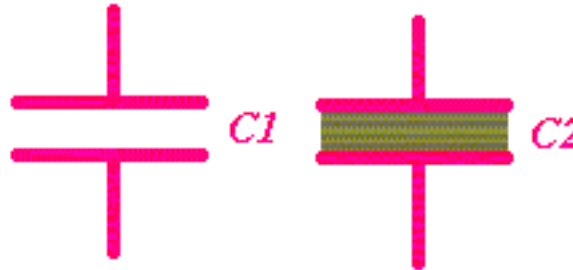Two identical parallel plate capacitors are given the same charge Q , after which they are disconnected from the battery. Then, a dielectric is placed between the plates of C_2



Compare the potential energy stored by the two capacitors.


- A) $U_1 > U_2$ B) $U_1 = U_2$ C) $U_1 < U_2$

$U = (0.5)QV$. As we know that V_2 is smaller than V_1 .

Since there is no battery to supply additional energy, they have the same amount of stored energy.

Since the capacitance of 2 is greater than 1 and the V 's are equal then the charge on 2 must increase and therefore U_2 is greater than U_1


Capacitors with and without a Dielectric:
Question 3 (N = 785)

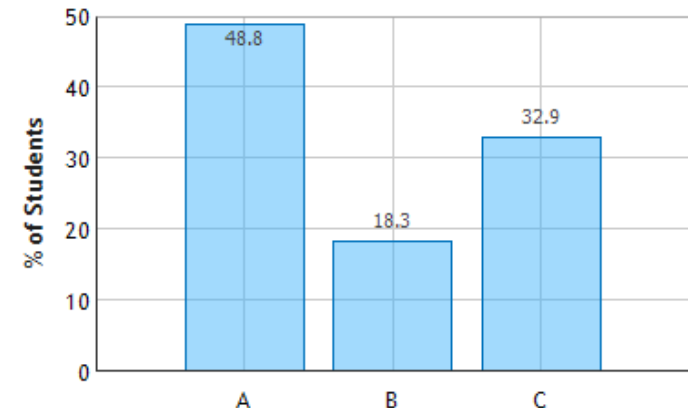

Checkpoint 4c



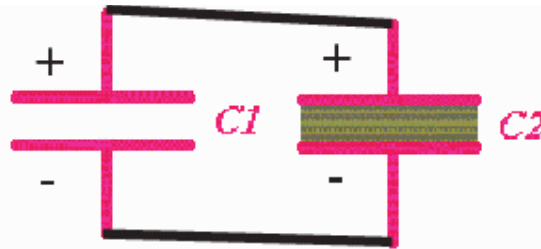Two identical parallel plate capacitors are given the same charge Q , after which they are disconnected from the battery. After C_2 has been charged and disconnected, it is filled with a dielectric. **The two capacitors are now connected to each other by wires as shown. How will the charge redistribute itself, if at all?**




- A. The charges will flow so that the charge on C_1 will become equal to the charge on C_2 .
- B. The charges will flow so that the energy stored in C_1 will become equal to the energy stored in C_2 .
- C. The charges will flow so that the potential difference across C_1 will become the same as the potential difference across C_2 .
- D. No charges will flow. The charge on the capacitors will remain what it was before they were connected.


V must be the same !!

Q: $\frac{Q_1}{C_1} = \frac{Q_2}{C_2} \rightarrow Q_1 = \frac{C_1}{C_2} Q_2$

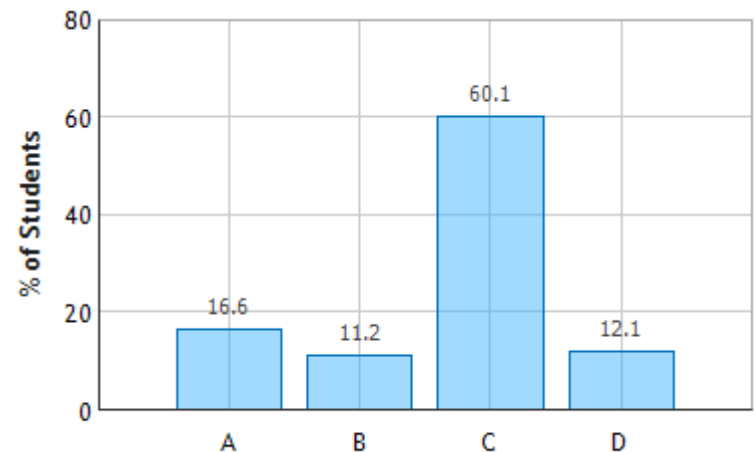U: $U_1 = \frac{1}{2} C_1 V^2$
 $U_2 = \frac{1}{2} C_2 V^2 \rightarrow U_1 = \frac{C_1}{C_2} U_2$



Calculation

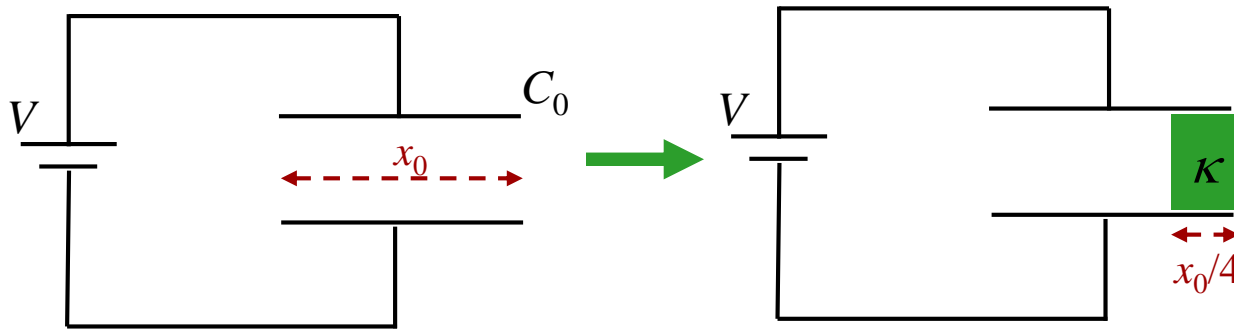

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

Conceptual Analysis:

$$C \equiv \frac{Q}{V}$$

What changes when the dielectric added?

- A) Only C B) only Q C) only V **D) C and Q** E) V and Q


Adding dielectric changes the physical capacitor

→ C changes

V does not change and C changes

→ Q changes

Calculation

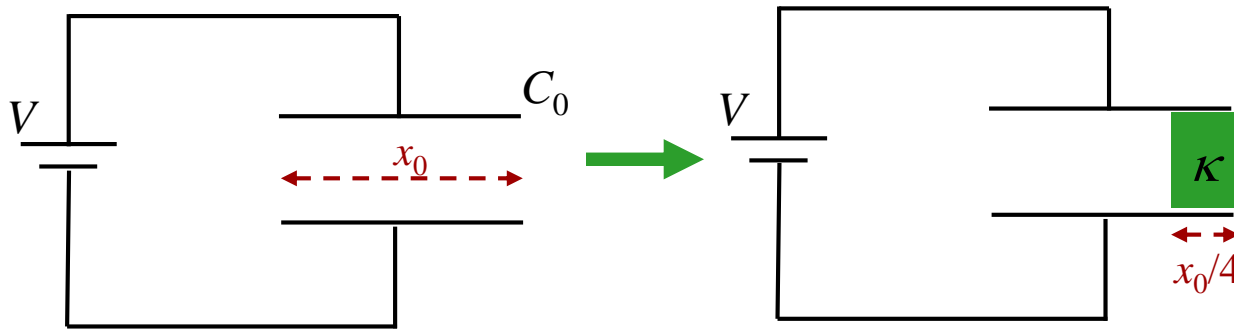

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .


A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Strategic Analysis:

- Calculate new capacitance C
- Apply definition of capacitance to determine Q

What is Q_f , the final charge on the capacitor?

To calculate C , let's first look at:

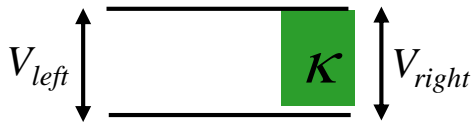


A) $V_{left} < V_{right}$

B) $V_{left} = V_{right}$

C) $V_{left} > V_{right}$

The conducting plate is an equipotential !

Calculation

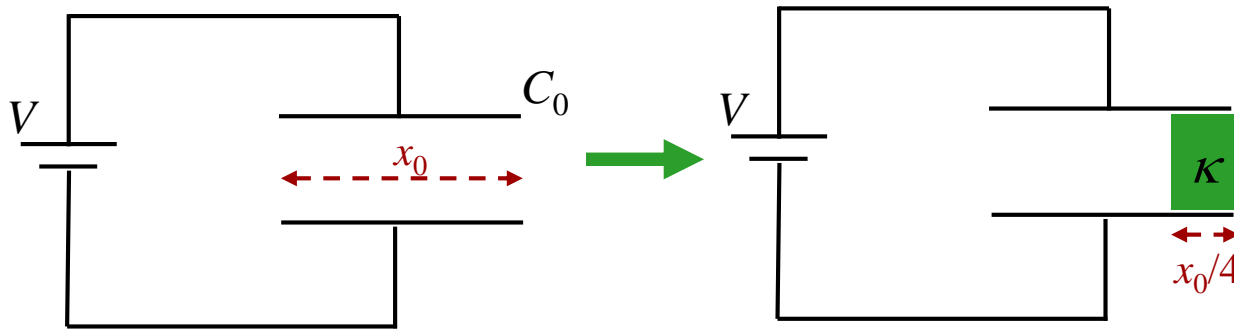


An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

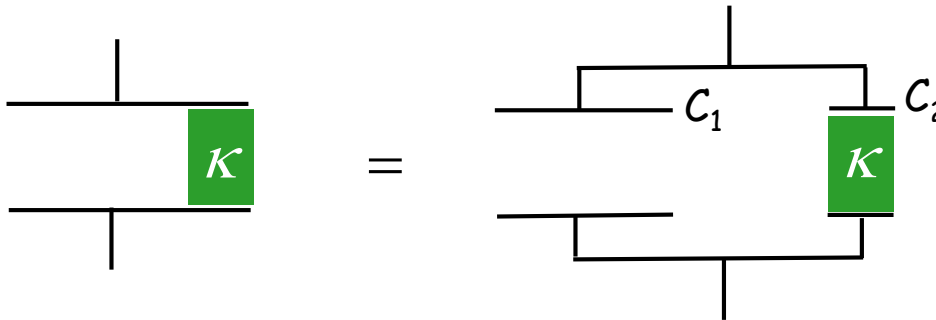Can consider capacitor to be two capacitances, C_1 and C_2 , in parallel




What is C_1 ?

- A) $C_1 = C_0$ B) $C_1 = \frac{3}{4}C_0$ C) $C_1 = \frac{4}{3}C_0$ D) $C_1 = \frac{1}{4}C_0$

In general. For parallel plate capacitor: $C = \epsilon_0 A / d$

$$\begin{array}{l} A = \frac{3}{4}A_0 \\ d = d_0 \end{array} \quad \rightarrow \quad C_1 = \frac{3}{4}(\epsilon_0 A_0 / d_0) \quad \rightarrow \quad C_1 = \frac{3}{4}C_0$$

Calculation

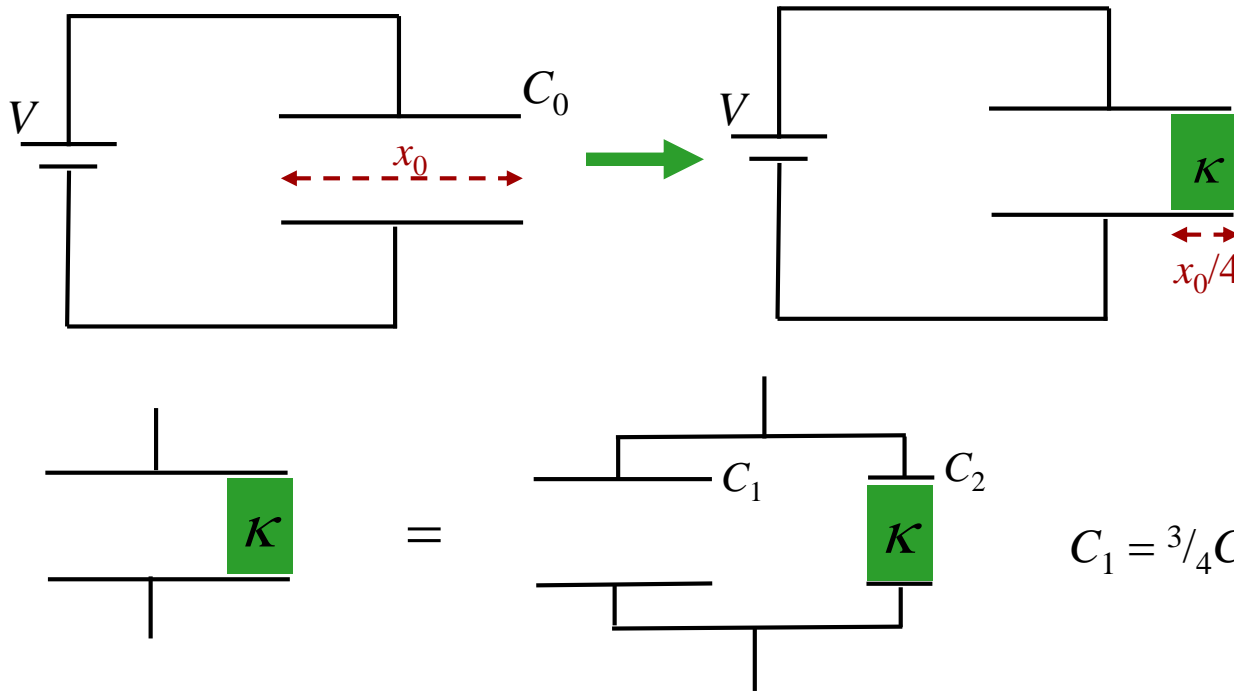

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

What is C_2 ?

A) $C_2 = \kappa C_0$

B) $C_2 = \frac{3}{4} \kappa C_0$


C) $C_2 = \frac{4}{3} \kappa C_0$

D) $C_2 = \frac{1}{4} \kappa C_0$

In general. For parallel plate capacitor filled with dielectric: $C = \kappa \epsilon_0 A/d$


$$\begin{matrix} A = \frac{1}{4}A_0 \\ d = d_0 \end{matrix} \quad \rightarrow \quad C = \frac{1}{4}(\kappa \epsilon_0 A_0/d_0) \quad \rightarrow \quad C_2 = \frac{1}{4} \kappa C_0$$

Calculation

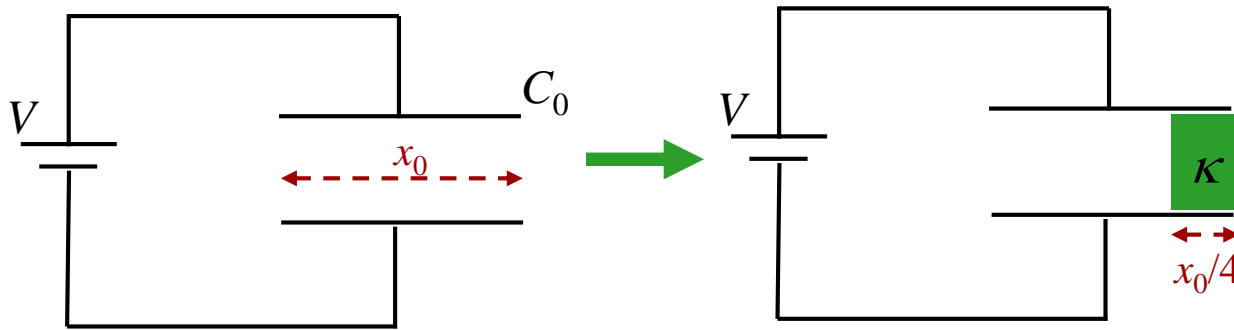

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

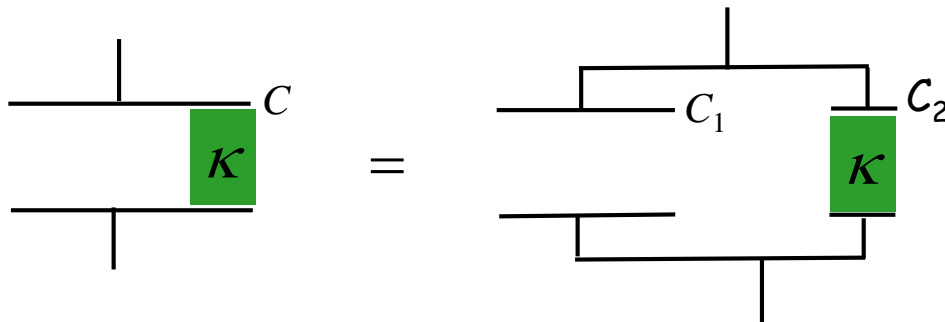A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.



$$C_1 = \frac{3}{4}C_0$$

$$C_2 = \frac{1}{4}\kappa C_0$$

What is Q_f , the final charge on the capacitor?

What is C ?

A) $C = C_1 + C_2$


B) $C = C_1 + \kappa C_2$

C) $C = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$

C = parallel combination of C_1 and C_2 : $C = C_1 + C_2$

$\rightarrow C = C_0 \left(\frac{3}{4} + \frac{1}{4}\kappa \right)$


Calculation

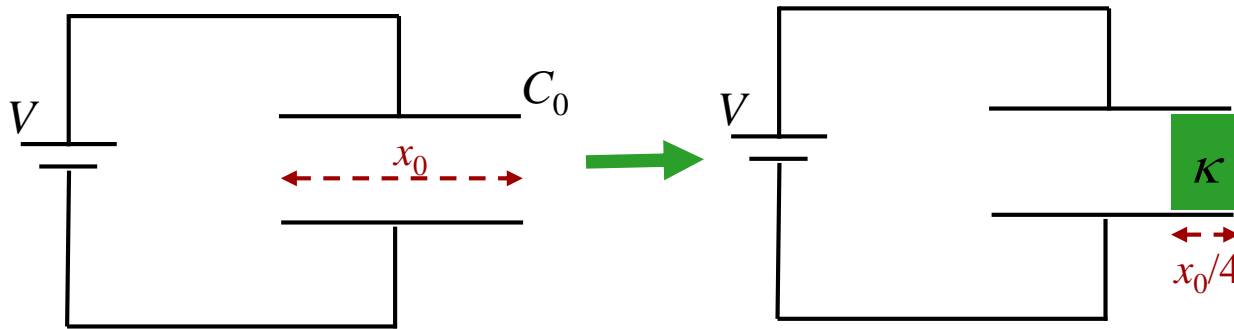

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

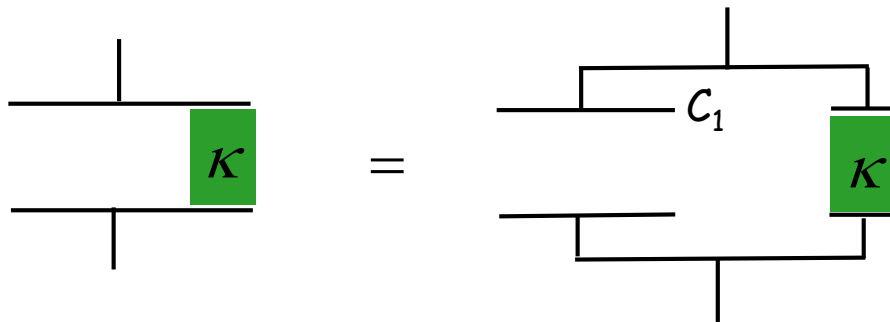What is Q_f , the final charge on the capacitor?



$$C_1 = \frac{3}{4}C_0$$

$$C_2 = \frac{1}{4}\kappa C_0$$

$$\rightarrow C = C_0 \left(\frac{3}{4} + \frac{1}{4}\kappa \right)$$

What is Q ?

$$C \equiv \frac{Q}{V} \rightarrow Q = VC$$

$$Q_f = VC_0 \left(\frac{3}{4} + \frac{1}{4}\kappa \right)$$