

# Your Comments

The checkpoint wasn't bad the prelecture itself was really confusing. I'm too nervous about this exam to get stressed about this stuff! (Also please explain how to calculate  $I_{\max}$ . I believe it's  $w \cdot Q_{\max}$  but I'm not sure)

There was a circuit with a battery, inductor and capacitor in parallel... Why is the charge at  $t = \infty$  zero?

Could we go over the first prelecture question and the derivations of the equations for charge and current for RLC circuits?

I really dislike learning new material the day before the exam, but I'm still optimistic about this lecture.

Do we need to memorize the differential equations?

In 211, around finals time all the homeworks were opened back up and were worth 70%. I was just curious if this would also happen in 212? **Probably.**

Why did the capacitor kiss the inductor? He just couldn't resistor.

# *Some Exam Stuff*

## Exam 2: Wed. Oct. 29 at 7:00

- Covers material in Lectures 9 – 18

## Exam Preparation:

- Study HW, worked HW examples, Discussion, Checkpoints
- Prelecture of Fall 2010 solutions available (10/29 “prelecture”)
- Video Solutions of Spring 2014 Hour Exam 2 (10/29 “optional HW”)
- **For most people, taking old exams is most beneficial**
  - » Take them like real exam (calculator and formula sheet)
  - » Complete full exam, then grade (harshly)
  - » Review problems got wrong (why did you get it wrong)
  - » Repeat

## Extra Office Hours:

- Tue., Wed. (see website for schedule and rooms)

# The Big Ideas L9-18

## Kirchoff's Rules

- Sum of voltages around a loop is zero
- Sum of currents into a node is zero
- Kirchoff's rules with capacitors and inductors
  - In RC and RL circuits: charge and current involve exponential functions with time constant: “charging and discharging”
  - E.g.  $IR + \frac{Q}{C} = V$
- Capacitors and inductors store energy


## Magnetic fields

- Generated by electric currents (no magnetic charges)
- Magnetic forces only on charges in motion  $\vec{F}_{mag} = q\vec{v} \times \vec{B}$
- Easiest to calculate with Ampere's Law  $\oint \vec{B} \cdot d\vec{l} = \mu_0 I_{enclosed}$
- Changing magnetic fields can generate electric fields! FARADAY'S LAW

$$\int \vec{E} \cdot d\vec{l} = EMF = \Delta V = -\frac{d}{dt} \int \vec{B} \cdot d\vec{A} = -\frac{d\phi_{mag}}{dt}$$




# Physics 212

## Lecture 19

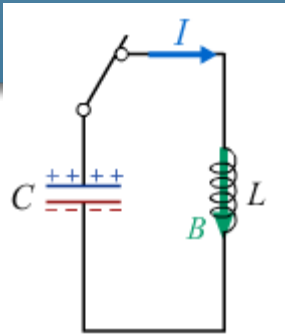


Today's Concepts:

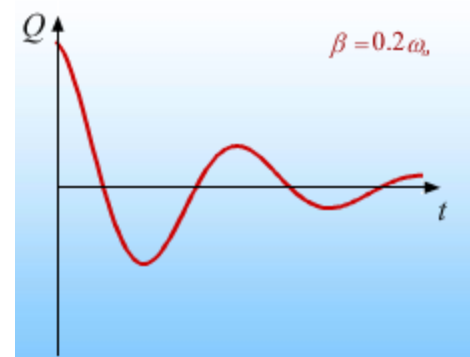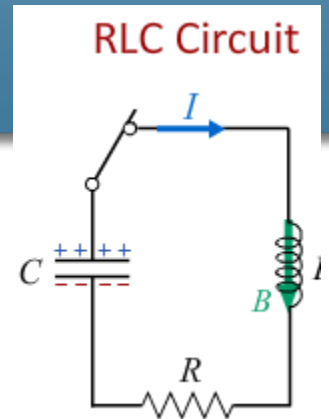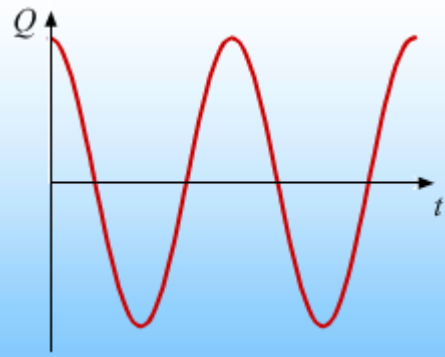- A) Oscillation Frequency
- B) Energy
- C) Damping



# LC Circuit

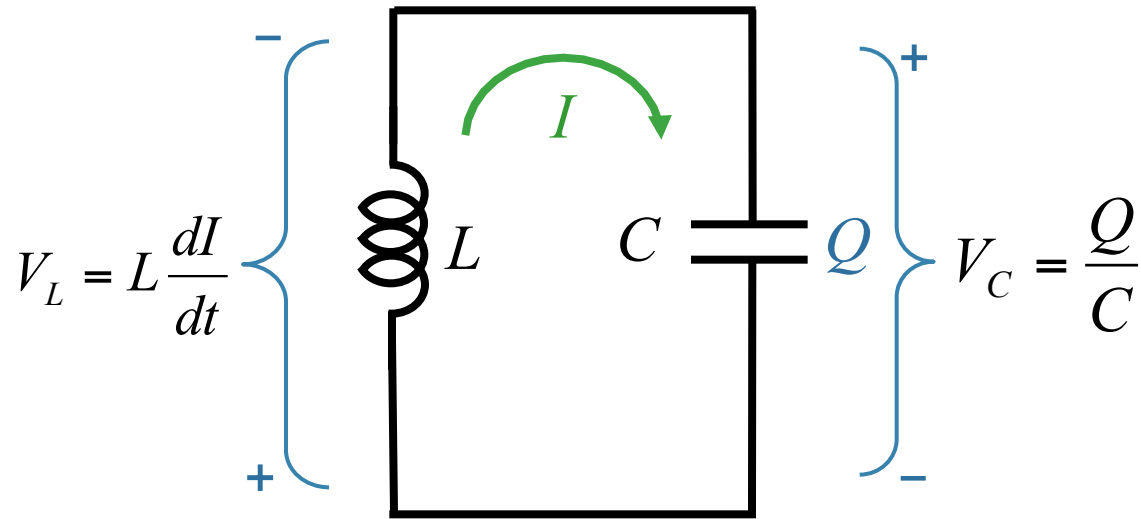

Circuit Equation:  $\frac{Q}{C} + L \frac{dI}{dt} = 0$

$$I = \frac{dQ}{dt} \longrightarrow \frac{d^2 Q}{dt^2} = -\frac{Q}{LC} \longrightarrow \frac{d^2 Q}{dt^2} = -\omega^2 Q$$

where


$$\omega = \frac{1}{\sqrt{LC}}$$

Pendulum.
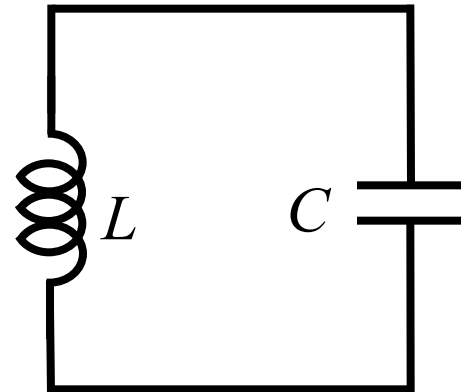
# CheckPoint 1a



At time  $t = 0$  the capacitor is fully charged with  $Q_{max}$  and the current through the circuit is 0.



What is the potential difference across the inductor at  $t = 0$ ?

A)  $V_L = 0$


B)  $V_L = Q_{max}/C$

C)  $V_L = Q_{max}/2C$

since  $V_L = V_C$

The two elements are in parallel,  
so  $V_L = V_C = Q/C$


LC Circuit: Question 1 (N = 815)

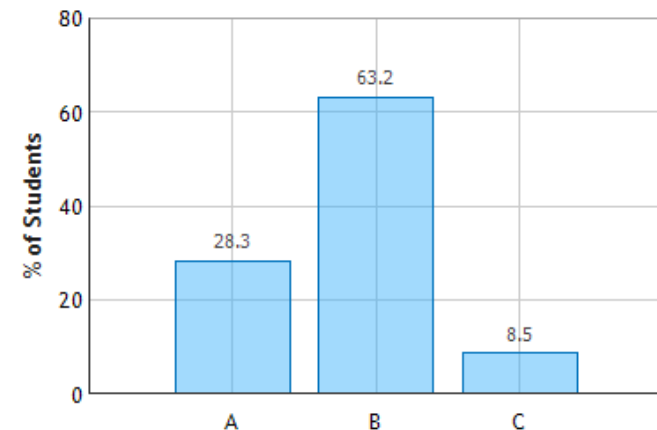

# LC Circuits analogous to mass on spring


$$\frac{d^2 Q}{dt^2} = -\omega^2 Q$$

$$\omega = \frac{1}{\sqrt{LC}}$$

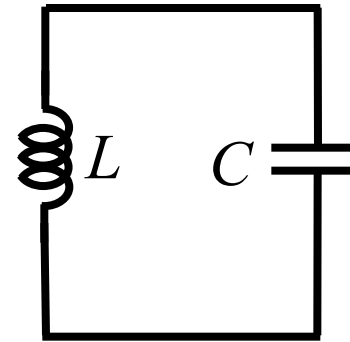

$$\frac{d^2 x}{dt^2} = -\omega^2 x$$

$$\omega = \sqrt{\frac{k}{m}}$$

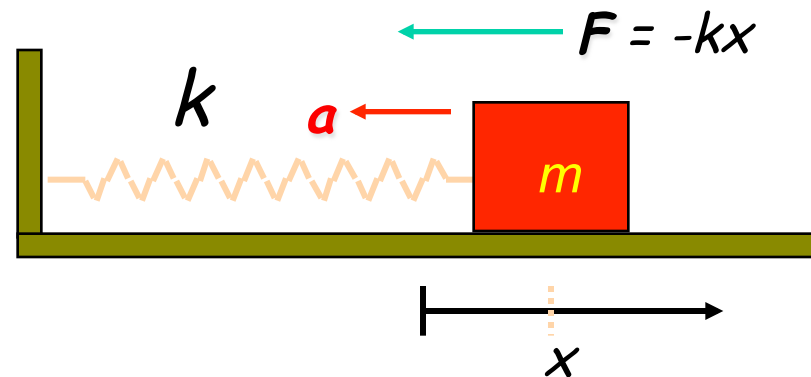



Same thing if we notice that

$$k \leftrightarrow \frac{1}{C}$$

and

$$m \leftrightarrow L$$

# Time Dependence

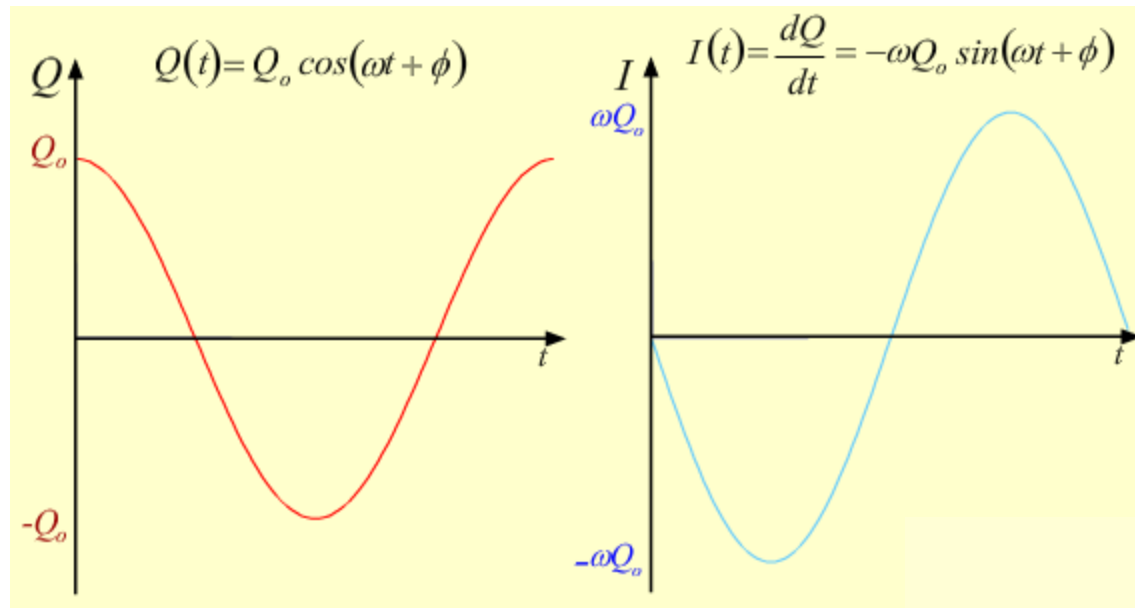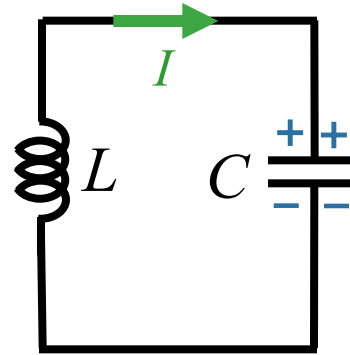



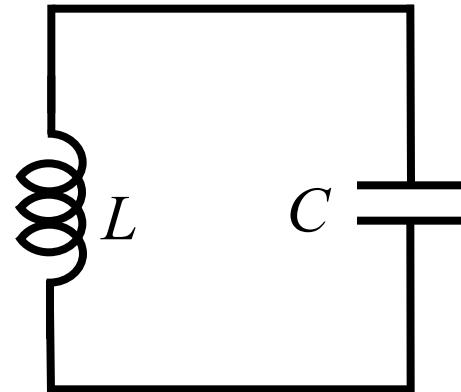
# CheckPoint 1b



At time  $t = 0$  the capacitor is fully charged with  $Q_{max}$  and the current through the circuit is 0.




What is the potential difference across the inductor at when the current is maximum?

- A)  $V_L = 0$
- B)  $V_L = Q_{max}/C$
- C)  $V_L = Q_{max}/2C$

$dI/dt$  is zero when current is maximum


LC Circuit: Question 3 (N = 815)

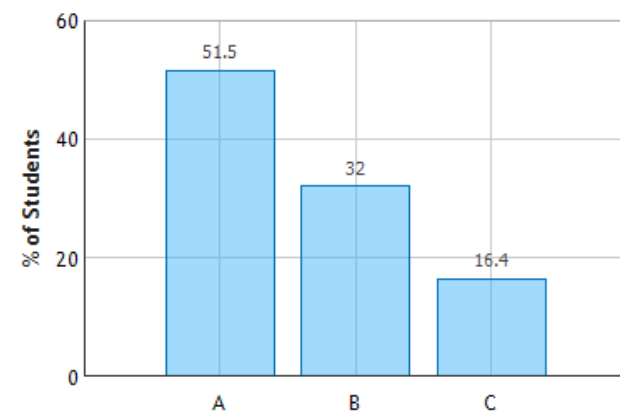
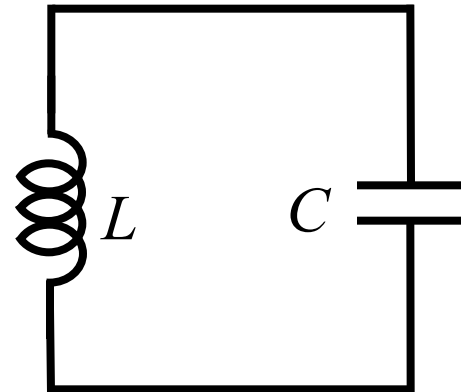
# CheckPoint 1c



At time  $t = 0$  the capacitor is fully charged with  $Q_{max}$  and the current through the circuit is 0.



How much energy is stored in the capacitor when the current is a maximum ?

A)  $U = Q_{max}^2 / (2C)$

B)  $U = Q_{max}^2 / (4C)$

C)  $U = 0$


**Total Energy is constant!**

$$U_{Lmax} = \frac{1}{2} L I_{max}^2$$

$$U_{Cmax} = Q_{max}^2 / 2C$$

$$I = max \text{ when } Q = 0$$


LC Circuit: Question 5 (N = 815)

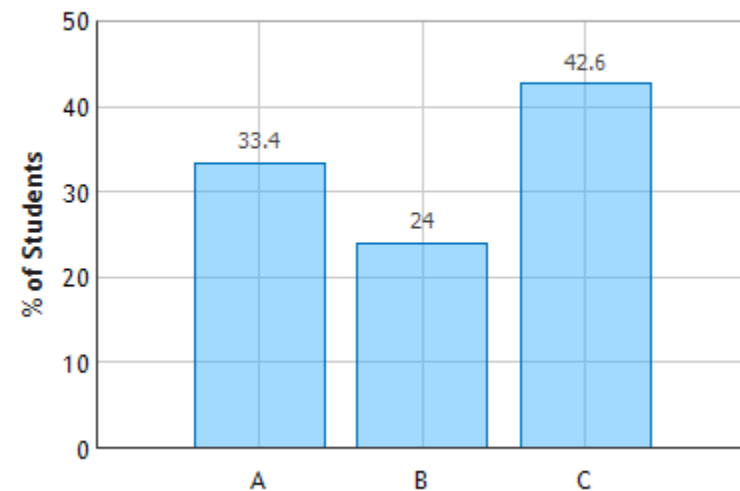
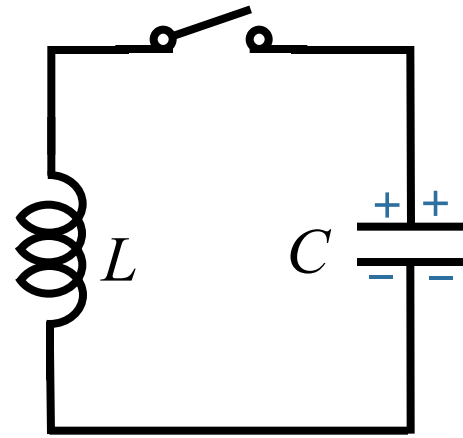
## Checkpoint 2a



The capacitor is charged such that the top plate has a charge  $+Q_0$  and the bottom plate  $-Q_0$ . At time  $t = 0$ , the switch is closed and the circuit oscillates with frequency  $\omega = 500$  radians/s.



$$L = 4 \times 10^{-3} \text{ H}$$
$$\omega = 500 \text{ rad/s}$$

What is the value of the capacitor  $C$ ?


A)  $C = 1 \times 10^{-3} \text{ F}$

B)  $C = 2 \times 10^{-3} \text{ F}$


C)  $C = 4 \times 10^{-3} \text{ F}$

$$\omega = \frac{1}{\sqrt{LC}} \longrightarrow C = \frac{1}{\omega^2 L} = \frac{1}{(25 \times 10^4)(4 \times 10^{-3})} = 10^{-3}$$






LC Circuit 2: Question 1 (N = 811)

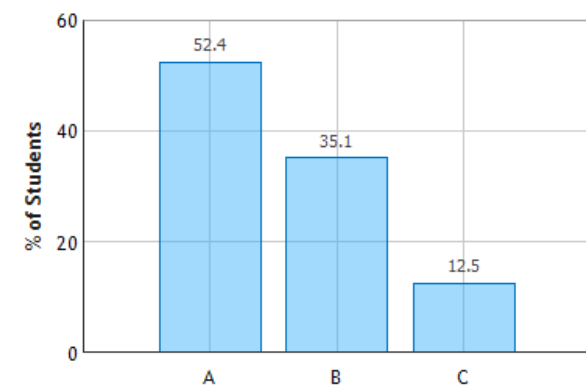

# CheckPoint 2b

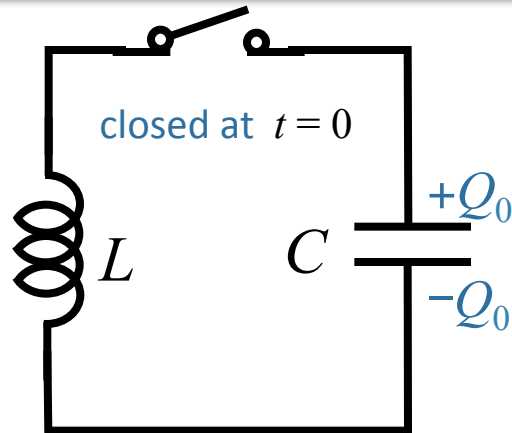

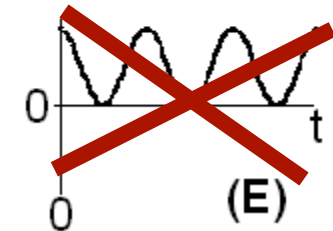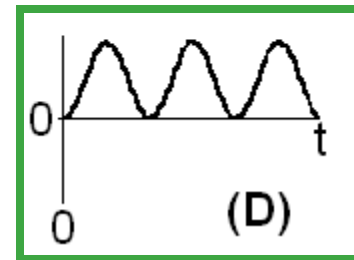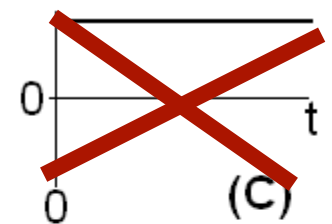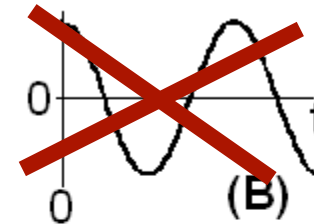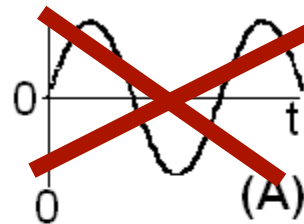Which plot best represents the energy in the inductor as a function of time starting just after the switch is closed?




$$U_L = \frac{1}{2}LI^2$$

Energy proportional to  $I^2$   $\Rightarrow U_L$  cannot be negative

Current is changing  $\Rightarrow U_L$  is not constant

Initial current is zero


LC Circuit 2: Question 3 (N = 813)

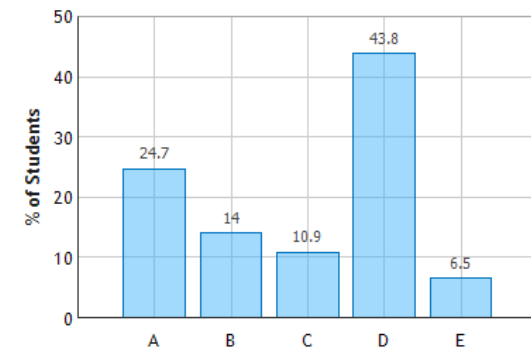

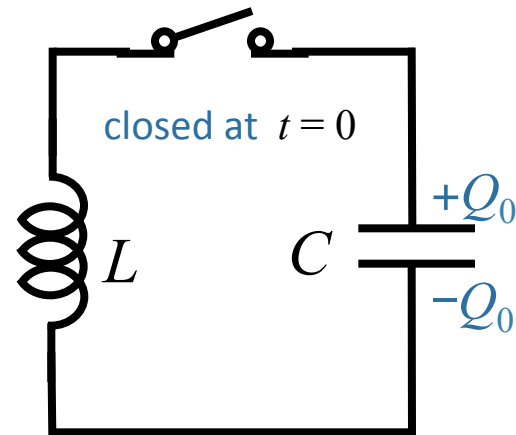
## CheckPoint 2c



When the energy stored in the capacitor reaches its maximum again for the **first time after  $t = 0$** , how much charge is stored on the top plate of the capacitor?



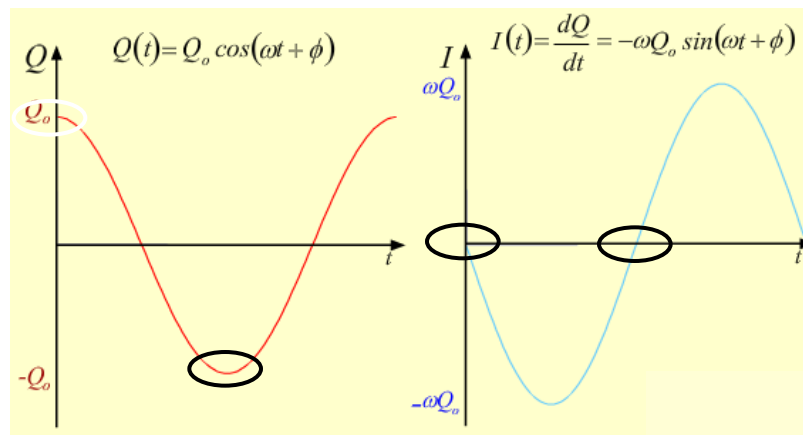- A)  $+Q_0$
- B)  $+Q_0/2$
- C) 0
- D)  $-Q_0/2$
- E)  $-Q_0$**




$Q$  is maximum when current goes to zero

$$I = \frac{dQ}{dt}$$


Current goes to zero twice during one cycle

LC Circuit 2: Question 5 (N = 811)

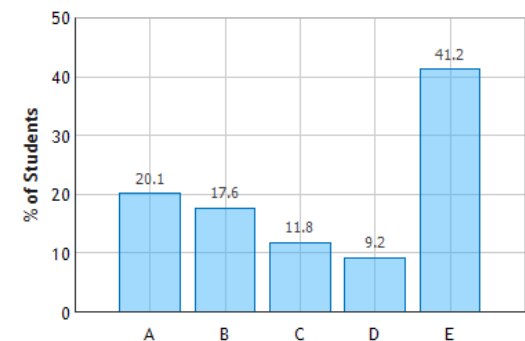
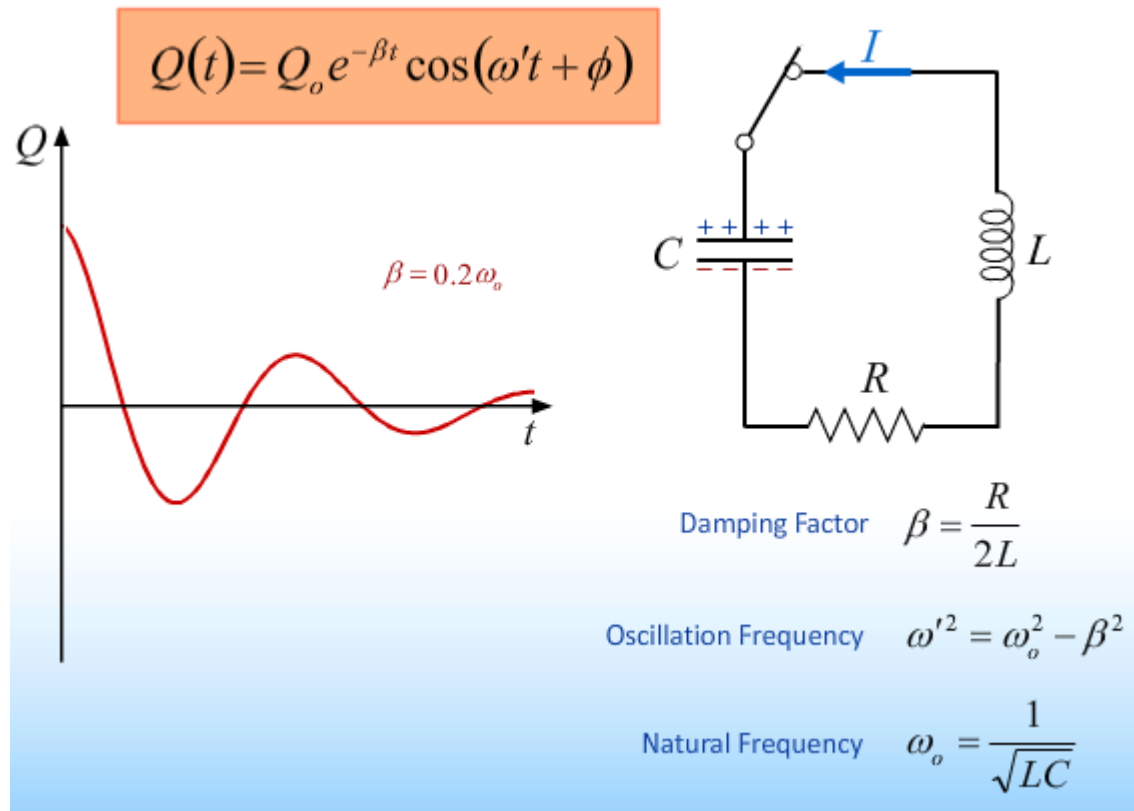
# Add R: Damping

Just like  $LC$  circuit but energy but the oscillations get smaller because of  $R$



Concept makes sense...

...but answer looks kind of complicated

# Physics Truth #1:

Even though the answer sometimes looks complicated...


$$Q(t) = Q_o \cos(\omega t - \phi)$$

the physics under the hood is still very simple!

$$\frac{d^2 Q}{dt^2} = -\omega^2 Q$$

The elements of a circuit are very simple:

$$V_L = L \frac{dI}{dt}$$

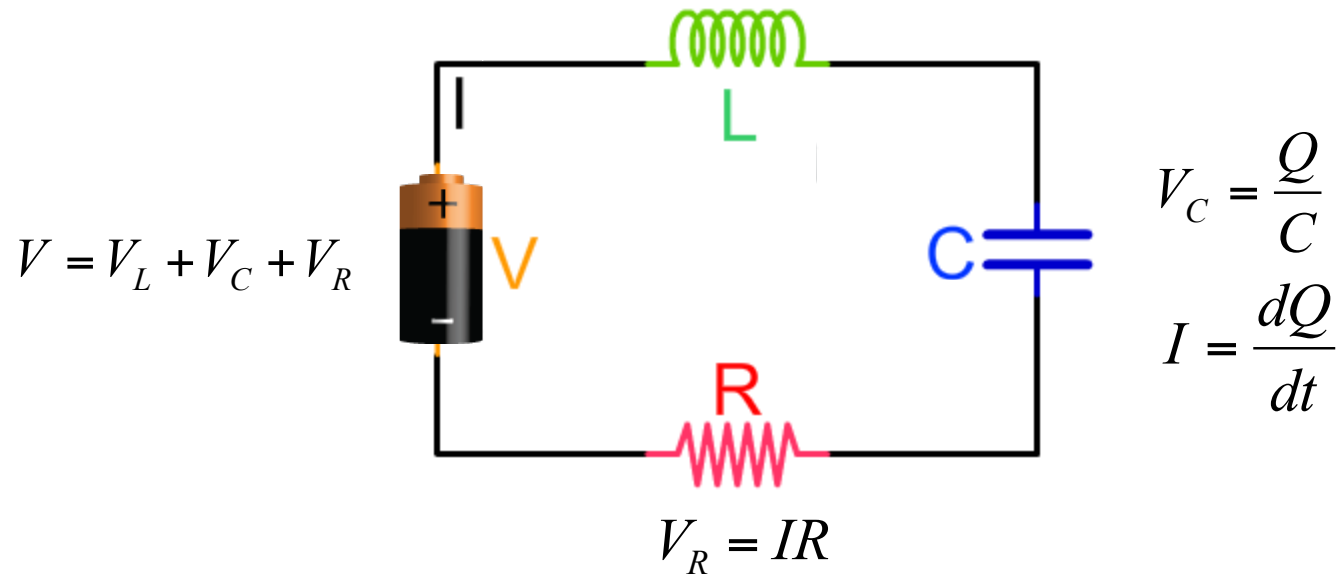


This is all we need to know to solve for anything!



# A Different Approach

Start with some initial  $V$ ,  $I$ ,  $Q$ ,  $V_L$

Now take a tiny time step  $dt$  (1 ms)

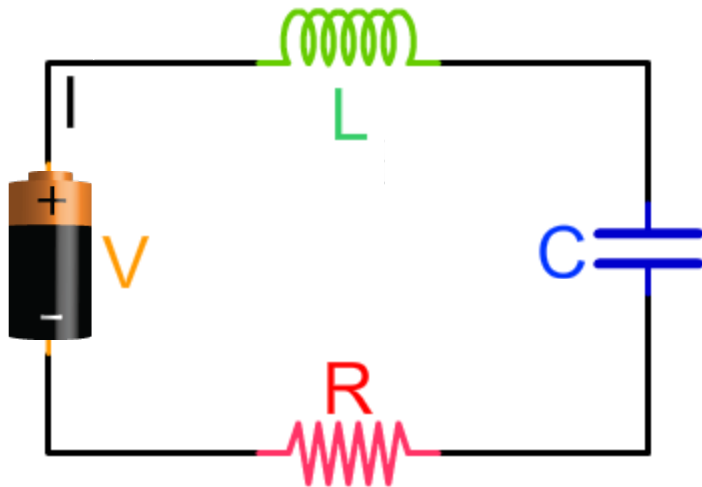

```
for (var t=0; t<tStepSec; t+=dt) {  
  I += Vind_last*dt/L;  
  Qcap += I*dt;  
  Vcap = Qcap/C;  
  Vres = I*R1;  
  Vind_last = Vind;  
  Vind = Va - Vres - Vcap;  
}
```

$$dI = \frac{V_L}{L} dt$$


$$dQ = Idt$$

$$V_C = \frac{Q}{C}$$

$$V_R = IR$$

$$V_L = V - V_R - V_C$$


Repeat...

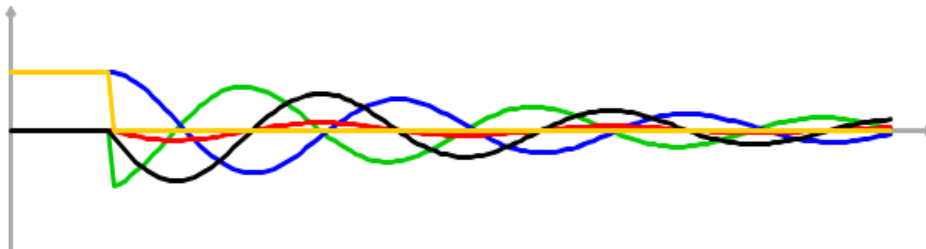
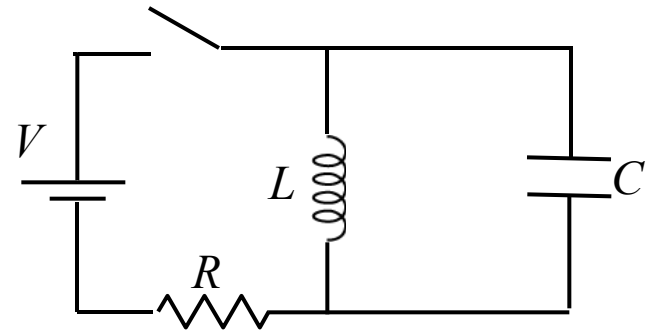
# Calculation

The switch in the circuit shown has been closed for a long time. At  $t = 0$ , the switch is opened.

What is  $Q_{MAX}$ , the maximum charge on the capacitor?



## Conceptual Analysis


Once switch is opened, we have an  $LC$  circuit  
Current will oscillate with natural frequency  $\omega_0$

## Strategic Analysis

Determine initial current  
Determine oscillation frequency  $\omega_0$   
Find maximum charge on capacitor
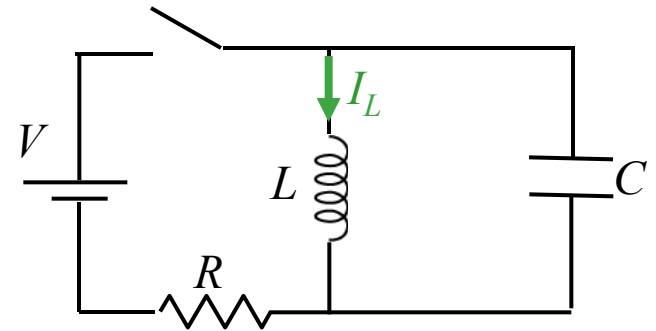
# Calculation

The switch in the circuit shown has been closed for a long time. At  $t = 0$ , the switch is opened.



What is  $I_L$ , the current in the inductor, immediately **after** the switch is opened? Take positive direction as shown.

A)  $I_L < 0$

B)  $I_L = 0$

C)  $I_L > 0$


Current through inductor immediately **after** switch is opened  
**is the same as**  
the current through inductor immediately **before** switch is opened

**before switch is opened:**  
all current goes through inductor in direction shown
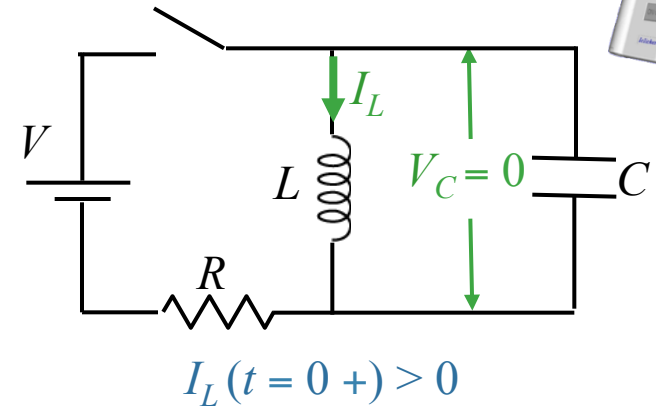
# Calculation



The switch in the circuit shown has been closed for a long time. At  $t = 0$ , the switch is opened.



The energy stored in the capacitor immediately after the switch is opened is zero.

**A) TRUE**

B) FALSE

before switch is opened:

$$dI_L/dt \sim 0 \Rightarrow V_L = 0$$

BUT:  $V_L = V_C$   
since they are in parallel

$$\longrightarrow V_C = 0$$

after switch is opened:

$V_C$  cannot change abruptly

$$\longrightarrow V_C = 0$$

$$\longrightarrow U_C = \frac{1}{2} C V_C^2 = 0 !$$

**IMPORTANT:** NOTE DIFFERENT CONSTRAINTS AFTER SWITCH OPENED


CURRENT through INDUCTOR cannot change abruptly

VOLTAGE across CAPACITOR cannot change abruptly
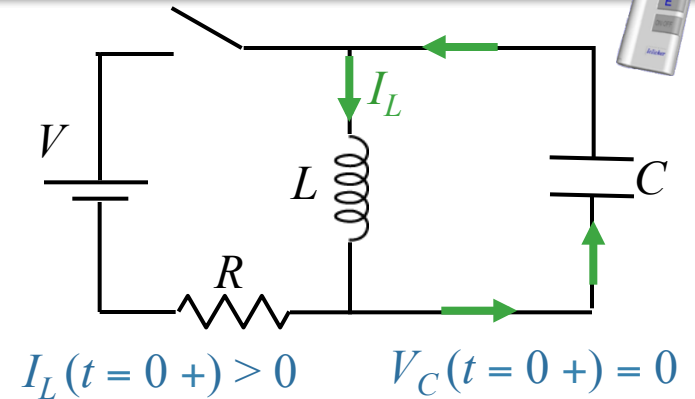
# Calculation



The switch in the circuit shown has been closed for a long time. At  $t = 0$ , the switch is opened.



What is the direction of the current immediately after the switch is opened?

A) clockwise

B) counterclockwise

Current through inductor immediately **after** switch is opened  
**is the same as**  
the current through inductor immediately **before** switch is opened


**Before** switch is opened: Current moves down through  $L$

**After** switch is opened: Current continues to move down through  $L$
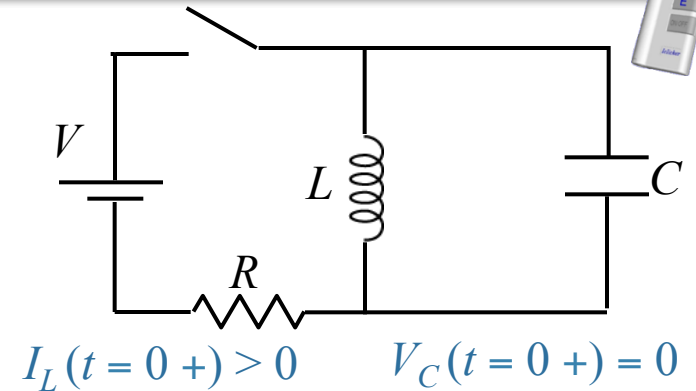
# Calculation



The switch in the circuit shown has been closed for a long time. At  $t = 0$ , the switch is opened.



What is the magnitude of the current right after the switch is opened?

A)  $I_o = V \sqrt{\frac{C}{L}}$


B)  $I_o = \frac{V}{R^2} \sqrt{\frac{L}{C}}$

C)  $I_o = \frac{V}{R}$

D)  $I_o = \frac{V}{2R}$

Current through inductor immediately **after** switch is opened  
is the same as  
the current through inductor immediately **before** switch is opened

Before switch is opened:

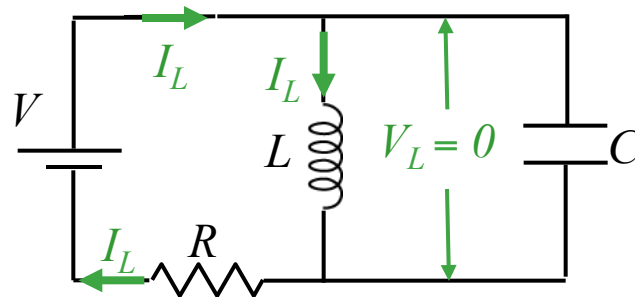


$$V_L = 0$$
$$\downarrow$$
$$V = I_L R$$

# Calculation



The switch in the circuit shown has been closed for a long time. At  $t = 0$ , the switch is opened.

**Hint:** Energy is conserved

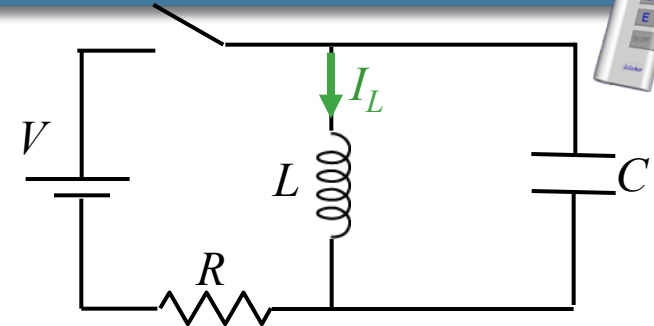

$$I_L(t = 0+) = V/R \quad V_C(t = 0+) = 0$$


What is  $Q_{\max}$ , the maximum charge on the capacitor during the oscillations?

**A)**  $Q_{\max} = \frac{V}{R} \sqrt{LC}$

**B)**  $Q_{\max} = \frac{1}{2} CV$


**C)**  $Q_{\max} = CV$

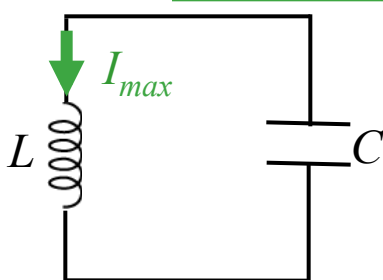**D)**  $Q_{\max} = \frac{V}{R\sqrt{LC}}$



When  $I$  is *max*  
(and  $Q$  is 0)

$$U = \frac{1}{2} LI_{\max}^2$$

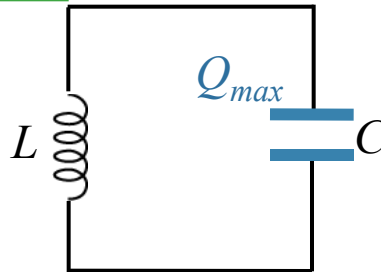

When  $Q$  is *max*  
(and  $I$  is 0)

$$U = \frac{1}{2} \frac{Q_{\max}^2}{C}$$



$$\frac{1}{2} LI_{\max}^2 = \frac{1}{2} \frac{Q_{\max}^2}{C}$$

$$Q_{\max} = I_{\max} \sqrt{LC}$$


$$= \frac{V}{R} \sqrt{LC}$$
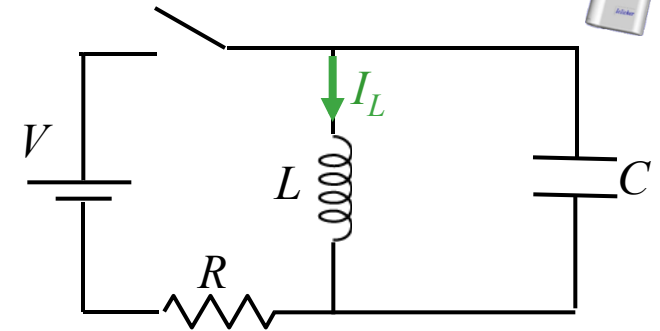
# Follow-Up



The switch in the circuit shown has been closed for a long time. At  $t = 0$ , the switch is opened.

Is it possible for the maximum voltage on the capacitor to be greater than  $V$ ?



A) YES

B) NO

$$I_{\max} = V/R \qquad Q_{\max} = \frac{V}{R} \sqrt{LC}$$

$$Q_{\max} = \frac{V}{R} \sqrt{LC} \rightarrow V_{\max} = \frac{V}{R} \sqrt{\frac{L}{C}} \rightarrow V_{\max} \text{ can be greater than } V \text{ IF: } \sqrt{\frac{L}{C}} > R$$

We can rewrite this condition in terms of the resonant frequency:

$$\omega_0 L > R \quad \text{OR} \quad \frac{1}{\omega_0 C} > R$$

We will see these forms again when we study  $AC$  circuits!