

Electric Current

Physics 212 *Lecture 9*

Today's Concept:

Ohm's Law, Resistors in circuits

Your comments

It's nice that the new material is a little easier to understand while there's an exam coming up. If this was by design when the course was made, thank you.

I just want to know why we aren't doing any sort of review the day before a midterm. That really sucks you know, some of us have a job on top of being a full time student. No review and just plowing through topics without any sort of break is awful.

Quick Q: Why is an E-Field created inside the conducting copper wire? It was explained a bit in the prefecture. But I thought that, "CONDUCTOR" " $E=0!!$ " right?

Can we talk more about current density?

I don't know if i have the capacity to see another bad joke in lecture, but I currently can't resist.

Oh my gosh I'm so nervous for the midterm ahhh!!!!!!!

I don't expect to have a review session in class on Tuesday, but I'm not going to say that that wouldn't make me feel at least a bit better about Wednesday's exam.

Can you go more into depth about ne I don't exactly understand that.

Could we go over current density before? I have seen $V=IR$ and resistors before, but that is new.

Exam Logistics

1) EXAM 1: WED February 18th at 7pm

- Sign Up in Gradebook for Conflict Exam at 5:15pm if desired
- If you have double conflict please email Prof. Ben Hooberman
- MATERIAL: Lectures 1 - 8

2) EXAM 1 PREPARATION

- Study HW, Disc
- Old Exams are
- See SmartPhys

3) Extra Office Hours (Tues rooms/times)

Tuesday, February 17 | 9:30 AM | [tstetzer@illinois.edu](#) | [account](#) | [log off](#)

smartPhysics
Powered by smartFramework

PHYS 212 Spring 2015
University of Illinois

[Home](#) [Calendar](#) [Assignments](#) [Instructor Links](#) [Administrator Links](#)

[Instructor](#) [Student Stetzer, Timothy](#)

[+] Go to current unit

- + Electricity
- + DC Circuits
- + Magnetism
- + AC Circuits
- + Light and Optics

- Exam Review Solutions [Edit Title](#)

29. Past Hour Exam 1 Solutions [Edit Title](#)

Copy an Assignment	New Prelecture	New Checkpoint Set	New Homework Set
Prelecture - Fall 2010 Exam 1 Solu...	-- Optional --	Due: May, 13 at 8:00 AM	
Homework - Spring 2014 Exam 1	-- Optional --	Due: May, 12 at 8:00 AM	
Homework - Spring 2015 Exam	-- Optional --	Start: Feb. 18 at 10:00 PM / Due: May, 12 at 8:00 AM	

Unassigned Assignments
The assignments below can be added to the Course schedule via the Calendar.
[Homework - Hour Exam 1 Version](#)

- 30. Hour Exam 2 (Fall 2010 Solutions)
- 31. Hour Exam 3 (Spring 2013 w/ Solutions)
- 32. Final Exam (Lect 29)

Daily Planner

Thursday, February 19
8:00 am [Prelecture - Kirchhoff's Rules](#)
8:00 am [Checkpoint - Kirchhoff's Rules](#)

Tuesday, February 24
8:00 am [Homework - Electric Current](#)
8:00 am [Prelecture - RC Circuits](#)
8:00 am [Checkpoint - RC Circuits](#)

Thursday, February 26
8:00 am [Prelecture - Magnetism](#)
8:00 am [Checkpoint - Magnetism](#)

Tuesday, March 3
8:00 am [Homework - RC Circuits + Magnetism](#)
8:00 am [Prelecture - Forces And Toroues](#)

Announcements
[Add Announcement](#)

Copyright © 2015 Freeman Worth Publishers - a division of Macmillan Higher Education.
[About](#) | [Contact Us](#) | [Find Your Local Sales Rep](#) | [Privacy Policy](#)


macmillan
education

A Big Idea Review

Coulomb's Law

Force law between point charges
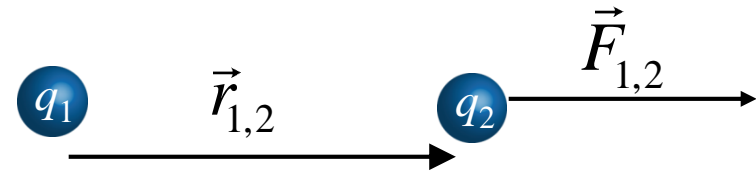
$$\vec{F}_{1,2} = \frac{kq_1q_2}{r_{1,2}^2} \hat{r}_{1,2}$$



Electric Field

Force per unit charge

$$\vec{E} \equiv \frac{\vec{F}}{q}$$

Electric Field

Property of Space
Created by Charges
Superposition

Gauss' Law

Flux through closed surface is always proportional to charge enclosed

$$\int \vec{E} \cdot d\vec{A} = \frac{Q_{enc}}{\epsilon_0}$$

Gauss' Law

Can be used to determine E field



Spheres
Cylinders
Infinite Planes

Electric Potential

Potential energy per unit charge

$$\Delta V_{a \rightarrow b} \equiv \frac{\Delta U_{a \rightarrow b}}{q} = - \int_a^b \vec{E} \cdot d\vec{l}$$

Capacitance

Relates charge and potential for two conductor system

$$C \equiv \frac{Q}{V}$$

Electric Potential

Scalar Function that can be used to determine E

$$\vec{E} = -\vec{\nabla} V$$

Applications of Big Ideas

Conductors
Charges free to move



What Determines
How They Move?




They move until
 $E = 0$!




$E = 0$ in conductor
determines charge
densities on surfaces

Spheres
Cylinders
Infinite Planes

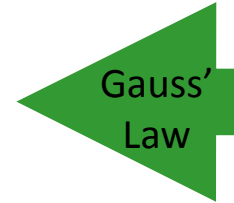

Field Lines &
Equipotentials

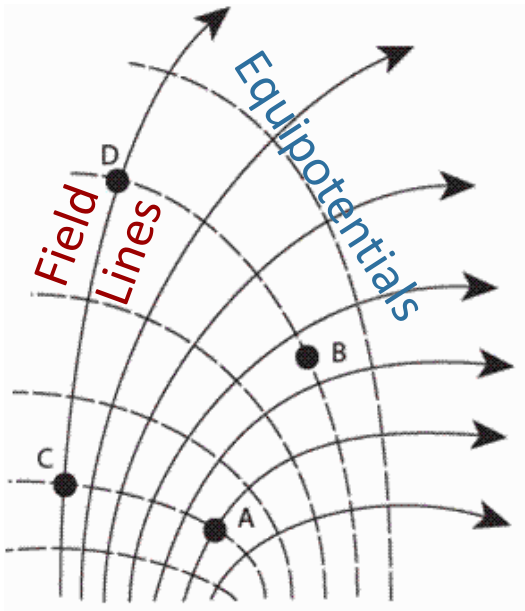


Work Done By E Field

$$W_{a \rightarrow b} = \int_a^b \vec{F} \cdot d\vec{l} = \int_a^b q\vec{E} \cdot d\vec{l}$$

Change in Potential Energy

$$\Delta U_{a \rightarrow b} = -W_{a \rightarrow b} = -\int_a^b q\vec{E} \cdot d\vec{l}$$

Capacitor Networks

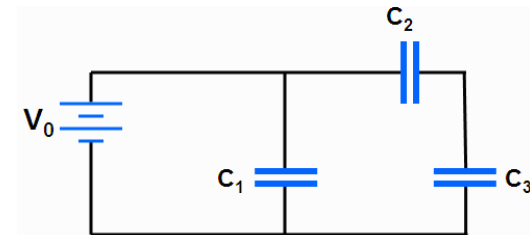

Series:

$$(1/C_{23}) = (1/C_2) + (1/C_3)$$

Parallel

$$C_{123} = C_1 + C_{23}$$


Current and Resistance


Key Concepts:

- 1) How resistance depends on A , L , σ , r
- 2) How to combine resistors in series and parallel
- 3) Understanding resistors in circuits

Today's Plan:

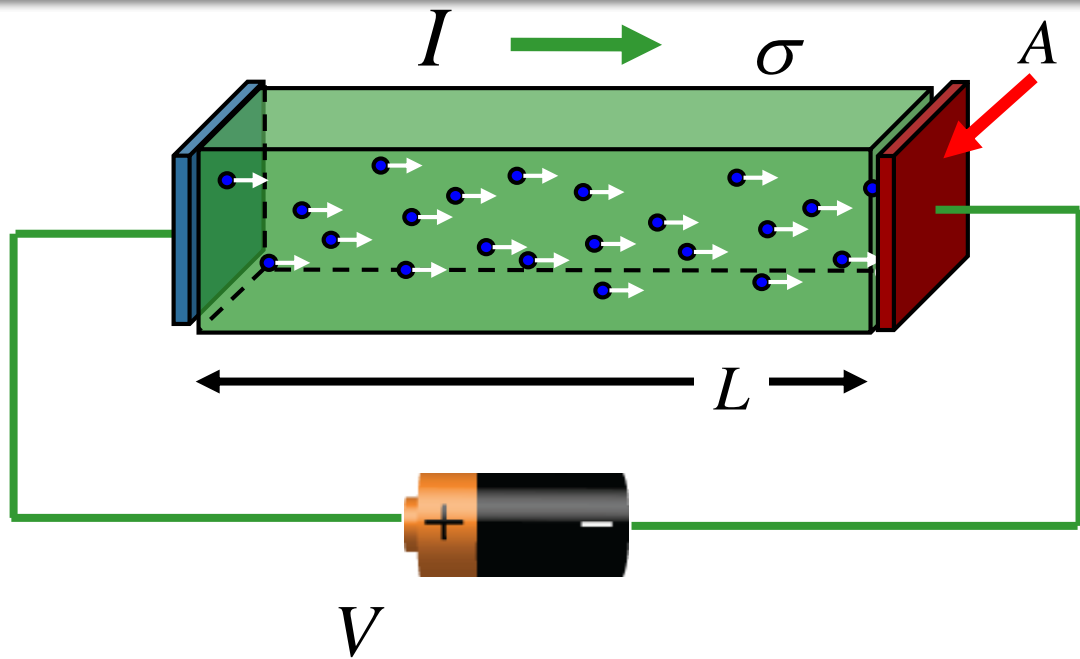- 1) Review of resistance & preflights
- 2) Work out a circuit problem in detail



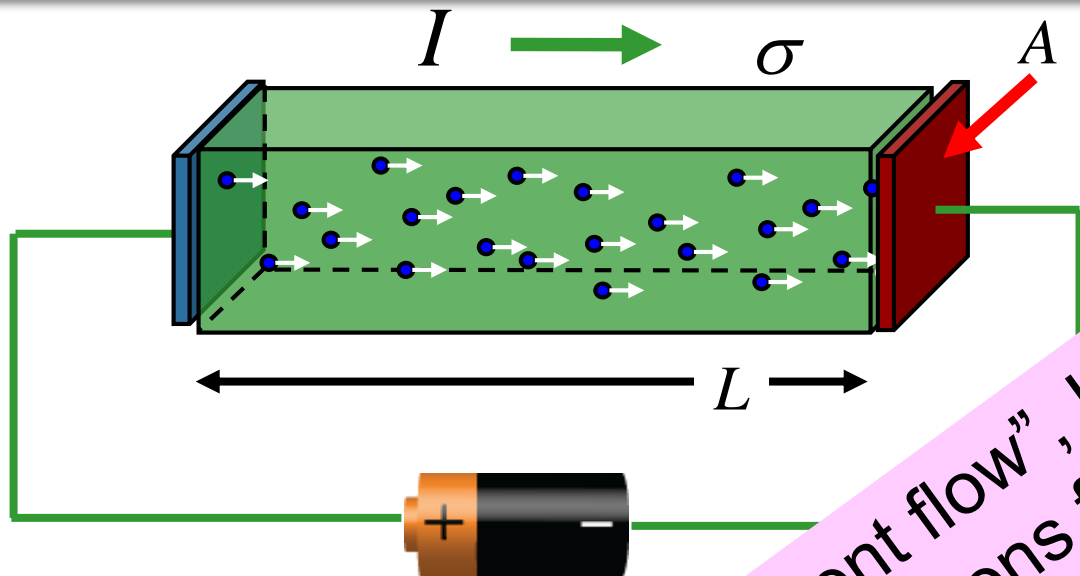

Ohm's Law: $V = EL$

Current density: $J = \sigma E$

Observables:

$$V = EL$$

$$I = JA$$

$$J = \sigma V/L$$

$$I = V/(L/\sigma A)$$

Resistance

$$\rho = 1/\sigma$$

$$I = V/R$$


$$R = \frac{L}{\sigma A}$$

Note: "Conventional current flow", I , is opposite to direction electrons flow

Conductivity – high for good conductors.

CheckPoint 3

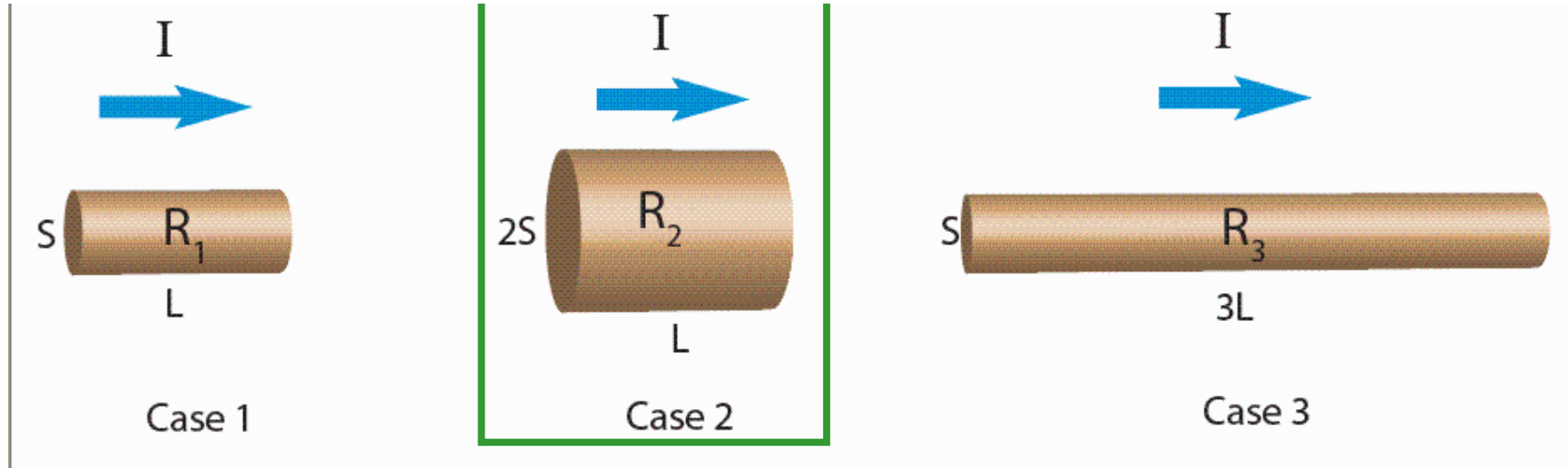The SAME amount of current I passes through three different resistors. R_2 has twice the cross-sectional area and the same length as R_1 , and R_3 is three times as long as R_1 but has the same cross-sectional area as R_1 .



In which case is the CURRENT DENSITY through the resistor the smallest?

A. Case 1


B. Case 2

C. Case 3

$$J \equiv \frac{I}{A} \quad \longrightarrow \quad J_1 = J_3 = 2J_2$$

Same Current $\longrightarrow J \propto \frac{1}{A}$

Current Density: Question 1 (N = 814)

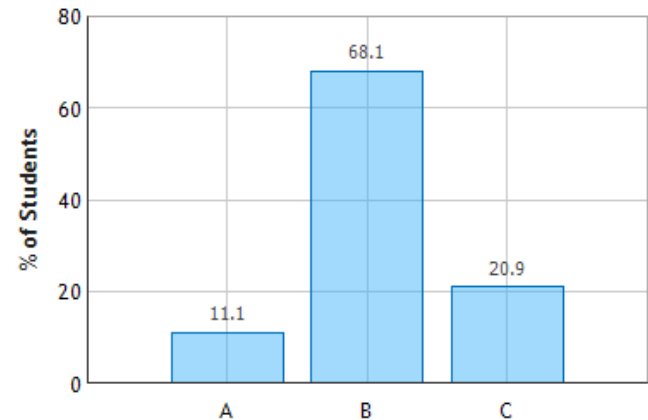

This is just like Plumbing!

I is like flow rate of water

V is like pressure


R is how hard it is for water to flow in a pipe

$$R = \frac{L}{\sigma A}$$

To make R big, make L long or A small




To make R small, make L short or A big

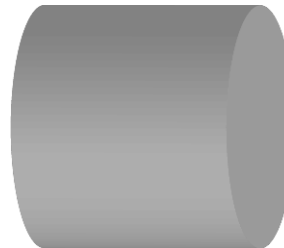


CheckPoint 1a

CheckPoint 1b

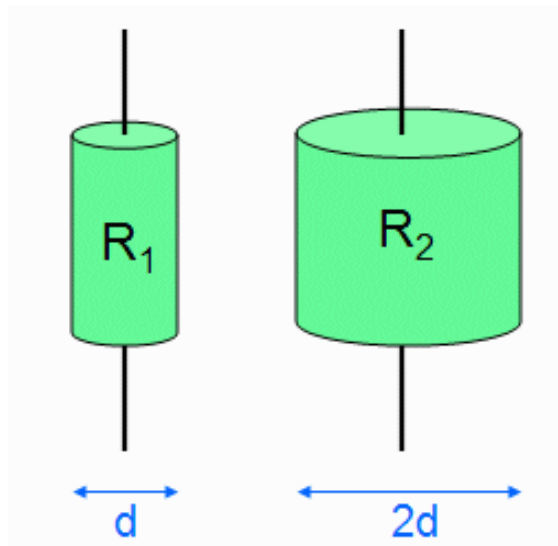

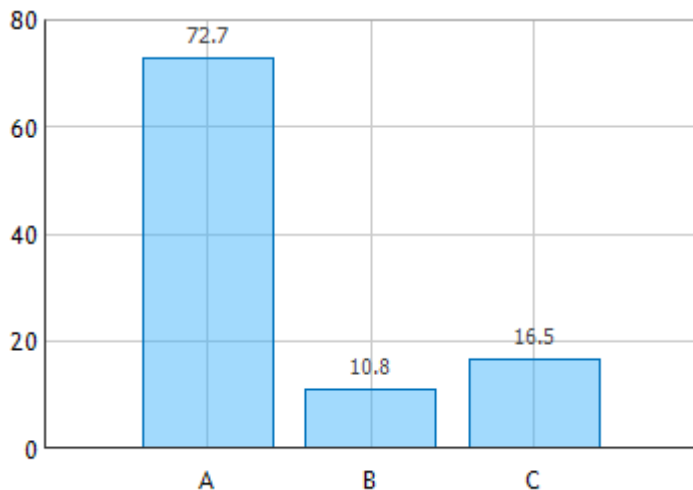☒ $V_1 > V_2$
☐ $V_1 = V_2$
☐ $V_1 < V_2$




Same current through both resistors


Compare voltages across resistors

$$R \propto \frac{L}{A}$$

$$V = IR \propto \frac{L}{A}$$

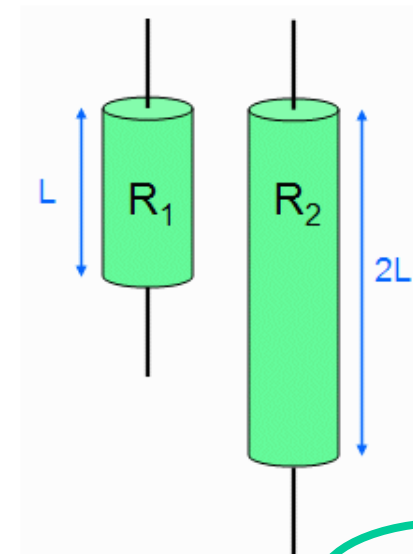

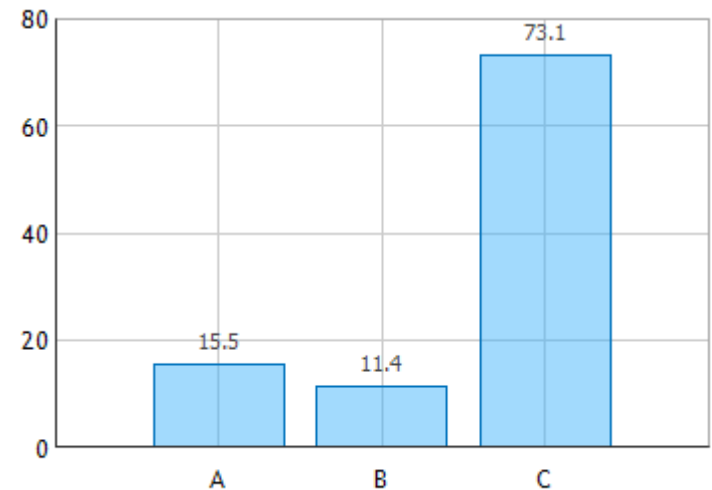
☐ $V_1 > V_2$
☐ $V_1 = V_2$
☒ $V_1 < V_2$



Resistor Summary

Series

Every loop with R_1 also has R_2

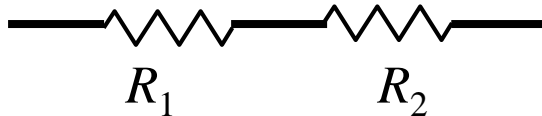

Each resistor on the same wire.

Different for each resistor.

$$V_{total} = V_1 + V_2$$

Same for each resistor


$$I_{total} = I_1 = I_2$$

Increases

$$R_{eq} = R_1 + R_2$$

Parallel

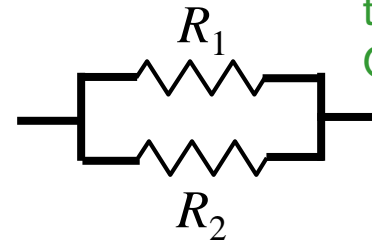There is a loop that contains ONLY R_1 and R_2



Each resistor on a different wire.

Same for each resistor.

$$V_{total} = V_1 = V_2$$

Different for each resistor

$$I_{total} = I_1 + I_2$$

Decreases

$$1/R_{eq} = 1/R_1 + 1/R_2$$

Wiring


Voltage

Current


Resistance

CheckPoint 2a

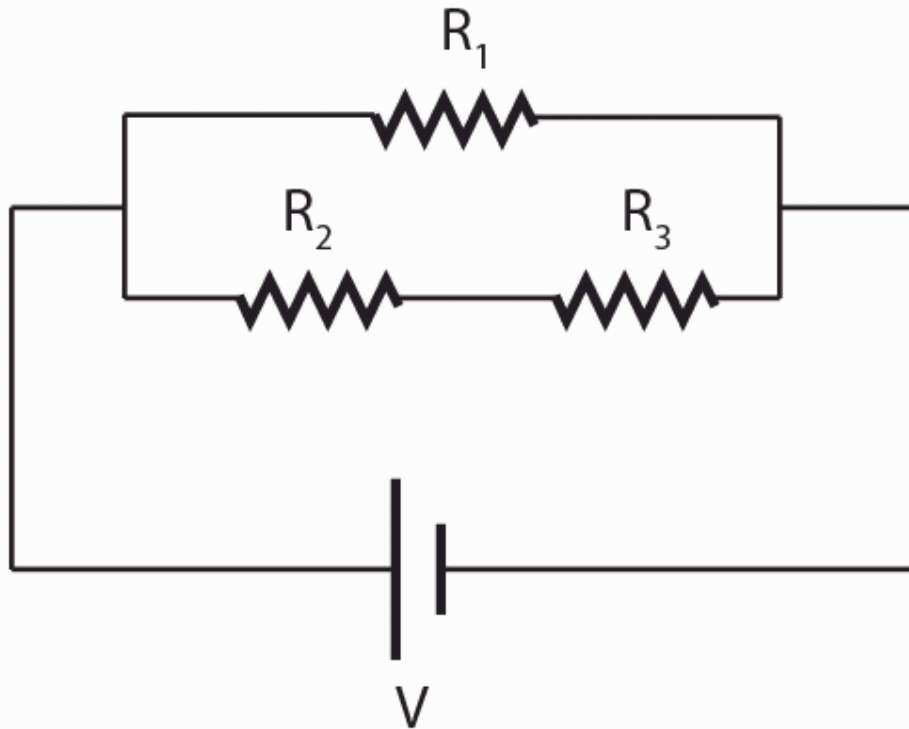Three resistors are connected to a battery with emf V as shown. The resistances of the resistors are all the same, i.e. $R_1 = R_2 = R_3 = R$.



Resistor Network: Question 1 (N = 814)

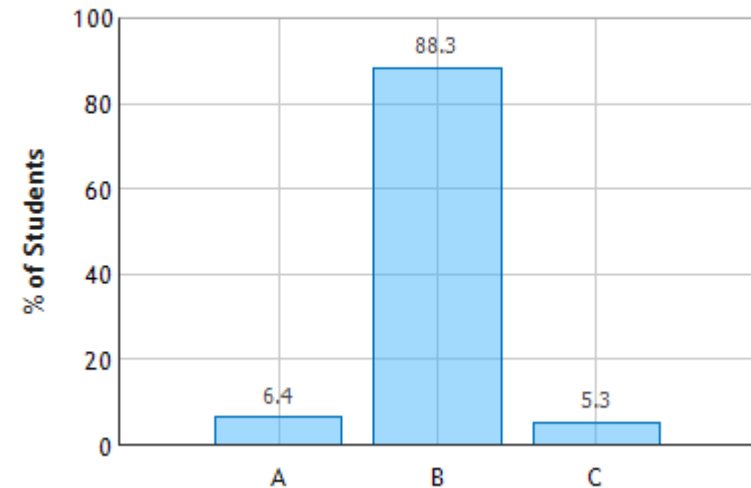

Compare the current through R_2 with the current through R_3 :

A. $I_2 > I_3$

B. $I_2 = I_3$

C. $I_2 < I_3$


R_2 in series with R_3



Current through R_2 and R_3 is the same

$$I_{23} = \frac{V}{R_2 + R_3}$$

Checkpoint 2b

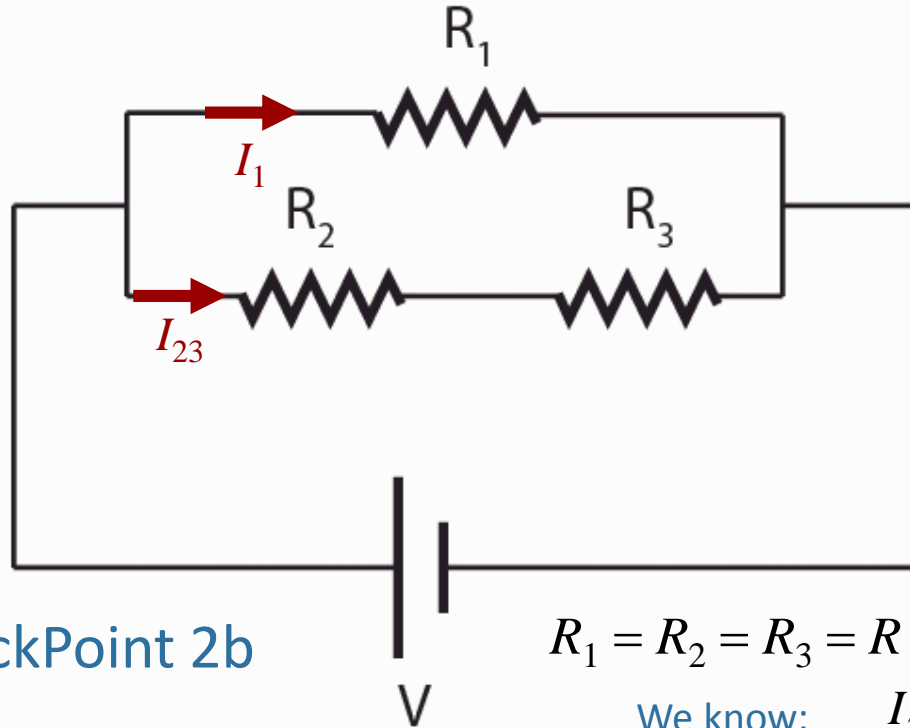

CheckPoint 2b

Compare the current through R_1 with the current through R_2

- A $I_1/I_2 = 1/2$
- B $I_1/I_2 = 1/3$
- C $I_1/I_2 = 1$
- D $I_1/I_2 = 2$**
- E $I_1/I_2 = 3$

We know:

$$I_{23} = \frac{V}{R_2 + R_3}$$

Similarly:

$$I_1 = \frac{V}{R_1}$$





$$I_1 = I_{23} \frac{R_2 + R_3}{R_1}$$




$$\frac{I_1}{I_{23}} = \frac{R_2 + R_3}{R_1} = 2$$

Resistor Network: Question 2 (N = 814)

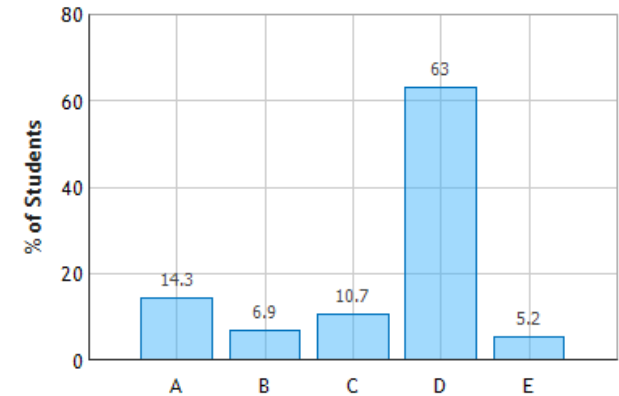

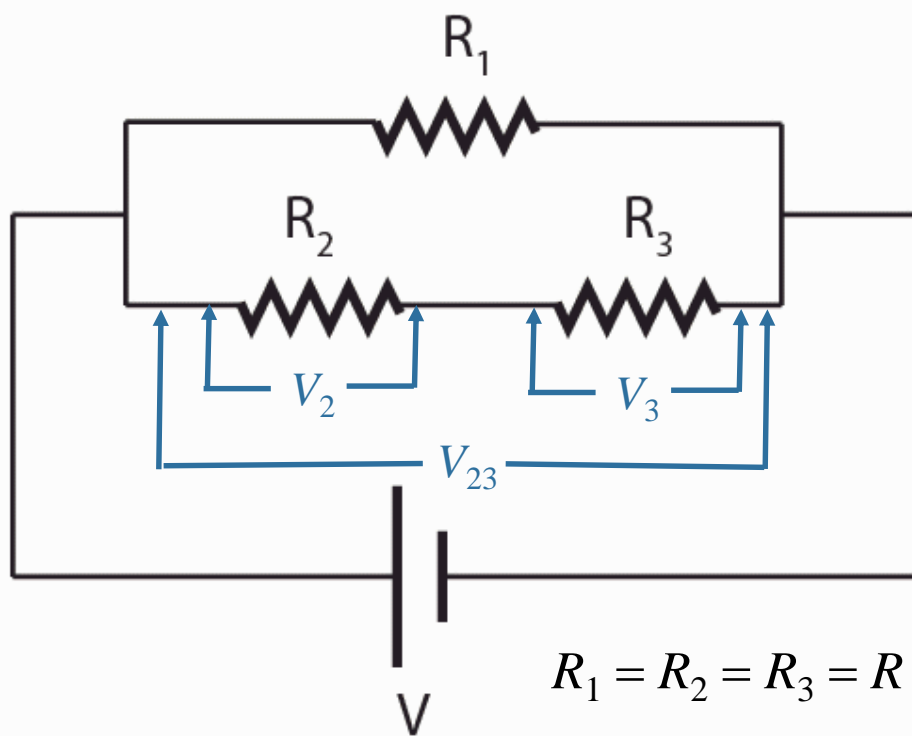

Resistor Network: Question 5 (N = 814)

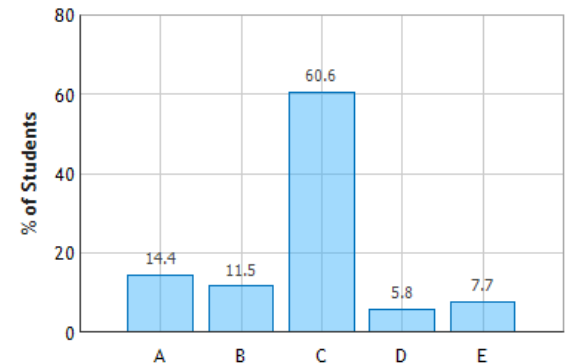

CheckPoint 2c

Compare the voltage across R_2 with the voltage across R_3

A $V_2 > V_3$

B $V_2 = V_3 = V$

C $V_2 = V_3 < V$

D $V_2 < V_3$

$$V_2 = I_2 R_2$$

$$V_3 = I_3 R_3$$


$I_2 = I_3$ (Series)
 $R_2 = R_3$ (Problem statement)

$$V_2 = V_3$$

$$V_{23} = V$$

$$V_{23} = V_2 + V_3$$

$$V_2 = V_3 = \frac{V}{2}$$

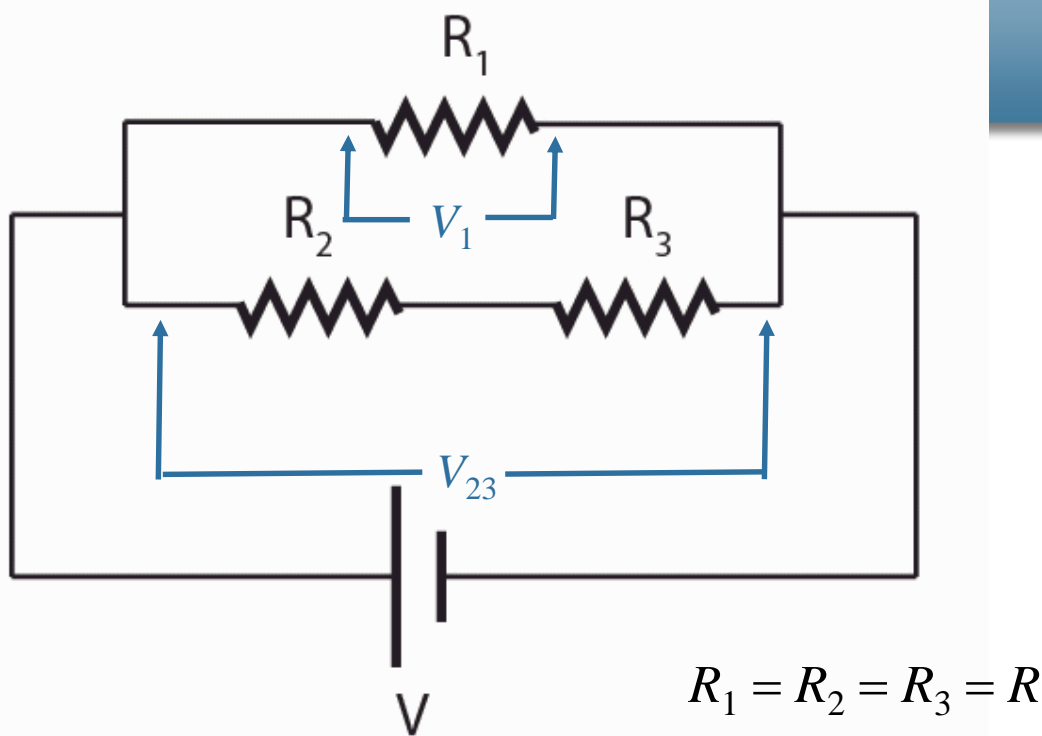

CheckPoint 2d

Compare the voltage across R_1 with the voltage across R_2

A $V_1 = V_2 = V$

B $V_1 = \frac{1}{2} V_2 = V$

C $V_1 = 2V_2 = V$

D $V_1 = \frac{1}{2} V_2 = \frac{1}{5} V$

E $V_1 = \frac{1}{2} V_2 = \frac{1}{2} V$

R_1 in parallel with series combination of R_2 and R_3


$$V_1 = V_{23}$$

$$R_2 = R_3 \Rightarrow V_2 = V_3$$


$$V_{23} = V_2 + V_3 = 2V_2$$

$$\longrightarrow V_1 = 2V_2 = V$$

Resistor Network: Question 5 (N = 814)

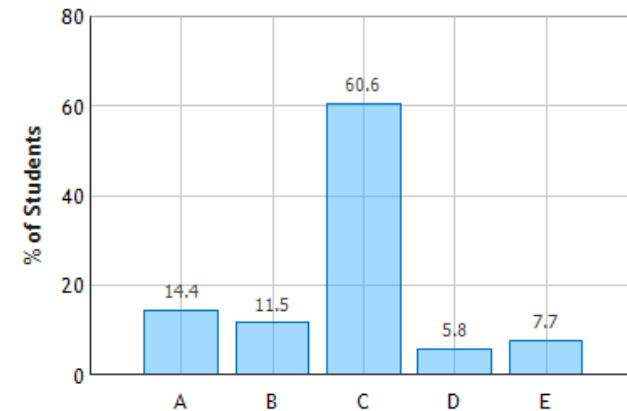

Calculation

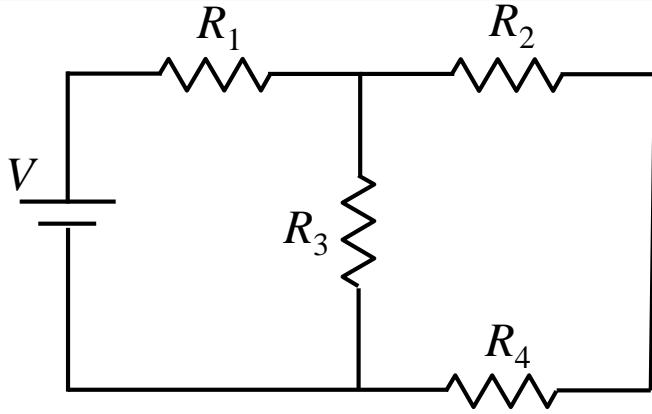

In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.

What is V_2 , the voltage across R_2 ?

Conceptual Analysis:

Ohm's Law: when current I flows through resistance R , the potential drop V is given by:
 $V = IR$.

Resistances are combined in series and parallel combinations

$$R_{series} = R_a + R_b$$

$$(1/R_{parallel}) = (1/R_a) + (1/R_b)$$


Strategic Analysis:

Combine resistances to form equivalent resistances

Evaluate voltages or currents from Ohm's Law

Expand circuit back using knowledge of voltages and currents

Calculation

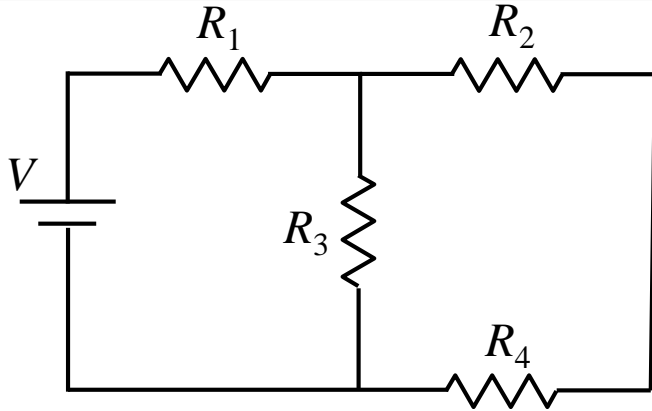

In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.

What is V_2 , the voltage across R_2 ?


Combine Resistances:

R_1 and R_2 are connected:


A) in series

B) in parallel

C) neither in series nor in parallel

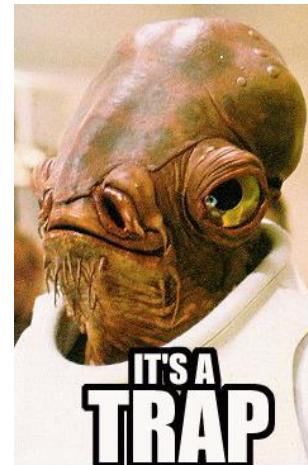

Parallel Combination

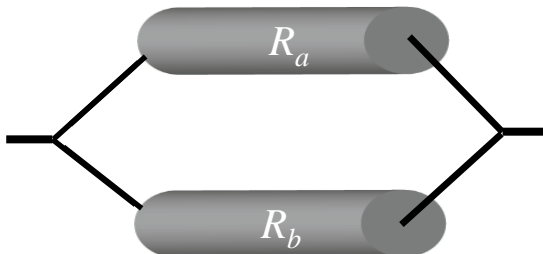


Parallel: Can make a loop that contains only those two resistors

Series Combination



Series : Every loop with resistor 1 also has resistor 2.

Calculation

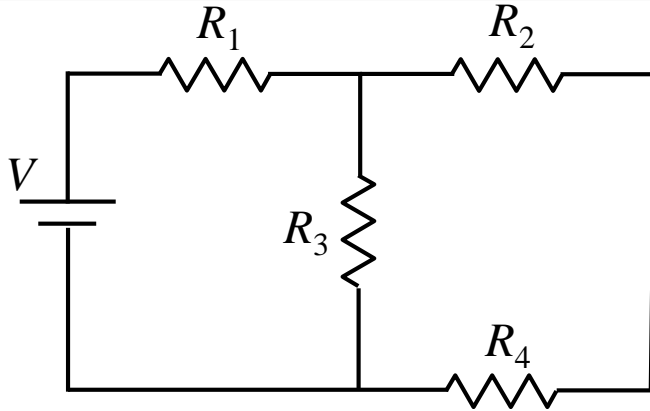

In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.


What is V_2 , the voltage across R_2 ?

We first will combine resistances R_2 , R_3 , R_4 :

Which of the following is true?

- A) R_2 , R_3 and R_4 are connected in series
- B) R_2 , R_3 , and R_4 are connected in parallel
- C) R_3 and R_4 are connected in series (R_{34}) which is connected in parallel with R_2
- D) R_2 and R_4 are connected in series (R_{24}) which is connected in parallel with R_3**
- E) R_2 and R_4 are connected in parallel (R_{24}) which is connected in parallel with R_3

Calculation

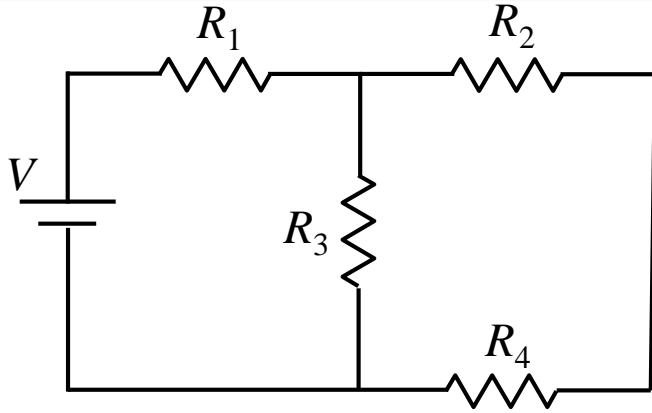


In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.


What is V_2 , the voltage across R_2 ?

R_2 and R_4 are connected in series (R_{24}) which is connected in parallel with R_3

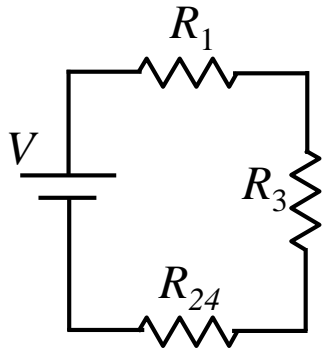
Redraw the circuit using the equivalent resistor R_{24} = series combination of R_2 and R_4 .



(A)

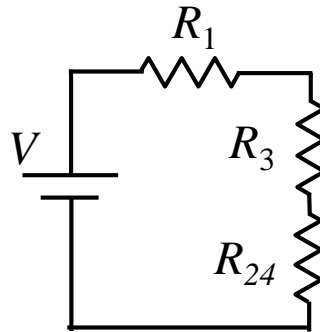


(B)

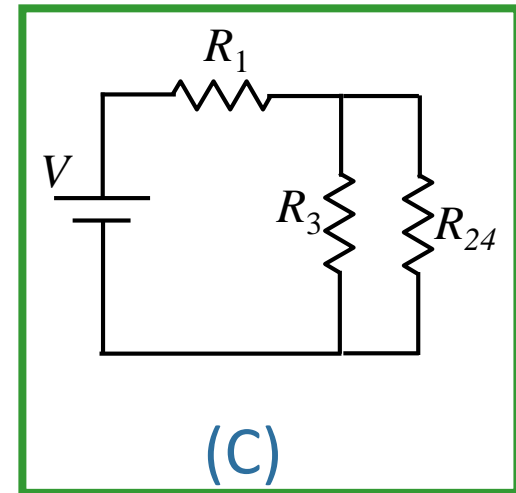

(C)

Calculation

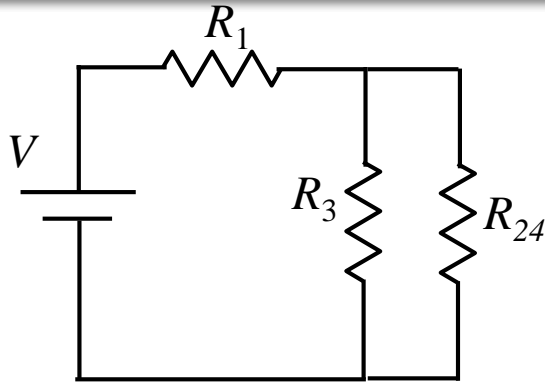

In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.

What is V_2 , the voltage across R_2 ?

Combine Resistances:

R_2 and R_4 are connected in series $= R_{24}$

R_3 and R_{24} are connected in parallel $= R_{234}$


What is the value of R_{234} ?

A) $R_{234} = 1\Omega$ B) $R_{234} = 2\Omega$ C) $R_{234} = 4\Omega$ D) $R_{234} = 6\Omega$

R_2 and R_4 in series $\rightarrow R_{24} = R_2 + R_4 = 2\Omega + 4\Omega = 6\Omega$

$(1/R_{\text{parallel}}) = (1/R_a) + (1/R_b) \rightarrow 1/R_{234} = (1/3) + (1/6) = (3/6)\Omega^{-1} \rightarrow R_{234} = 2\Omega$

Calculation

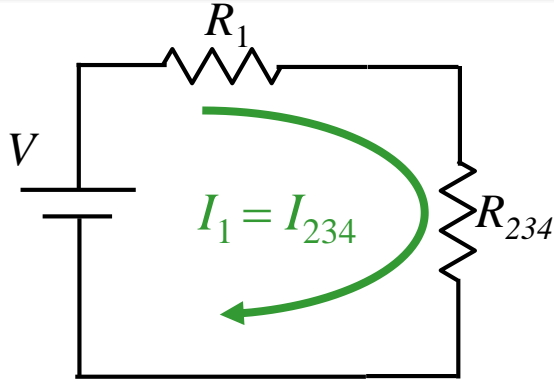


In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.

$$R_{24} = 6\Omega \quad R_{234} = 2\Omega$$

What is V_2 , the voltage across R_2 ?


R_1 and R_{234} are in series. $R_{1234} = 1 + 2 = 3\Omega$

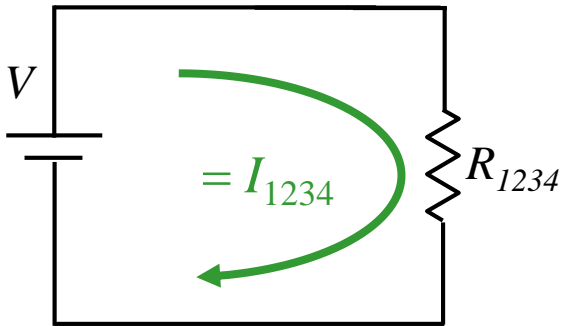Our next task is to calculate the total current in the circuit



Ohm's Law tells us:
$$\begin{aligned} I_{1234} &= V/R_{1234} \\ &= 18 / 3 \\ &= 6 \text{ Amps} \end{aligned}$$


Calculation

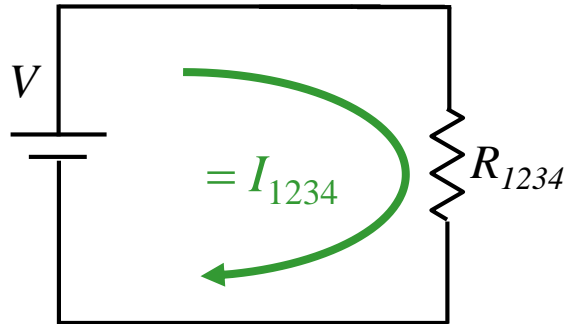

In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.

$$R_{24} = 6\Omega \quad R_{234} = 2\Omega \quad I_{1234} = 6A$$

What is V_2 , the voltage across R_2 ?

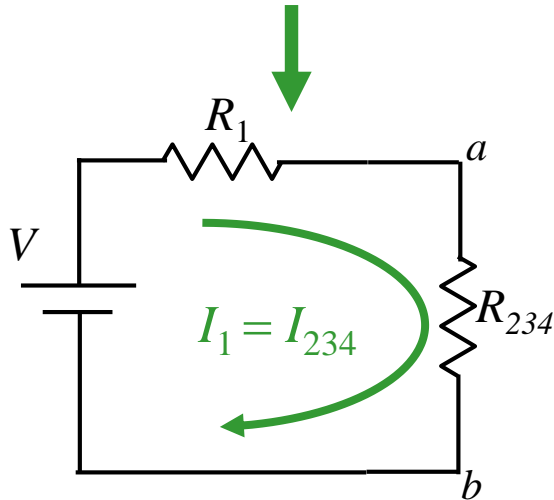

$$I_{234} = I_{1234} \quad \text{Since } R_1 \text{ in series with } R_{234}$$

$$\begin{aligned} V_{234} &= I_{234} R_{234} \\ &= 6 \times 2 \\ &= 12 \text{ Volts} \end{aligned}$$

What is V_{ab} , the voltage across R_{234} ?

A) $V_{ab} = 1V$


B) $V_{ab} = 2V$

C) $V_{ab} = 9V$

D) $V_{ab} = 12V$

E) $V_{ab} = 16V$

Calculation

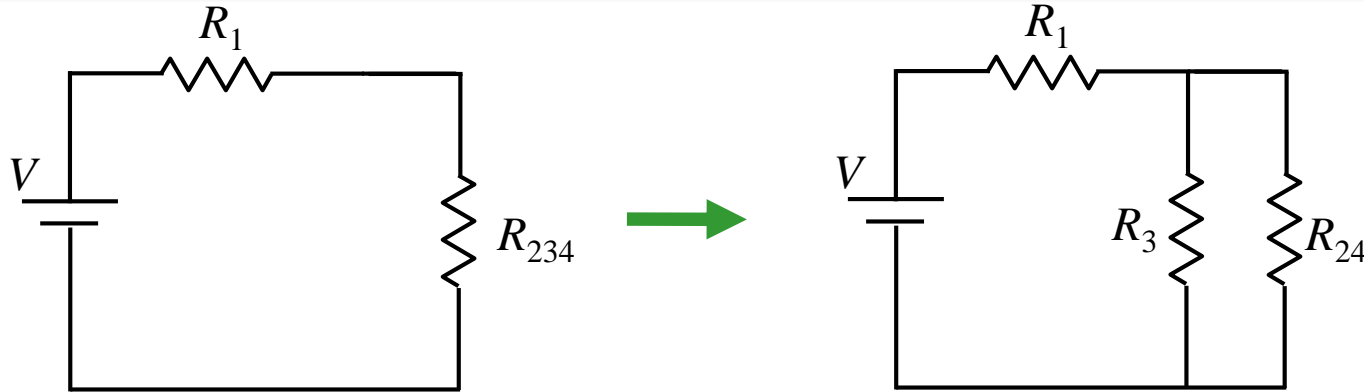

Which of the following are true?

A) $V_{234} = V_{24}$

B) $I_{234} = I_{24}$

C) Both A+B

D) None

$$V = 18V$$

$$R_1 = 1\Omega$$

$$R_2 = 2\Omega$$

$$R_3 = 3\Omega$$

$$R_4 = 4\Omega$$

$$R_{24} = 6\Omega$$

$$R_{234} = 2\Omega$$

$$I_{1234} = 6 \text{ Amps}$$

$$I_{234} = 6 \text{ Amps}$$

$$V_{234} = 12V$$

What is V_2 ?

R_3 and R_{24} were combined in parallel to get R_{234} → Voltages are same!



Ohm's Law

$$I_{24} = V_{24} / R_{24}$$

$$= 12 / 6$$

$$= 2 \text{ Amps}$$

Calculation

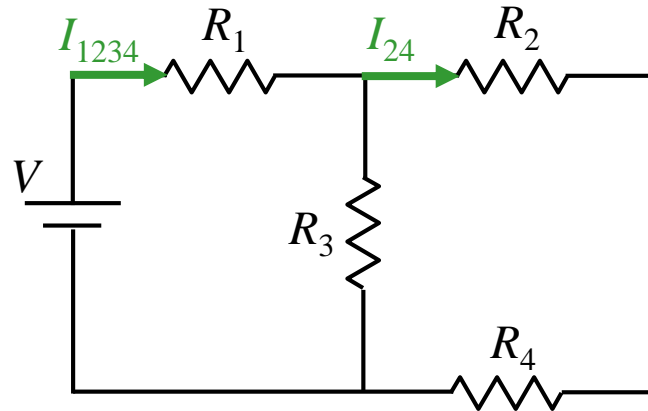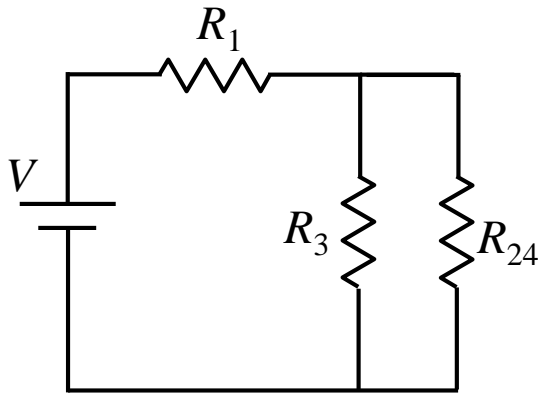

$$V = 18V$$

$$R_1 = 1\Omega$$

$$R_2 = 2\Omega$$

$$R_3 = 3\Omega$$

$$R_4 = 4\Omega$$

$$R_{24} = 6\Omega$$

$$R_{234} = 2\Omega$$

$$I_{1234} = 6 \text{ Amps}$$

$$I_{234} = 6 \text{ Amps}$$

$$V_{234} = 12V$$

$$V_{24} = 12V$$

$$I_{24} = 2 \text{ Amps}$$

What is V_2 ?

Which of the following are true?

- A) $V_{24} = V_2$ B) $I_{24} = I_2$ C) Both A+B D) None

R_2 and R_4 where combined in series to get R_{24} → Currents are same!

Ohm's Law


$$V_2 = I_2 R_2$$

$$= 2 \times 2$$

$$= 4 \text{ Volts!}$$

The Problem Can Now Be Solved!

Quick Follow-Ups

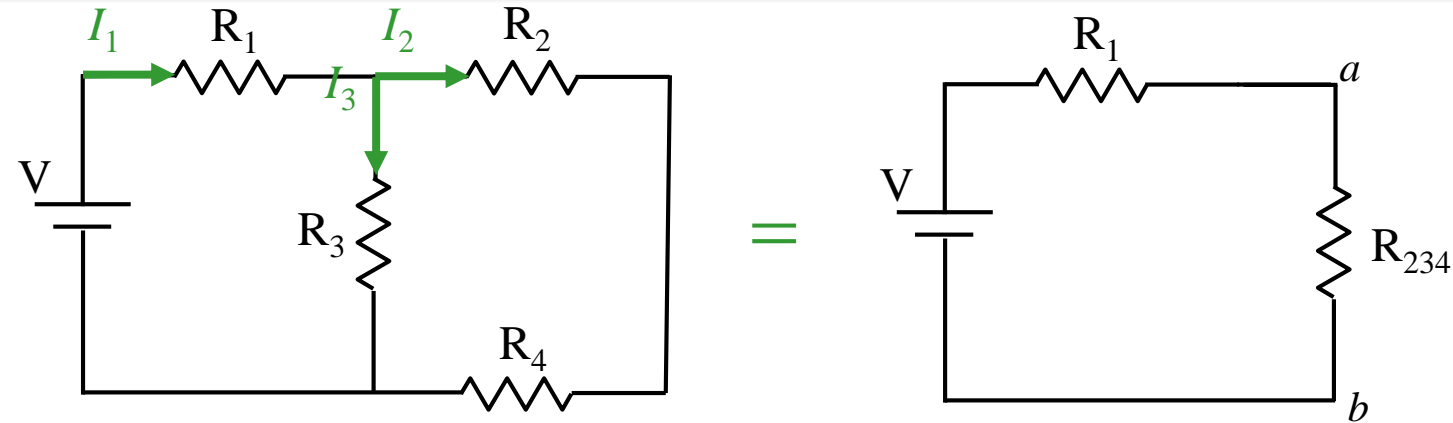

$$V = 18V$$

$$R_1 = 1\Omega$$

$$R_2 = 2\Omega$$

$$R_3 = 3\Omega$$

$$R_4 = 4\Omega$$

$$R_{24} = 6\Omega$$

$$R_{234} = 2\Omega$$

$$V_{234} = 12V$$

$$V_2 = 4V$$

$$I_{1234} = 6 \text{ Amps}$$

What is I_3 ?

A) $I_3 = 2 A$

B) $I_3 = 3 A$

C) $I_3 = 4 A$

$$V_3 = V_{234} = 12V \rightarrow I_3 = V_3/R_3 = 12V/3\Omega = 4A$$

What is I_1 ?

$$\text{We know } I_1 = I_{1234} = 6 A$$

NOTE: $I_2 = V_2/R_2 = 4/2 = 2 A$

$$\rightarrow I_1 = I_2 + I_3$$

Make Sense?