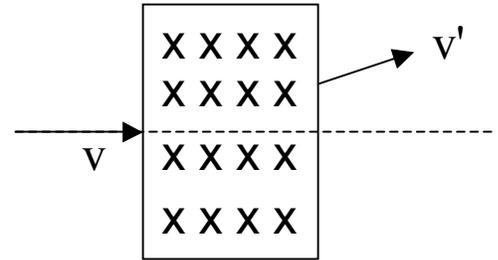


- 1) A proton (mass  $m$ , charge  $q$ ) moving at velocity  $v$  enters a region of constant magnetic field  $\mathbf{B}$  directed into the paper as shown. The proton exits the magnetic field region with velocity  $v'$  as shown. Compare  $v_x'$  (the  $x$ -component of this final velocity) with the initial velocity  $v$ . [4]




- (a)  $v_x' < v$                       (b)  $v_x' = v$                       (c)  $v_x' > v$

In the circuit below, the switch is initially open (as shown) and the capacitors are uncharged.

$$R_1 = 4 \, \Omega \quad C_1 = 40 \, \mu\text{F}$$

$$R_2 = 2 \, \Omega \quad C_2 = 20 \, \mu\text{F}$$

$$\mathcal{E} = 20\text{V}$$

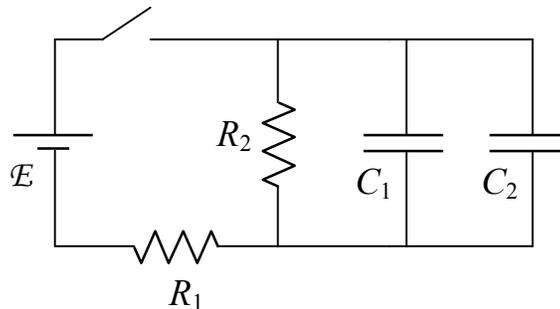


- 2) What is the current  $I_1$  through resistor  $R_1$  immediately after the switch is closed? [3]
- 3) What is the current  $I_1$  through resistor  $R_1$  after the switch has been closed for a long time? [3]

Initials: \_\_\_\_\_ Sec. \_\_\_\_\_

P212: Quiz 2 Week 7
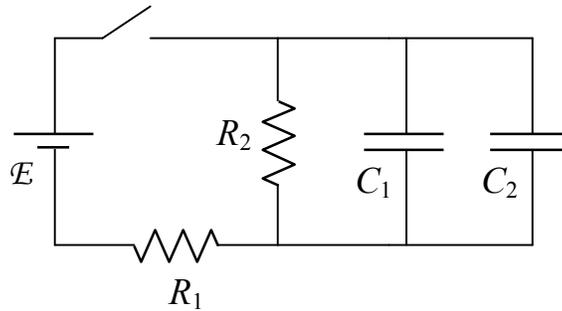
$$\begin{aligned} R_1 &= 4 \, \Omega & C_1 &= 40 \, \mu\text{F} \\ R_2 &= 2 \, \Omega & C_2 &= 20 \, \mu\text{F} \\ \mathcal{E} &= 20 \, \text{V} \end{aligned}$$



- 4) What is the charge  $Q_1$  on capacitor  $C_1$  a long time after the switch is closed? You will receive full credit for a correct algebraic or numerical answer. [6]
- 5) After a long time, the capacitors are fully charged and the switch is reopened. What is the time constant  $\tau$  for discharging the capacitors? Specify your answer in units of seconds. [4]