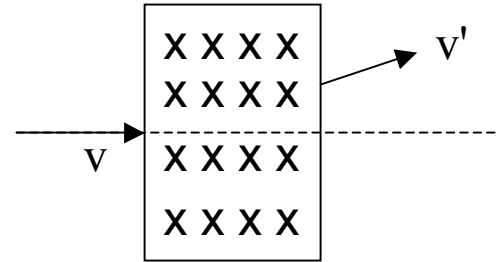


- 1) A proton (mass m , charge q) moving at velocity v enters a region of constant magnetic field \mathbf{B} directed into the paper as shown. The proton exits the magnetic field region with velocity v' as shown. Compare v_x' (the x -component of this final velocity) with the initial velocity v . [4]




- (a) $v_x' < v$ (b) $v_x' = v$ (c) $v_x' > v$

Rubric:

Correct solution (4)

In the circuit below, the switch is initially open (as shown) and the capacitors are uncharged.
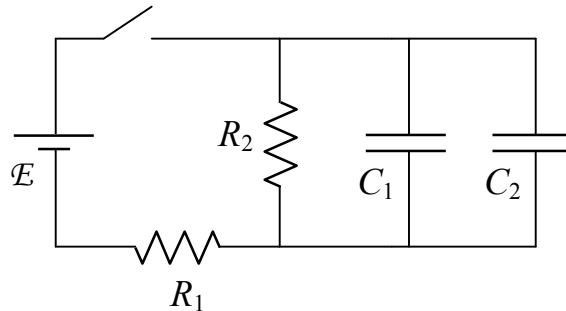
$$\begin{aligned} R_1 &= 4 \, \Omega & C_1 &= 40 \, \mu\text{F} \\ R_2 &= 2 \, \Omega & C_2 &= 20 \, \mu\text{F} \\ \mathcal{E} &= 20\text{V} \end{aligned}$$



- 2) What is the current I_1 through resistor R_1 immediately after the switch is closed? [3]

$$\Delta V_{\text{cap}} = 0 \text{ initially} \rightarrow \mathcal{E} - I_1 R_1 = 0 \rightarrow I_1 = 5\text{A}$$

Rubric:

Setup (2)

Answer (1)

- 3) What is the current I_1 through resistor R_1 after the switch has been closed for a long time? [3]


$$\mathcal{E} - I_1 (R_1 + R_2) = 0 \rightarrow I_1 = 3.33 \text{ A}$$

Rubric:

Setup (2)

Correct answer (1)
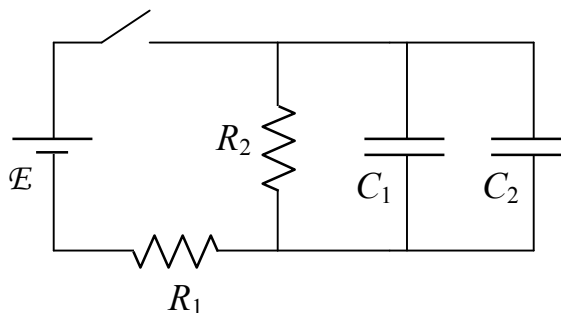
$$\begin{aligned} R_1 &= 4 \, \Omega & C_1 &= 40 \, \mu\text{F} \\ R_2 &= 2 \, \Omega & C_2 &= 20 \, \mu\text{F} \\ \mathcal{E} &= 20 \, \text{V} \end{aligned}$$



- 4) What is the charge Q_1 on capacitor C_1 a long time after the switch is closed? You will receive full credit for a correct algebraic or numerical answer. [6]

After a long time C_1 is like an open circuit

$$\Delta V = I_1 R_2 = \mathcal{E} R_2 / (R_1 + R_2) = Q_1 / C_1 \rightarrow Q_1 = 2.7 \cdot 10^{-4} \, \text{C}$$

Rubric:

Correct setup (4)

Correct answer (2)

- 5) After a long time, the capacitors are fully charged and the switch is reopened. What is the time constant τ for discharging the capacitors? Specify your answer in units of seconds. [4]

$$\tau = C_{12} R_2 = 1.2 \cdot 10^{-4} \, \text{s}$$

Rubric:

Correct formula (2)

Correct result (2)