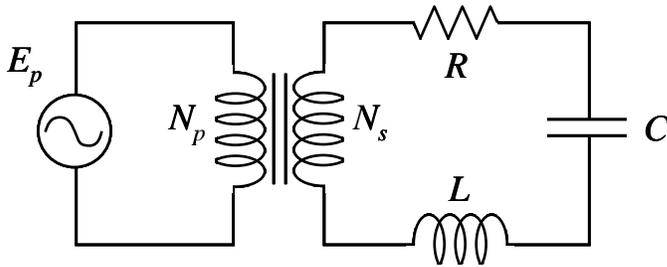


Discussion Question 12A
P212, Week 12
Power in AC Circuits

An electronic device, consisting of a simple RLC circuit, is designed to be connected to an American-standard power outlet delivering an EMF of $120 \text{ V}_{\text{rms}}$ at 60 Hz frequency. However, you have transported this device to Guyana, where standard AC power outlets deliver a blazing $240 \text{ V}_{\text{rms}}$. To overcome this problem, you connect your device to the Guyanese wall outlet through a step-down transformer with N_p turns in the primary coil and N_s turns in the secondary. The values of the resistance, capacitance, and inductance in your device are given in the figure.



$$\begin{aligned}
 E_{p,\text{rms}} &= 240 \text{ V} \\
 E_{\text{rms}} &= 120 \text{ V} \\
 f &= 60 \text{ Hz} \\
 R &= 3.8 \Omega \\
 L &= 0.05 \text{ H} \\
 C &= 177 \mu\text{F}
 \end{aligned}$$




(a) First, let's design the transformer. What relation must you impose on N_p and N_s to drop the Guyanese line voltage E_p down to $\mathcal{E} = 120 \text{ V}_{\text{rms}}$?

Try thinking physically: As is typical, your transformer has an iron core which ensures that the magnetic field produced in the primary coil is transferred exactly to the secondary coil. Now $\mathcal{E} = -d\Phi/dt \dots$ to step down the voltage, which coil needs to have more turns?

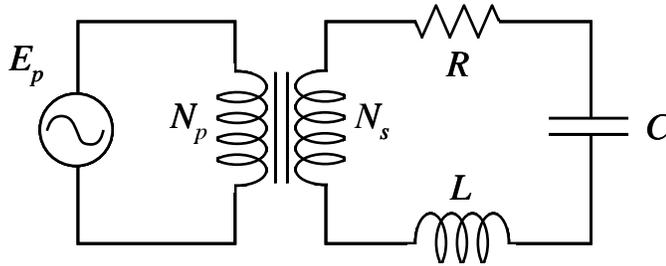(b) Let the time-dependent EMF produced by the Euro generator be $\mathcal{E}_p(t) = \mathcal{E}_{p,\text{max}} \sin(\omega t)$ which means $\mathcal{E}(t) = (120\sqrt{2}) \sin \omega t$ where $\mathcal{E}(t)$ EMF delivered to the secondary side of the transformer. What is the time-dependent current $I(t)$ produced in the load? Write your answer in the form $I(t) = I_{\text{max}} \sin(\omega t - \phi)$, and determine the numerical values of I_{max} and ϕ .

Discussion Question 12A
P212, Week 12
Power in AC Circuits



$$E_{p,rms} = 240 \text{ V}$$

$$E_{rms} = 120 \text{ V}$$

$$f = 60 \text{ Hz}$$

$$R = 3.8 \ \Omega$$

$$L = 0.05 \text{ H}$$

$$C = 177 \ \mu\text{F}$$

(c) What is the average power $\langle P \rangle$ delivered to the load?

Your formula sheet has a couple of “cookbook” formulas you can use.


(d) Obtain an algebraic expression for the $\langle P \rangle$ delivered to the load in terms of \mathcal{E}_{rms} , R , and $X \equiv X_L - X_C$. *Hint -write a phasor diagram for Z in terms of X and L and use trig to find the required phase angle.*

(e) Suppose your Guyanese AC generator has a *variable* frequency f , though the EMF it supplies is fixed at 240 V_{rms} . What f would you select so that the maximum possible power is delivered to your device? *Hint- sketch the expression for $\langle P \rangle$ you obtained in part (d) as a function of X . Which value of X maximizes $\langle P \rangle$? What frequency gives you that value for X ?*

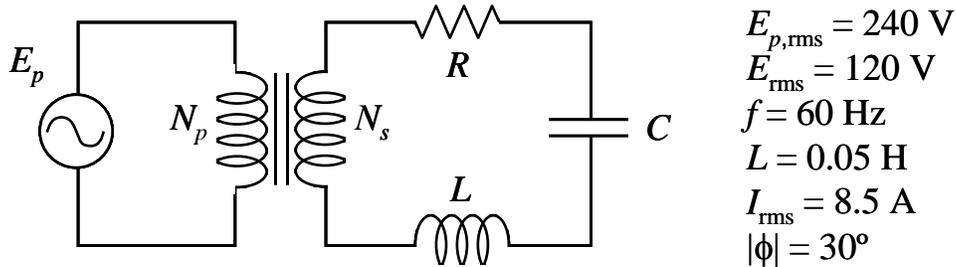(f) What is the maximum average power $\langle P \rangle_{max}$ that you can deliver to your device?

Discussion Question 12A
P212, Week 12
Power in AC Circuits

Consider a slightly different situation. Let's say you built your device to be purely inductive \rightarrow it contains nothing more than a coil you wound yourself, giving $L = 0.05$ H. However, no device is perfect: *every* electronic circuit element contains *some* residual inductance, capacitance, and resistance. You connect your device to the Guyanese wall outlet and measure the response in the load. You find a current with an rms value of $I_{\text{rms}} = 8.5$ A and lags the transformer EMF by 30° .



(g) What is the resistance R of your device?

You will need a couple of equations to “reverse engineer” this circuit: you measured the voltage, current, and phase and now you have to figure out R . Big hint: obtain an equation for R in terms of the impedance Z and the phase ϕ . (It's a useful equation, you might want to remember it!)

(h) What is the capacitance C of your device?

Discussion Question 12A
P212, Week 12
Power in AC Circuits

(i) In part (c), you probably used the average-power formula $\langle P \rangle = E_{\text{rms}} I_{\text{rms}} \cos(\phi)$ from your formula sheet (the others, like $\langle P \rangle = I_{\text{rms}}^2 R$, are equivalent). Let's derive that result! First, what is the instantaneous power $P(t)$ delivered to the load? Give an algebraic answer (no numbers) in terms of E_{rms} , I_{rms} , ϕ , ω , and t .

Instantaneous power is $P = IV$, forever and ever, under all circumstances. Remember the time-dependent expressions you found in part (b) ... and in preparation for the next question, you should “massage” your result using $\sin(a - b) = \sin a \cos b - \cos a \sin b$.

(j) Now calculate the time-average of your result for $P(t)$ over one cycle to obtain the average power $\langle P \rangle$ delivered to the load.

Remember, the average of \sin^2 and \cos^2 is $1/2$, while the average of $(\sin \cdot \cos)$ is zero.