

**Discussion Question 6B**  
**P212, Week 6**  
*Kirchhoff's Law Analysis of a Resistor Network*

So we now have two methods for analyzing resistor networks. Which one should we use?


(i) It depends on the particular problem, and (ii) often a *mixture* of methods is the best.

In general, method 1 (successive combination of elements) is easier, but method 2 (Kirchhoff's Laws) is more powerful ... and some circuits simply *cannot* be analyzed with method 1 alone.

The circuit shown at right is a typical example: here we have *three* batteries and they prevent us from “collapsing” *any* of the resistors in groups, as none of them are in simple series or parallel combinations.

Our only chance is to use Kirchhoff's Laws!

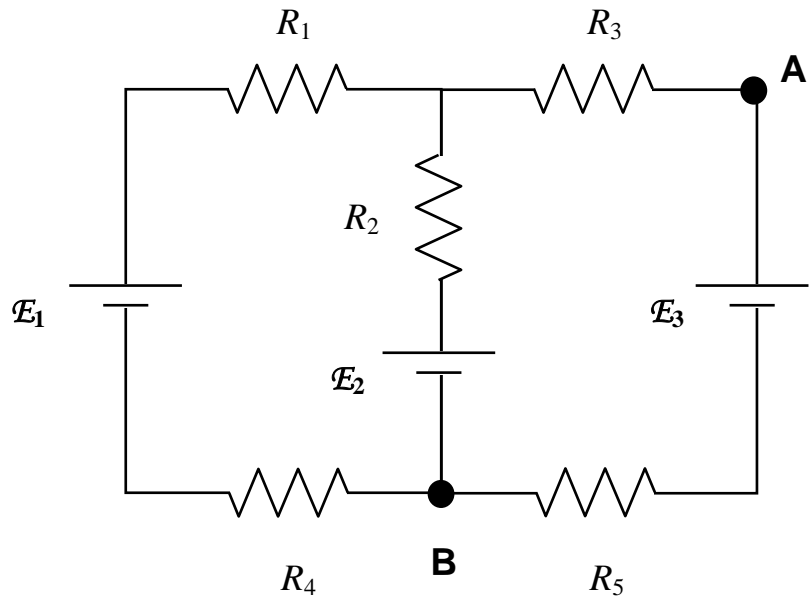Let all the resistors  $R_i$  have resistance  $10\ \Omega$ , and let the battery EMF's be  $\mathcal{E}_1 = 10\ \text{V}$ ,  $\mathcal{E}_2 = 20\ \text{V}$ ,  $\mathcal{E}_3 = 30\ \text{V}$ . Your tasks are:



(a) Find the **current  $I_3$**  through resistor  $R_3$ .

(b) Find the electric **potential difference,  $V_A - V_B$** , for the points A and B indicated on the circuit.